 


ALL INDIA 1st RANK 19 TIMES IN GATE

&

ALL INDIA 2nd RANK 10 TIMES IN GATE



ACE EDUCATIONAL ACADEMY

H.O : 204, Rahman Plaza, Opp: Methodist School, Fernandez Hospital Lane,
Abids, Hyderabad. Ph: 040 – 24752469 / 24750437

B.O : 201 A & B, Pancom Business Centre, Opp: J.C.Brothers, Ameerpet,
Hyderabad. Ph: 040 – 65974465

website: www.aceenggacademy.com email: ace.gateguru@gmail.com

ACE ENGINEERING ACADEMY
HYDERABAD.

Rohini

Congratulations!!

Our Top Ranks (within 100) in GATE-2009

EEE

S. No	Name	GATE Hall Ticket No.	Rank	GATE SCORE	GATE PERCENTILE
1	Anil Kumar Adapa	EE 6240284	2 *	1000	99.99
2	Girishkumar Dasari	EE 6760582	7 *	1000	99.97
3	V Narasimha Murthy	EE 7640633	13	1000	99.94
4	M. Nagarjuna Reddy	EE 7630195	14	1000	99.93
5	Thokare Nithin D	EE 1600530	18	1000	99.92
6	D chandra Mouli	EE 7640509	21	982	99.9
7	Ashish Kumar Nanda	EE 1620466	31	912	99.86
8	E. Ravi Kumar	EE 1450424	38	879	99.83
9	Shiva Sekhar Yellapu	EE 1540004	39	874	99.82
10	M. Leela Krishna	EE 1560672	39	874	99.82
11	M Sreekanth Reddy	EE 1540352	42	863	99.79
12	B. Narasimha Reddy	EE 7020242	47	841	99.78
13	Venkata Rangasivaswaroop	EE 6760518	62	798	99.71
14	Naga Potha Rao G	EE 6790106	65	792	99.7
15	Bugga Amanulla	EE 1540554	79	776	99.62
16	Chinta Kuntaveeraiah	EE 1210228	79	776	99.62
17	Satish Kumar Mittapalli	EE 6610184	87	760	99.59
18	V. Sujayendra	EE 1600002	91	754	99.57
19	M. Vidya Sagar Reddy	EE 1450536	95	749	99.56
20	Naresh Adepu	EE 7680168	98	744	99.54

* Our test series candidates

ACE ENGINEERING ACADEMY
HYDERABAD.

Congratulations!!

Our Top Ranks (within 100) in GATE-2009

ECE

S No	Name	GATE Hall Ticket No.	Rank	GATE SCORE	GATE PERCENTILE
1	M. Yeshwanth	EC1440615	9	949	99.98
2	Sandeep Sharath Waikar	EC1460408	11	946	99.98
3	Girish M Prabhu	EC 1690004	13	927	99.97
4	Venkatesh Sasanapuri	EC1490210	16	918	99.96
5	Naveen Kumar K	EC1500400	18	914	99.96
6	V. Gopala Krishna Murthy	EC1320585	18	914	99.96
7	Nikhil M Duragkar	EC1500054	24	894	99.94
8	K Naveen Kumar	EC1580156	26	890	99.94
9	M. Kartheek	EC7630362	29	882	99.93
10	Chandra sekhar Reddy	EC7640504	33	874	99.93
11	T. Chaitanya Reddy	EC1420657	40	859	99.9
12	Md Asif Sheik	EC7290318	43	855	99.9
13	K.Subhasini	EC1410519	43	855	99.9
14	M. Mahender	EC1520240	46	847	99.89
15	A. Santhosh Kumar Reddy	EC1470246	46	847	99.89
16	M.Sreenivasulu	EC1400672	46	847	99.89
17	Kameshwar Atchutaram	EC1460676	55	839	99.87
18	MD. Musharaf ali Faruqui	EC1590628	55	839	99.87
19	S. Dev Sekhar	EC7620512	60	835	99.86
20	Hari Kiran M	EC1400420	63	831	99.85
21	N.Kondal Reddy	EC1470572	63	831	99.85
22	V. Anil Kumar	EC6860302	73	815	99.83
23	Bojja Sandeep Kumar	EC1590626	76	811	99.82
24	Ch Srikanth Raj	EC1440189	79	807	99.81
25	Hintendra sharma	EC8190306	83	803	99.81
26	Shreyan Parakh	EC6660519	85	795	99.8
27	M. Nagendra Kumar	EC7190009	90	791	99.78
28	MonikaG.K	EC1530164	90	791	99.78
29	Sunil Kumar. V	EC1580438	96	787	99.76
30	Jithin R	EC1470384	96	787	99.76

ANALOG CIRCUITS

CONTENTS

S.No	Chapters	Page No:
1.	Diode Circuits Objective Questions	01 – 18 9 & 10, 14 – 18
2.	BJT and FET Biasing Objective Questions	19 – 42 27 – 34, 40 – 42
3.	Small Signal Modeling and Analysis Objective Questions	43 – 55 52 – 55
4.	Frequency Response Objective Questions	56 – 66 64 – 66
5.	Operational Amplifier and Applications Objective Questions	67 – 89 72 – 81, 86 – 89
6.	Feedback Amplifiers and Oscillators Objective Questions	90 – 107 96 – 107
7.	Power Amplifiers Objective Questions	108 – 115 113 – 115
8.	Function Generator and 555 timer Objective Questions	116 – 120 119 & 120
9.	Objective Questions Revision and Practice Set	121 - 140

For

GATE, DRDO & IES

Managing Director
Prof. Y.V. Gopala Krishna Murthy

GATE SYLLABUS

ANALOG CIRCUITS (ECE)

Small Signal Equivalent circuits of diodes, BJTs, MOSFETs and analog CMOS. Simple diode circuits, clipping, clamping, rectifier. Biasing and bias stability of transistor and FET amplifiers. Amplifiers: single-and multi-stage, differential and operational, feedback, and power. Frequency response of amplifiers. Simple op-amp circuits. Filters. Sinusoidal oscillators; criterion for oscillation; single-transistor and op-amp configurations. Function generators and wave-shaping circuits, 555 Timers. Power supplies.

ANALOG CIRCUITS (EEE)

Characteristic of diodes, BJT, FET, SCR; amplifiers – biasing, equivalent circuit and frequency response; oscillators and feedback amplifiers; operational amplifiers - Characteristics and applications; simple active filters; VCO's timers.

Chapter: 1

Diode circuits

1.1: Wave Shaping Circuits

Wave shaping circuits are of two types

- a) linear wave shaping circuits
- b) non linear wave shaping circuits


a. Linear Wave shaping circuits

The process by which the wave form of a non sinusoidal signal is altered by passing it through the linear network is called the linear wave shaping

High Pass Circuit

This circuit is called the high pass filter because it passes the high frequency components and attenuates the low frequency components.

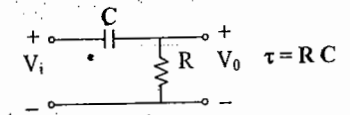For low frequency, the reactance of the capacitance is large $X_C = \frac{1}{2\pi fC}$




(a) Sinusoidal input:

$$\frac{V_o}{V_i} = \frac{R}{R + 1/j\omega C}$$

$$= \frac{1}{1 - j \frac{1}{\omega RC}}$$

$$\frac{V_o}{V_i} = \frac{1}{\sqrt{1 - j(f_1/f)}} \quad \text{Where } f_1 = 1/2\pi RC$$


$$\left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{1 + (f_1/f)^2}}, \quad \angle V_o / V_i = -\tan^{-1}(-f_1/f) = \tan^{-1}(f_1/f)$$

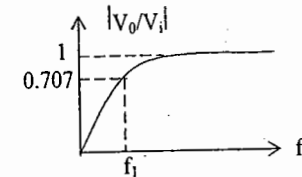

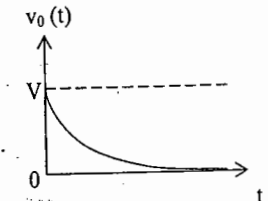(b) Step input: $v_i(t) = v_c(t) + v_0(t)$, $v_i(t) = Vu(t)$

$$= 1/C \int i dt + v_0(t)$$

$$v_0(t) = iR, 1/RC \int v_0(t) dt + v_0(t) = Vu(t)$$



It is a single time constant circuit and a first order equation is obtained. The general solution of any single time constant circuit can be written as

$$v_0(t) = V_f + (V_i - V_f) e^{-t/\tau}, \text{ here } V_f = 0, V_i = V, v_0(t) = V e^{-t/\tau}$$


(c) Pulse input: $v_i(t) = V[u(t) - u(t - \tau_p)]$

$$1) v_0 = V e^{-t/\tau}, V_p = V e^{-\tau_p/\tau}$$

$$2) v_0 = V_2 e^{-(t-\tau_p)/\tau}, V_2 = V_p - V$$

τ large \Rightarrow slow response and

τ small \Rightarrow fast response

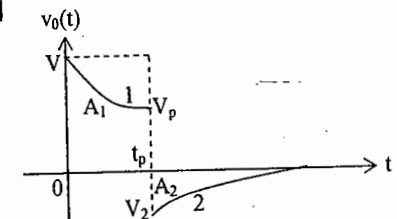

For a low time constant the peak-to-peak amplitude will be double. The process of converting pulses into spikes by means of a low time constant is called peaking. In high pass RC circuit, the average level of the output is always zero. The area above the zero axis should be equal to the area below the zero axis, $A_1 = A_2$

(d) Square wave input

For a non-symmetrical square wave $T_1 \neq T_2$, $T_1 + T_2 = T = 1/f$. The two extreme cases are case 1: $\tau \gg T_1, \tau \gg T_2$. The I/P and O/P are shown below.

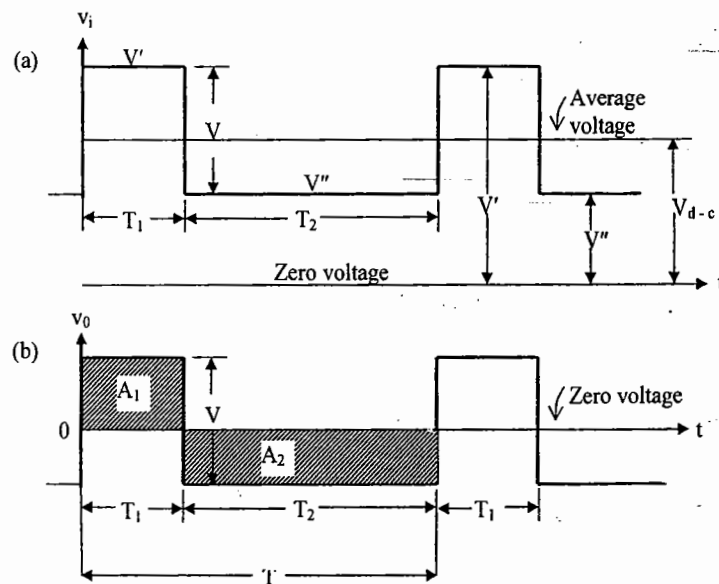


Fig: (a) Square wave input ;(b) Output voltage if the time constant is very large(compared with T).The d-c component V_{d-c} of the output is always zero. Area A_1 equals area A_2 .

Case 2: $\tau \ll T_1, \tau \ll T_2$. The response is shown below:

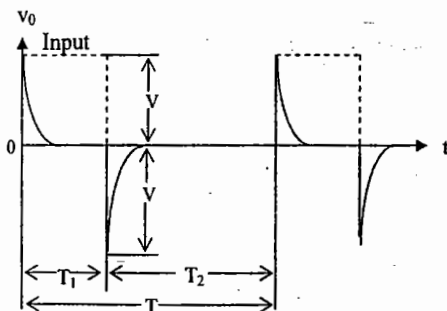


Fig: Peaking of a square wave resulting from a time constant small compared with T .

More generally the response to a square wave must have the appearance shown below:

The four levels V_1, V_1', V_2, V_2' can be determined from

$$V_1' = V_1 e^{-T_1/\tau} \quad V_1' - V_2 = V$$

$$V_2' = V_2 e^{-T_2/\tau} \quad V_1 - V_2' = V$$

For symmetrical square wave:

$$T_1 = T_2 = T/2$$

$V_1 = -V_2, V_1' = V_2'$ and the response is shown below:

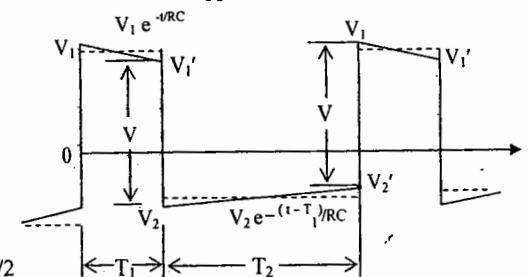


Fig: Linear tilt of a square wave when $RC/T \gg 1$.

Percentage tilt 'P' is defined by

$$P = \frac{V_1 - V_1'}{V/2} \times 100 \approx \frac{T}{2\tau} \times 100\% \\ = \frac{\pi f_1}{f} \times 100\%$$

$$\text{Where } f_1 = \frac{1}{2\pi\tau} \text{ and } f = 1/T$$

(e) Ramp input:

$v_i(t) = \alpha t u(t)$ and $v_o(t) = \alpha \tau (1 - e^{-t/\tau})$ are shown below,

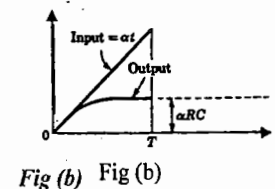
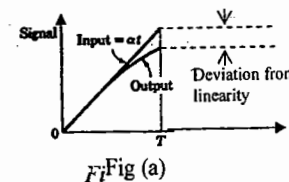
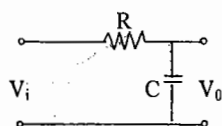


Fig. (a) Response of a high pass RC circuit to a ramp voltage for $RC/T \gg 1$;
(b) Response to a ramp voltage for $RC/T \ll 1$.

For $t \ll \tau$, as a measure of departure from linearity, transmission error, e_t is defined as

$$e_t = \frac{v_i - v_o}{v_i} \quad \text{At } t = T, e_t \approx T/(2\tau) = \pi f_1 T$$


Low Pass Filter:

This circuit allows the low frequency components and attenuates the high frequency components.

(a) Sinusoidal input:

$$\left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{1 + (f/f_2)^2}}$$

$$\angle V_o / V_i = -\tan^{-1} (f / f_2), \text{ where } f_2 = 1/(2\pi RC)$$

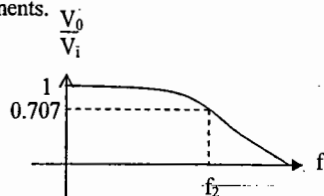(b) Step input:

$$v_{i(t)} = Vu(t)$$

$$v_o(t) = V(1 - e^{-t/\tau})$$

$$t_r = 2.2 \tau = 0.35 / f_2$$

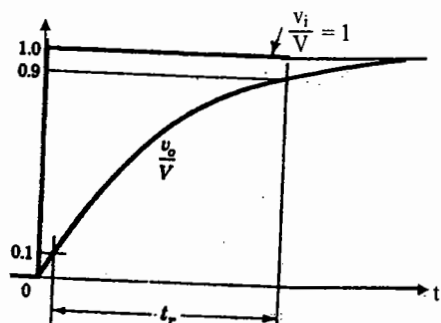


Fig. Step – voltage response of the low – pass RC circuit. The rise time t_r is indicated.

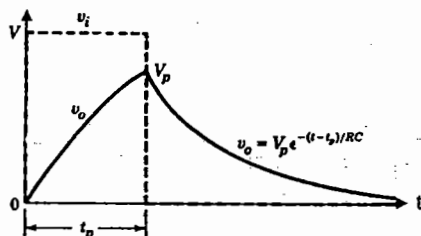
(C) Pulse input:

Fig. Pulse response of the low – pass RC circuits.

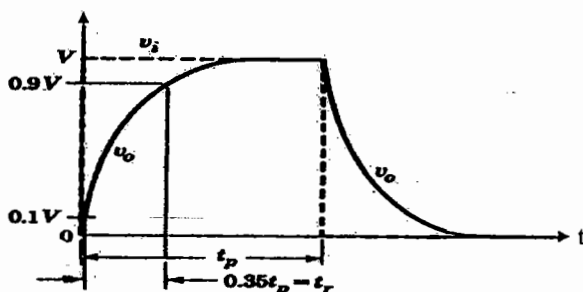


Fig. Pulse response for the case $f_2 = 1/t_p$

(d) Square wave input:

$$v_{01} = V^1 + (V_1 - V^1) e^{-t/\tau}$$

$$v_{02} = V^2 + (V_2 - V^2) e^{-(t-T_1)/\tau}$$

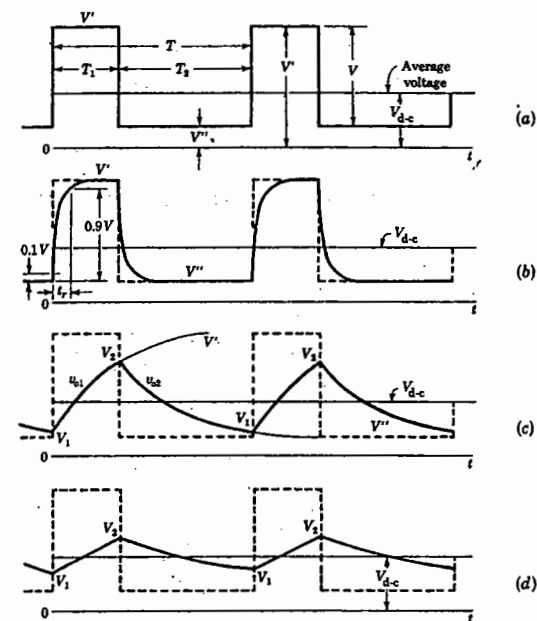


Fig. 2-18 (a) Square-wave input; (b-d) output of the low-pass RC circuit. The time constant is smallest for (b) and largest for (d).

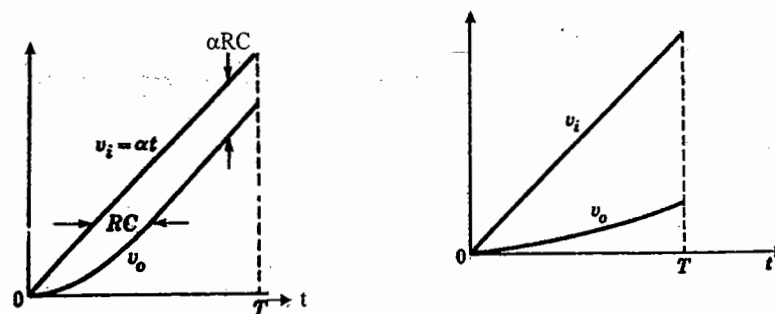
(e) Ramp input:

Fig. Response of a low – pass RC circuit to a ramp voltage

(a) $RC/T \ll 1$; (b) $RC/T \gg 1$.

$$v_o = \alpha t - \alpha \tau (1 - e^{-t/\tau}), \quad e_1 \approx \tau/T = 1/2\pi f_2 T$$

b. Non linear wave shaping circuits

These devices are used for the purpose of switching.


CLIPPERS (Limiters or amplitude selectors or slicers)

There are a variety of diode networks called clippers that have the ability to "clip" off a portion of the input signal without distorting the remaining part of the alternating waveform. Depending on the orientation of the diode, the positive or negative region of the input signal is "clipped" off.

There are two general categories of clippers: series and parallel. The series configuration is defined as one where the diode is in series with the load, while the parallel variety has the diode in a branch parallel to the load.

There is no general procedure for analyzing clippers, but there are a few thoughts to be kept in mind as you work toward a solution.

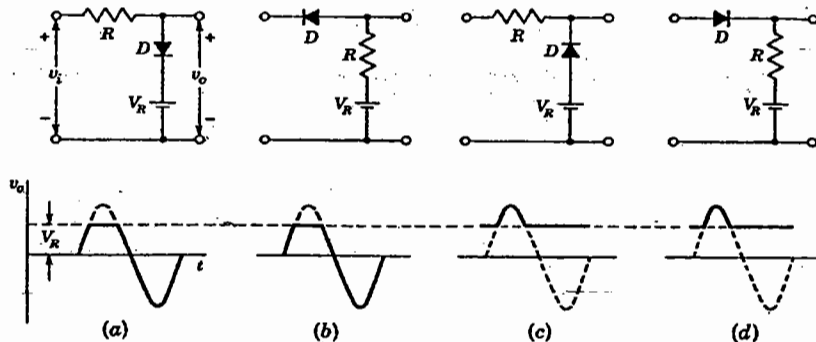
1. Make a mental sketch of the response of the network based on the direction of the diode and the applied voltage levels.
2. Determine the applied voltage (transition voltage) that will cause a change in state for the diode.
3. Be continually aware of the defined terminals and polarity of V_0 .
4. It can be helpful to sketch the input signal above the output and determine the output.



It is reasonable to select $R = \sqrt{R_f R_r}$.

The ratio R_f / R_r may well serve as a figure of merit for diodes used in the present application.

CLIPPING AT TWO INDEPENDENT LEVELS:

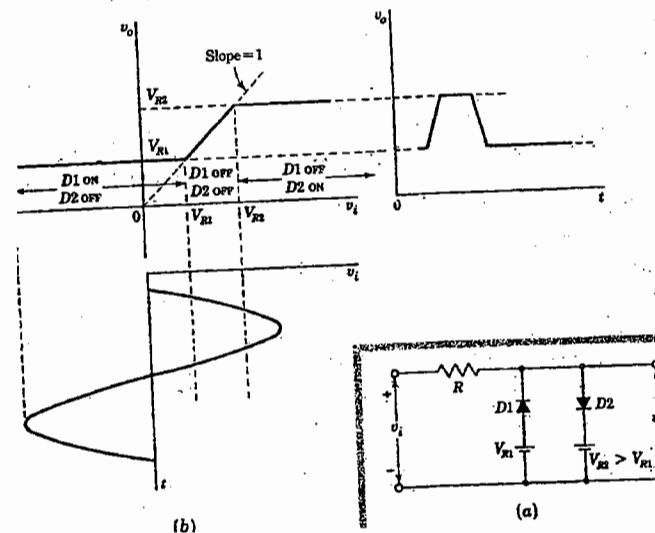

This circuit is referred to as a slicer because the output contains a slice of the input between the two reference levels V_{R1} and V_{R2} . The circuit is used as a means of converting a sinusoidal waveform into a square wave. In this application, to generate a symmetrical square wave, V_{R1} and V_{R2} are adjusted to be numerically equal but of opposite sign. The transfer characteristic passes through the origin under these conditions, and the waveform is clipped symmetrically top and bottom.






CLAMPERS: -

The clamping network is one that will "clamp" a signal to a different dc level. The network must have a capacitor, a diode, and a resistive element, but it can also employ an independent dc supply to introduce an additional shift. The magnitude of R and C must be chosen such that the time constant $\tau = RC$ is large enough to ensure that the voltage across the capacitors does not discharge significantly during the interval, the diode is non-conducting. The total swing of the output is equal to the total swing of the input signal. This fact is an excellent checking tool for the result obtained.

In general, the following steps may be helpful when analyzing clamping networks.


1. Start the analysis of clamping networks by considering that part of the input signal that will forward bias the diode.
2. During the period that the diode is in the "on" state, assume that the capacitor will charge up instantaneously to a voltage level determined by the network.
3. Assume that during the period when the diode is in the "off" state the capacitor will hold on to its established voltage levels.
4. Throughout the analysis maintain a continual awareness of the location and reference polarity for V_0 to ensure that the proper levels for V_0 are obtained.
5. Keep in mind the general rule that the total swing of the output must match the total swing of the input signal.

Clamping Networks

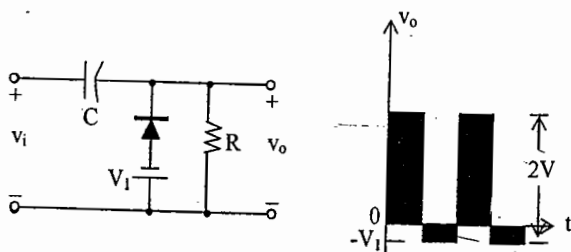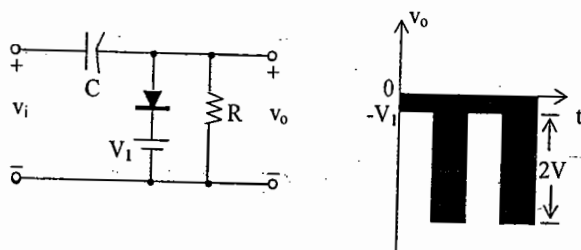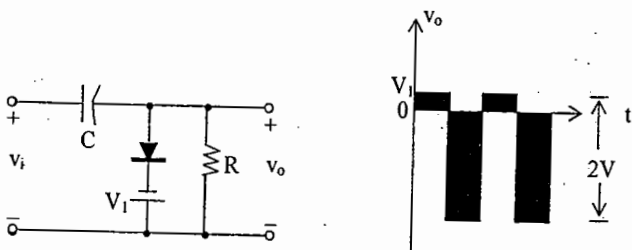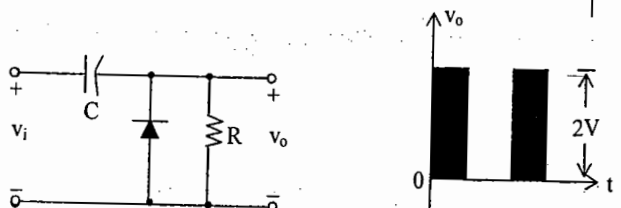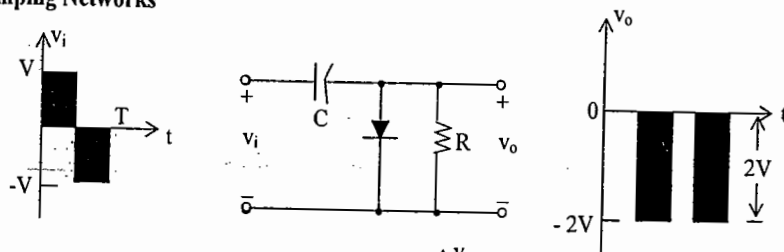


OBJECTIVE QUESTIONS: SET - A

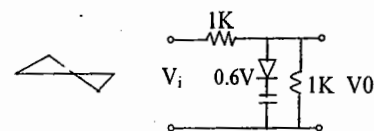1. In figure the input V_i is a 100 Hz triangular wave having a peak amplitude of 2 Volts and an average value of zero volt. Given that the diode is ideal, the average value of the output V_o is



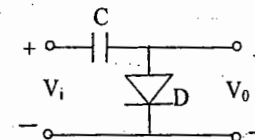2. The circuit shown in acts as
a) rectifier b) clamper
c) clipper d) comparator



3. The output waveform from an amplifier under pulse test has a rise time of $1\mu s$. The upper 3dB frequency of the amplifier is


- a) 250 KHz b) 350 KHz c) 175 KHz d) none

4. An amplifier with a lower cut off frequency of 10 Hz is to be employed for amplification of square waves for the tilt on the output waveform not to exceed 2%. The lowest input frequency that can be amplified is

- a) 1.75 MHz b) 9.5 Hz c) 1.57 KHz d) 59.3 Hz


5. The circuit shown is to have an output voltage of 9V and an output current of approximately 1mA. If the input voltage is $\pm 10V$, the value of R_1 and the diode forward current, respectively are

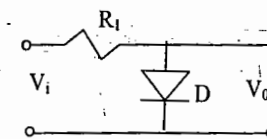- a) 1 K Ω , 6 mA
b) 10 K Ω , 3 mA
c) 1 K Ω , 9.3 mA
d) 10 K Ω , 1.5 mA




6. The average value of the output of the circuit for the input $V_i(t) = 10 \sin \omega t$, is

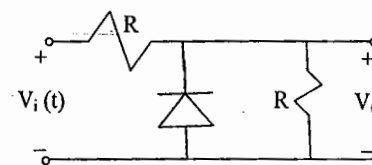- a) $10/\pi$
b) $-10/\pi$
c) $-5/\pi$
d) $5/\pi$



7 If input $V_i(t) = V_m \sin \omega t$, the output expression for the circuit shown is

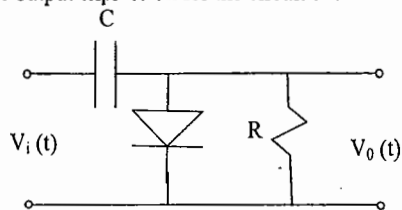- a) $-V_m + V_m \sin \omega t$
 b) $V_m - V_m \sin \omega t$
 c) $-2V_m \sin \omega t$
 d) $2 V_m \sin \omega t$



8. In a clamping circuit the value of R across the diode is

- a) The geometric mean of the forward and reverse resistance of that diode
 b) The arithmetic mean of the forward and reverse resistance of that diode
 c) The Harmonic mean of the forward and reverse resistance of that diode
 d) The product of the forward and reverse resistance of that diode

9. In a clamping circuit the forward and reverse resistance of the diode used, Respectively, are 100Ω and $120 K\Omega$. The value of R across the diode is


- a) $60.05 K\Omega$ b) $3.464 K\Omega$ c) $12 M\Omega$ d) $100 K\Omega$

KEY: (1) 0 (2) b (3) b (4) c (5) c (6) d (7) a (8) a (9) b

SET - B

01. The circuit shown in the figure is best described as

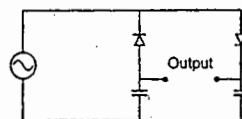
- (A) bridge rectifier (B) ring modulator
 (C) frequency discriminator (D) voltage doubler



02. In the following limiter circuit, an input voltage $V_i = 101 \sin 100 \pi t$ is applied.


Assume that the diode drop is $0.7 V$ when it is forward biased. The zener breakdown voltage is $6.8 V$. The maximum and minimum values of the output voltage respectively are

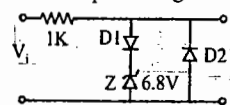- (A) $6.1 V, -0.7 V$ (B) $0.7 V, -7.5 V$
 (C) $7.5 V, -0.7 V$ (D) $7.5 V, -7.5 V$




03. Assuming that the diodes are ideal in figure, the current in diode D_1 is

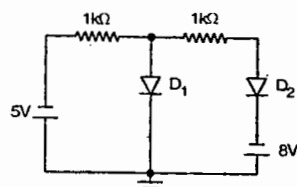- (A) $8 mA$ (B) $5 mA$
 (C) $0 mA$ (D) $-3 mA$



04. The states of the three ideal diodes of the circuit shown in figure are

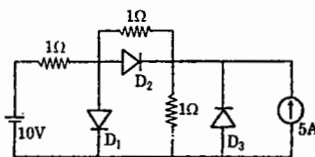- (A) D_1 ON, D_2 OFF, D_3 OFF (B) D_1 OFF, D_2 ON, D_3 OFF
 (C) D_1 ON, D_2 OFF, D_3 ON (D) D_1 OFF, D_2 ON, D_3 ON




KEY: (1) D (2) C (3) C (4) A

1.2 RECTIFIERS AND POWER SUPPLIES:


In a power supply, basically, starting with an AC voltage, a steady DC voltage is obtained by rectifying the AC voltage, then altering to a DC - level by filtering and finally regulating to obtain a desired fixed DC voltage.

Block diagram of a typical power supply:

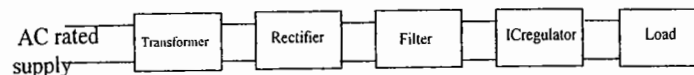


The AC voltage is connected to a transformer which steps that AC voltage down to the level for the desired DC output. A diode rectifier then provides a full-wave rectified voltage that is initially filtered by a simple capacitor filter to produce a DC voltage. This resulting DC voltage usually has some ripple or AC voltage variation. A regulator circuit can use this DC input to provide DC voltage that not only has much less ripple voltage but also remains almost the same DC value even if the input DC voltage varies some what, or the load connected to the output dc voltage changes. This voltage regulation is usually obtained by using one of a number of popular voltage regulator IC units.


Half wave rectifier:

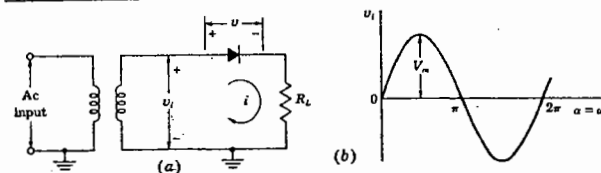




$$v_i(t) = V_m \sin(\omega t)$$

Full wave rectifier: (CT transformer)

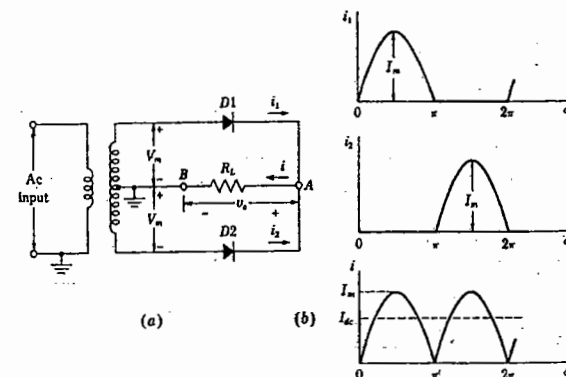

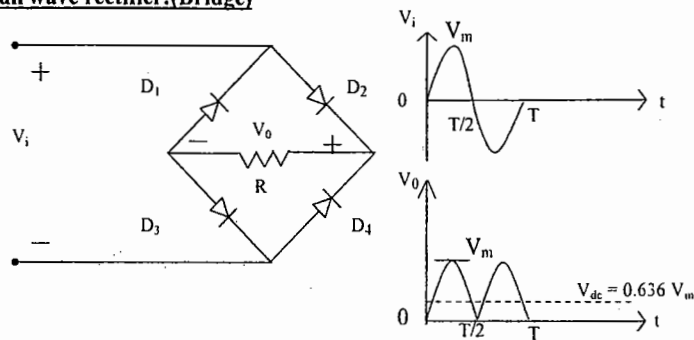Full wave rectifier:(Bridge)

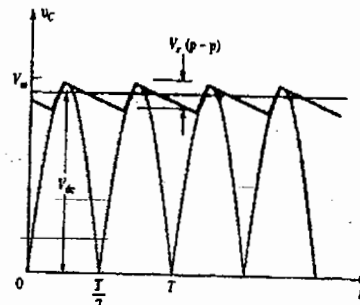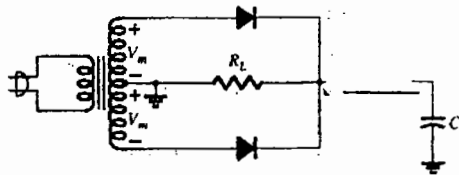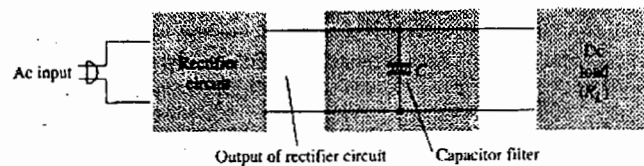
The output resulting from a rectifier is a pulsating DC voltage and not yet suitable as a battery replacement. A filter circuit is necessary to provide a steadier DC voltage. The filtered output has a DC value and some AC variation (ripple). A very popular filter circuit is the **Capacitor filter circuit**:



$$V_{rms} = I_{dc} / (4\sqrt{3} f C)$$

$$r = V_{rms} / V_{dc} = 1 / (4\sqrt{3} f C R_L)$$

The ripple can be further reduced by using an additional RC section as shown below:

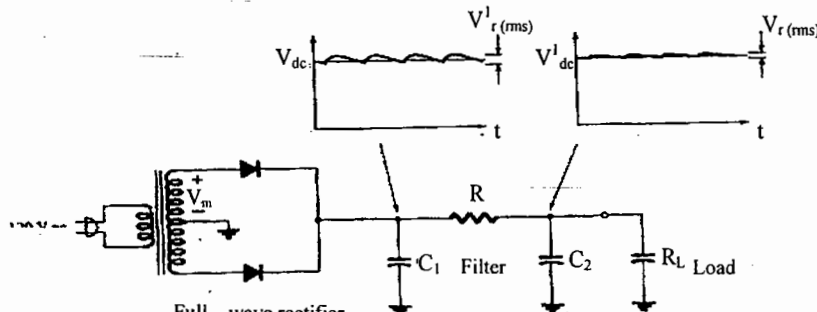Filter capacitor with additional RC filter section:

PARAMETER	HALF-WAVE	FULL-WAVE	BRIDGE
Ripple frequency(f_r)	f_s	$2 f_s$	$2 f_s$
P I V	V_m	$2 V_m$	V_m
I_m	$V_m / (R_f + R_L)$	$V_m / (R_f + R_L)$	$V_m / (2R_f + R_L)$
Average current(I_{dc})	I_m / π	$2 I_m / \pi$	$2 I_m / \pi$
R.M.S value(I_{rms})	$I_m / 2$	$I_m / \sqrt{2}$	$I_m / \sqrt{2}$
D.C voltage(V_{dc})	$V_m / \pi - I_{dc} R_f$	$2 V_m / \pi - I_{dc} R_f$	$2 V_m / \pi - 2 I_{dc} R_f$
Form factor (F)	1.57	1.11	1.11
Ripple factor(r)	1.21	0.482	0.482
P_{dc}	$I_{dc}^2 R_L$	$I_{dc}^2 R_L$	$I_{dc}^2 R_L$
P_i	$I_{rms}^2 (R_f + R_L)$	$I_{rms}^2 (R_f + R_L)$	$I_{rms}^2 (2R_f + R_L)$
Efficiency(η_r)	$\frac{40.5}{1 + (R_f / R_L)} \%$	$\frac{81.0}{1 + (R_f / R_L)} \%$	$\frac{81.0}{1 + (2R_f / R_L)} \%$
Regulation	$R_f / R_L \times 100 \%$	$R_f / R_L \times 100 \%$	

f_s = a.c. input supply frequency, P I V (Peak Inverse Voltage): The maximum voltage to

which the diode is subjected in a rectifier circuit

$$I_{dc} = \frac{1}{2\pi} \int_0^{2\pi} i d\alpha, I_{rms} = \left[\frac{1}{2\pi} \int_0^{2\pi} i^2 d\alpha \right]^{0.5}, V_{dc} = I_{dc} R_L, \text{ Form factor, } F = I_{rms} / I_{dc}$$

$$I'_{rms} = \text{R M S value of the ac components of current} = (I_{rms}^2 - I_{dc}^2)^{0.5}$$

$$\text{Ripple factor, } r = I'_{rms} / I_{dc} = V'_{rms} / V_{dc} = \sqrt{F^2 - 1}$$

$$\eta_r = \text{Efficiency of Rectification} = P_{dc} / P_i, \text{ Regulation} = \frac{(V_{NL} - V_{FL})}{V_{FL}} \times 100 \%$$

OBJECTIVES SET - A

- In a series regulated power supply circuit, the voltage gain A_v of the 'pass' transistor satisfies the condition:
 - $A_v \rightarrow \infty$
 - $1 \ll A_v < \infty$
 - $A_v \approx 1$
 - $A_v \ll 1$
- In rectifier circuits, the values of V_{dc} , V_{rms} , PIV rating of diode depends on the secondary voltage which is ultimately depends on _____.
 - primary voltage
 - turns ratio
 - both (a) & (b)
 - none of the above
- To get high regulated dc voltage which is greater than the rated voltage of a zener diode, zeners can be connected in _____.
 - series
 - parallel
 - none of the above
- For a given rectifier, calculate the value of ripple voltage if $V_{dc} = 10V$ ripple factor is 2%
 - 0.2v
 - 0.3V
 - 0.4v
 - none
- A 10:1 transformer is use in half wave rectifier find no load voltage what is the PIV rating of diode used
 - 23
 - $23\sqrt{2}$
 - $23\sqrt{5}$
 - none
- If the ripple voltage in full wave rectifier is 25v at a load current of 60mA. What would be the value at a load current of 120mA.
 - 100 V
 - 25V
 - 50V
 - none
- In a half wave rectifier, the load current flows for
 - the complete cycle of the input signal
 - only for positive half cycle of input signal
 - less than half cycle of input signal
 - more than half cycle but less than the complete cycle of input signal
- In a half wave rectification if the input frequency is 50Hz, then the output has a frequency of
 - 12.5Hz
 - 25Hz
 - 10Hz
 - 50Hz
- The disadvantage of half wave rectifier has a.c component _____ the d.c component
 - components are expensive
 - diodes must have a high power rating
 - output is difficult to filter
 - none
- The out put of a half wave rectifier has a a.c component _____ the d.c component.
 - equal to
 - more than
 - less than
 - none


- If the a.c input to a Half wave rectifier has an r.m.s value of $400/\sqrt{2}$ volts, then the diode PIV rating, is
 - 400V
 - $400/\sqrt{2}$
 - $400 \times \sqrt{2}$
 - 400×3
- A full wave rectifier is _____ as effective as a half wave rectifier.
 - twice
 - thrice
 - two and half times
 - four times
- In a full wave rectifier, the current in each of the diode flows for
 - the complete cycle of input signal
 - half cycle of input signal
 - for zero time
 - more than half cycle of input signal
- In a full wave rectifier, if the input signal frequency is 50Hz, then output has a frequency of
 - 100Hz
 - 50Hz
 - 25Hz
 - 200Hz
- The bridge rectifier is preferable to an ordinary two – diode full wave rectifier because
 - it uses four diodes
 - transformer has center – tap
 - needs much smaller transformer for the same output
 - it has higher safety factor
- In full wave rectification, transformer is _____
 - essential
 - center tapped
 - both (a) & (b)
 - none
- The a.c. component in the output of a full wave rectifier is _____ the d.c component
 - equal to
 - more than
 - less than
 - none
- The PIV of each diode in a bridge circuit is _____ that of equivalent center - tap circuit
 - equal to
 - half
 - greater than
 - none
- The primary function of a center – tapped transformer in a power supply is to _____
 - step up the voltage
 - step down the voltage
 - causes the diodes conduct alternatively
 - none
- For the same secondary voltage, the output voltage from a center – tap circuit is _____ than that of bridge circuit
 - twice
 - thrice
 - four times
 - one half
- If PIV rating of a diode is exceeded, the diode _____
 - stops conduction
 - is destroyed
 - conducts heavily in the forward direction
 - none
- The rectifier which of power supply is a measure of
 - half wave rectifier
 - full wave rectifier
 - voltage doubles circuit
 - none

23. The ripple factor of power supply is a measure of
 a) its filter efficiency b) diode rating
 c) its voltage regulation d) purity of power output
24. In a half wave rectifier, the peak value of the a.c voltage across the secondary of the transformer is $20\sqrt{2}$ if no filter circuit is used the max. d.c voltage across the load will be
 a) 28.28V b) 25V c) 14.14V d) 9V
25. In a full wave rectifier V_m is the peak voltage between the center tap and one of the secondary the max voltage across the reverse biased diode is _____
 a) V_m b) $\frac{1}{2} V_m$ c) $2V_m$ d) $4V_m$
26. The most widely used rectifier circuit is
 a) HWR b) center - tap circuit c) bridge circuit d) none
27. A crystal diode can be used as a rectifier because it offers
 a) low resistance in both directions
 b) high resistance in one direction and low resistance in the other direction
 c) high resistance in both direction
 d) none
28. A center tap circuit utilizes _____ secondary voltage for full wave rectification
 a) full b) only half of c) one fourth of d) none
29. The bridge rectifier provides 50mA current at 150V. the transformer voltage specification is
 a) 220V: 167V b) 120 V: 150V c) 220V: 236V d) 120V: 110V
30. The bridge rectifier provides 50 mA current at 150V. the average current and PIV of each diode, respectively are
 a) 79mA, 167V b) 25mA, 236V c) 79mA, 167V d) 25mA, 120V
31. If the ripple factor of the output wave of a rectifier is low, it means that
 a) output voltage will have less ripple b) output voltage will be low
 c) filter circuits may not be required d) none

Key : (01).C (02).C (03).B (04).A (05).B (06).C (07).B (08).D
 (09).C (10).B (11).A (12).A (13).B (14).A (15).C (16).C (17).C
 (18).B (19).B (20).D (21).B (22).B (23).D (24).D (25).C (26).C
 (27).B (28).B (29).A (30).B (31).A


SET - B

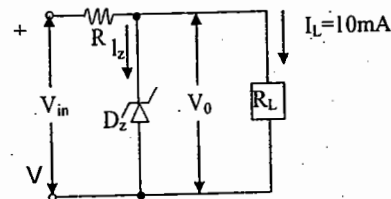01. A dc power supply has a no-load voltage of 30 V, and a full-load voltage of 25 V at a full-load current of 1 A. Its output resistance and load regulation, respectively, are
 (A) 5Ω and 20% (B) 25Ω and 20%
 (C) 5Ω and 16.7% (D) 25Ω and 16.7%
02. A zener diode regulator in the figure is to be designed to meet the specifications: $I_L = 10\text{ mA}$, $V_0 = 10\text{ V}$ and V_{in} varies from 30 V to 50V. The zener diode has $V_z = 10\text{ V}$ and I_{ZK} (knee current) = 1 mA. For satisfactory operation



- (A) $R \leq 1800\Omega$
 (B) $2000\Omega \leq R \leq 2200\Omega$
 (C) $3700\Omega \leq R \leq 4000\Omega$
 (D) $R > 4000\Omega$

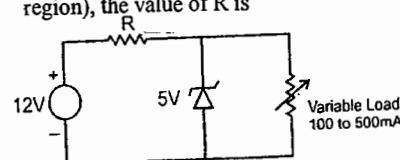03. In the voltage regulator shown in the figure, the load current can vary from 100 mA. Assuming that the Zener diode is ideal (i.e., the Zener knee current is negligibly small and Zener resistance is zero in the breakdown region), the value of R is




- (A) 7Ω (B) 70Ω
 (C) $70/3\Omega$ (D) 14Ω

04. In a full-wave rectifier using two ideal diodes, V_{dc} and V_m are the dc and peak values of the voltage respectively across a resistive load. If PIV is the peak inverse voltage of the diode, then the appropriate relationships for this rectifier are


- (A) $V_{dc} = \frac{V_m}{\pi}$, $PIV = 2V_m$
 (B) $V_{dc} = 2\frac{V_m}{\pi}$, $PIV = 2V_m$
 (C) $V_{dc} = 2\frac{V_m}{\pi}$, $PIV = V_m$
 (D) $V_{dc} = \frac{V_m}{\pi}$, $PIV = V_m$

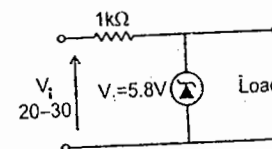05. The zener diode in the regulator circuit shown in the figure has a zener voltage of 5.8 volts and a zener knee current of 0.5 mA. The maximum load current drawn from this circuit ensuring proper functioning over the input voltage range between 20 and 30 volts, is




- (A) 23.7 mA (B) 14.2 mA
 (C) 13.7 mA (D) 24.2 mA

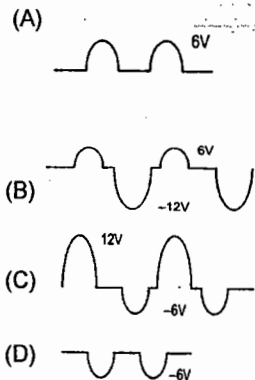
06. For the circuit shown below, assume that the zener diode is ideal with a breakdown voltage of 6 volts. The waveform observed across R is



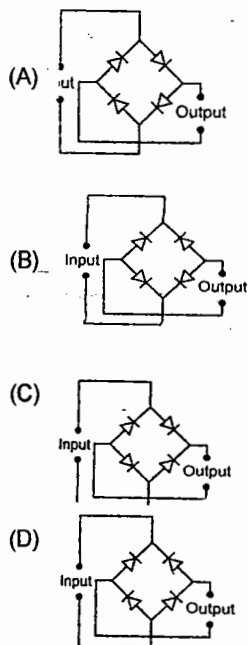07. The correct full rectifier circuit is



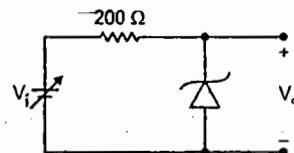08. For the zener diode shown in the figure, the zener voltage at knee is 7 V, the knee current is negligible and the zener dynamic resistance is $10\ \Omega$. If the input voltage (V_i) range is from 10 to 16 V, the output voltage (V_o) ranges from



- (A) 7.00 to 7.29 V
(B) 7.14 to 7.29 V
(C) 7.14 to 7.43 V
(D) 7.29 to 7.43 V

KEY :

- (1) B (2) A (3) D
(4) B (5) A (6) B
(7) C (8) C

Chapter: 2

BJT & FET BIASING

DC BIASING-BJT's

The analysis or design of a transistor amplifier requires knowledge of both the dc and ac response of the system. Too often it is assumed that the transistor is a magical device that can raise the level of the applied ac input without the assistance of an external energy source. In actuality, the improved output ac power level is the result of a transfer of energy from the applied dc supplies. The analysis or design of any electronic amplifier, therefore, has two components; the dc portion and the ac portion.


- Depending on the biasing of the junction there are four modes in which a transistor can operate.
- | | J_E | J_C | |
|------|-------|-------|---------------------|
| i) | FB | FB | --- Saturation mode |
| ii) | FB | RB | --- Active mode |
| iii) | RB | FB | --- Inverted mode |
| iv) | RB | RB | --- Cut off mode. |
- A Transistor can be operated as a switch when operated in saturation and cut off modes.
 - A Transistor can be used as an amplifier in active mode.
 - The transistor dissipates maximum power when it is operated in active mode.
 - Power dissipation in the transistor is given by $P_D = I_C V_{CE}$
 - Dissipation in the transistor is minimum in saturation and cut off modes.
 - In active mode the collector current depends on base current and is independent of collector emitter voltage.
 - Inverted mode is not used since the current gain is very low

For the BJT to be biased in its linear or active operating region the following must be true:

- The base - emitter junction must be forward-biased with a resulting forward bias voltage of about 0.6 to 0.7V.
- The base - collector junction must be reverse-biased, with the reverse-bias voltage being any value within the maximum limits of the device.

OPERATING POINT →

The term biasing appearing in the title of this chapter is an all inclusive term for the application of dc voltages to establish a fixed level of current and voltage. For transistor amplifiers the resulting dc current and voltage establish an operating point on the characteristics that define the region that will be employed for amplification of the applied signal. Since the operating point is a fixed point on the characteristics it is also called the quiescent point (abbreviated Q- point). By definition, quiescent means quiet, still, inactive. The following figure shows a general output device characteristics. The biasing circuit can be designed to set the device operation at Q (V_C, I_C) within the active region. The maximum ratings are indicated on the characteristics by a horizontal line for the maximum collector current $I_{C\max}$ and a vertical line at the maximum collector-to-emitter voltage $V_{CE\max}$. The maximum power constraint is defined by the curve $P_{C\max}$.

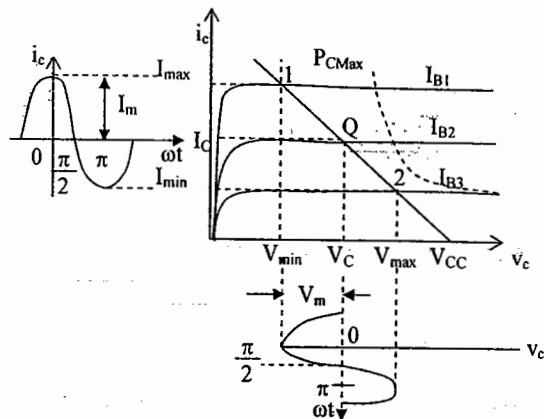

BIAS STABILIZATION

Temperature causes the device parameters such as the transistor current gain (β_{ac}) and the transistor leakage current (I_{CEO}) to change. Higher temperatures result in increased leakage currents in the device, thereby changing the operating condition set by the biasing network. The result is that the network design must also provide a degree of temperature stability so that temperature changes result in minimum changes in the operating point. This maintenance of the operating point can be specified by a stability factor, S , which indicates the degree of change in operating point due to temperature variation.

Thus the stability of a system is a measure of the sensitivity of a network to variations in its parameters. The collector current I_C is sensitive to each of the following parameters.

β : increases with increase in temperature

V_{BE} : decreases about 7.5 mV per degree Celsius ($^{\circ}\text{C}$) increase in temperature.

I_{CO} (reverse saturation current): doubles in value for every 10°C increase in temperature.

Any or all of these factors can cause the bias point to drift from the designed point of operation.

$$I_C = f(I_{CO}, V_{BE}, \beta)$$

$$\Delta I_C = \frac{\partial I_C}{\partial I_{CO}} \Delta I_{CO} + \frac{\partial I_C}{\partial V_{BE}} \Delta V_{BE} + \frac{\partial I_C}{\partial \beta} \Delta \beta$$

$$\Delta I_C = S \Delta I_{CO} + S' \Delta V_{BE} + S'' \Delta \beta$$


$$S, S', S'' \text{ are stability factors where } S = \frac{\partial I_C}{\partial I_{CO}} \bigg|_{V_{BE}, \beta \text{ const}}$$

$$S = \frac{\partial I_C}{\partial V_{BE}} \bigg|_{I_{CO}, \beta \text{ const}}$$

$$S = \frac{\partial I_C}{\partial \beta} \bigg|_{I_{CO}, V_{BE} \text{ const}}$$

FIXED BIAS CIRCUIT \rightarrow

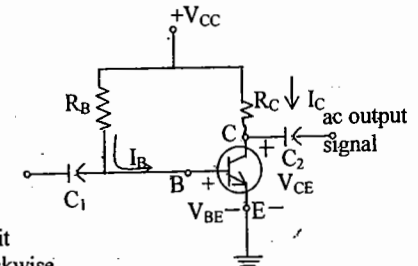The fixed bias circuit provides a relatively straight forward and simple introduction to transistor dc bias analysis.



Base-Emitter Loop: consider the base emitter circuit loop, writing Kirchhoff's voltage equation in the clockwise direction for the loop, we obtain.

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

Since the supply voltage V_{CC} and the base-emitter voltage V_{BE} are constants, the selection of R_B sets the levels of base current for the operating point.

Collector-Emitter Loop: $I_C = \beta I_B$

Since the base current is controlled by the level of R_B and I_C is related to I_B by a constant β the magnitude of I_C is not a function of the resistance R_C . However, the level of R_C will determine the magnitude of V_{CE} . Applying KVL in the clockwise direction around the closed loop

$$V_{CE} + I_C R_C - V_{CC} = 0 \quad \text{and} \quad V_{CE} = V_{CC} - I_C R_C$$

$$\text{But } V_{CE} = V_C - V_E = V_C \quad \text{and} \quad V_{BE} = V_B - V_E = V_B \quad \text{Since } V_E = 0V$$

Transistor saturation: For a transistor operating in the saturation region the current is a maximum value for the particular design. The highest saturation level is defined by the maximum collector current. To know the approximate maximum collector current for a design, simply insert a short-circuit equivalent between collector and emitter of the transistor and calculate the resulting collector current. For the fixed bias, the short circuit has been applied, causing the voltage across R_C to be the applied voltage V_{CC} .

$$I_{C \text{ sat}} = \frac{V_{CC}}{R_C}$$

Here I_B is fixed because the biasing voltage V_{CC} and base resistance R_B are constant. As the temperature increases I_{CO} increases hence I_C increases. As I_C increases temperature increases so again I_{CO} increases. This cumulative process leads to thermal run away because here I_B is constant

$$I_C = \beta I_B + (1 + \beta) I_{CO} \quad \text{Stability factor, } S = \frac{\partial I_C}{\partial I_{CO}}$$

$$\text{Since } I_B \text{ is constant, } \frac{\partial I_B}{\partial I_C} = 0$$

$$\therefore S = \frac{1 + \beta}{1 - \beta \frac{\partial I_B}{\partial I_C}} = 1 + \beta$$

From the above equation we can conclude that for a small change occurring in I_{CO} makes a large change in I_C . So, this circuit gives less stability and not commonly used.

FIXED BIAS CIRCUIT WITH EMITTER RESISTOR →**Base Emitter loop:**

Writing Kirchhoff's voltage law in the clockwise direction

$$+V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$\text{But } I_E = (1 + \beta) I_B$$

$$\therefore V_{CC} - I_B R_B - V_{BE} - (\beta + 1) I_B R_E = 0$$

$$\therefore I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

$$I_C = \beta I_B = \frac{\beta [V_{CC} - V_{BE}]}{R_B + (\beta + 1) R_E}$$

Since $\beta \gg 1$ and V_{BE} is very small,

$$I_C \approx \frac{V_{CC}}{\frac{R_E + R_B}{\beta}}$$

Collector-Emitter Loop:

Writing KVL in the clockwise direction,

$$I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

Substituting $I_E \cong I_C$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Again consider the Base-emitter loop,

$$I_B = \frac{V_{CC} - V_{BE} - I_C R_E}{R_B + R_E}$$

$$\frac{\partial I_B}{\partial I_C} = \frac{-R_E}{R_B + R_E}$$


$$\text{Stability factor } S = \frac{1 + \beta}{1 - \beta \frac{\partial I_B}{\partial I_C}} \quad S = \frac{1 + \beta}{1 + \beta \frac{R_E}{R_E + R_B}}$$

An increase in I_C due to an increase in I_{CO} will cause the voltage $V_E = I_E R_E \cong I_C R_E$ to increase. The result is a drop in the level of I_B . A drop in I_B will have the effect of reducing the level of I_C through transistor action and thereby offset the tendency of I_C to increase due to an increase in temperature. In total, therefore, the configuration is such that there is a reaction to an increase in I_C that will tend to oppose the change in bias conditions.

To decrease the stability factor we have to increase R_E value, but this

- decreases the gain of the amplifier
- increases voltage drop across R_E

The first drawback can be avoided by connecting a bypass capacitor across R_E but the second one cannot be avoided. Hence this circuit is not used.

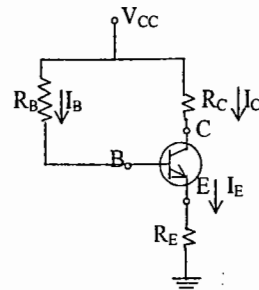**COLLECTOR TO BASE BIASING CIRCUIT (Self Bias)****Base-Emitter loop: Applying KVL**

$$V_{CC} - (I_B + I_C) R_C - I_B R_B - V_{BE} = 0$$

$$V_{CC} - I_B (R_C + R_B) - I_C R_C - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - I_C R_C - V_{BE}}{R_B + R_C}$$

Collector Emitter loop : Applying KVL $V_{CC} - (I_C + I_B) R_C - V_{CE} = 0$


$$\text{Neglecting } I_B, \quad V_{CC} - V_{CE} - I_C R_C = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$


$$\text{Stabilizing factor } S = \frac{1 + \beta}{1 - \beta \frac{\partial I_B}{\partial I_C}} \quad \frac{\partial I_B}{\partial I_C} = \frac{-R_C}{R_B + R_C} \quad S = \frac{1 + \beta}{1 + \beta \frac{R_C}{R_B + R_C}} \cong 1 \text{ for } R_C \gg R_B$$

R_B is the feedback resistor and eliminating the feedback is difficult. So this method is rarely used.


This feedback configuration operates in much the same way as the emitter-bias configuration when it comes to levels of stability. If I_C should increase due to an increase in temperature, the level of V across R_C will increase and the level of I_B will decrease. The result is a stabilizing effect as described for the emitter-bias configuration.

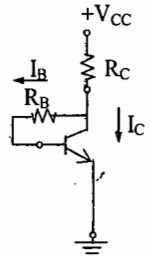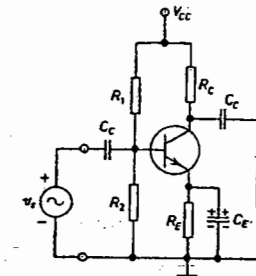**SELF BIAS CIRCUIT →**

This Voltage divider biasing circuit is the most widely used circuit.



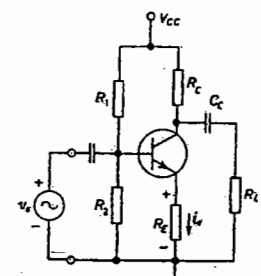Voltage Divider biasing with bypass capacitor




Voltage Divider biasing without bypass capacitor

Applying Thevenin's Theorem at the input side,

$$V_{th} = V_{CC} \frac{R_2}{R_1 + R_2}$$

$$R_B = \frac{R_1 R_2}{R_1 + R_2}$$

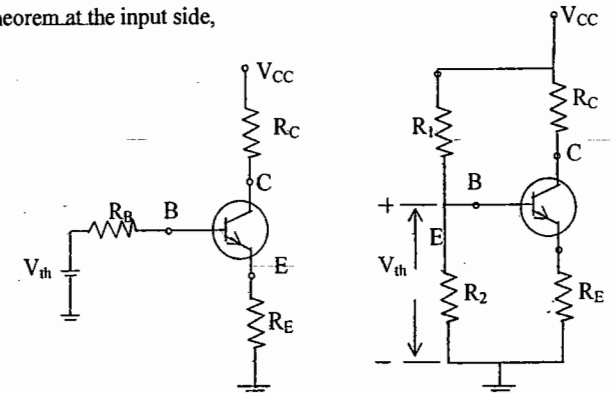

Applying KVL to input,

$$-V_{th} + I_B R_B + V_{BE} + I_E R_E = 0$$

$$V_{th} = I_B R_B + V_{BE} + R_E (I_C + I_B)$$

$$I_B = \frac{V_{th} - V_{BE} - R_E I_C}{R_B + R_E}$$

$$I_C = \beta I_B$$

Applying KVL to output,

$$V_{CC} - I_C R_C - V_{CE} - (I_C + I_B) R_E = 0$$

$$V_{CE} = V_{CC} - I_B R_E - I_C (R_C + R_E)$$


Neglecting V_{BE} , $I_C \cong \frac{\beta V_{th}}{R_B + (1 + \beta) R_E}$ Since $\beta \gg 1$ $I_C = \frac{V_{th}}{\frac{R_B}{\beta} + R_E}$

Stability factor, $S = \frac{1 + \beta}{1 - \beta \frac{\partial I_B}{\partial I_C}}$ $\frac{\partial I_B}{\partial I_C} = \frac{-R_E}{R_B + R_E}$

$$\frac{\partial I_B}{\partial I_C} = \frac{-R_E}{R_B + R_E}$$

$$S = \frac{1 + \beta}{1 + \beta \frac{R_E}{R_B + R_E}} \cong 1 \text{ for } R_B \ll R_E$$

Negative feedback can be eliminated by connecting a by pass capacitor across R_E . The most stable of the configurations is the voltage divider bias network. If the condition $\beta R_E \gg 10 R_2$ is satisfied, the voltage V_B will remain fairly constant for changing levels of I_C . The base to emitter voltage of the configuration is determined by $V_{BE} = V_B - V_E$. If I_C should increase, V_E will increase and for a constant V_B the voltage V_{BE} will drop. A drop in V_{BE} will establish a lower level of I_B which will try to offset the increased level of I_C .

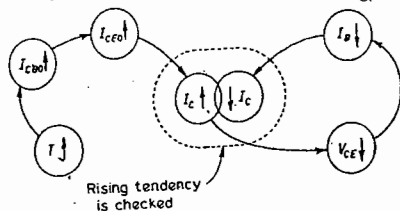


COMPENSATION TECHNIQUES

The compensation technique is used only to compensate the temperature parameters and not to fix the operating point in active region. The operating point is fixed by stabilization technique by using biasing resistors. So, the compensation technique is applicable only after the stabilization. With compensation technique we can compensate temperature parameter exactly.

There are four types of compensation techniques available.

- Diode compensation for V_{BE}
- Diode compensation for I_{CO}
- Thermistor compensation
- Sensistor compensation

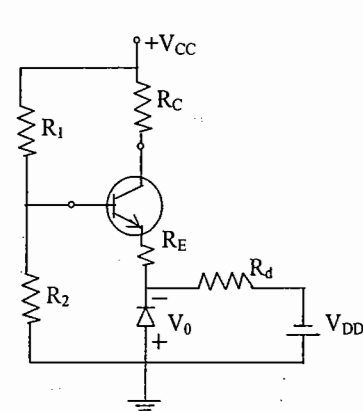DIODE COMPENSATION FOR $V_{BE} \rightarrow$



The variation in V_{BE} can be cancelled by connecting the diode in series with emitter such that the voltage across diode is in opposite direction to V_{BE} . Here the diode and transistor are made with same material to get the same temperature effect in both the devices.

Apply KVL to Thevenin's equivalent circuit,

$$V_{th} - I_B R_{th} - V_{BE} - I_E R_E + V_0 = 0$$

$$\text{Since } V_0 = V_{BE}$$

$$V_{th} - R_{th} I_B - R_E (\beta I_B + I_B) = 0$$

$V_{BE} = V_0$ because any change in V_{BE} due to temperature the same change occurs in V_0 . So, the collector current is independent of V_{BE} .

DIODE COMPENSATION FOR $I_{CO} \rightarrow$

If the diode and transistor are made of same material then the reverse saturation current I_0 of the diode will increase with temperature at the same rate as the transistor reverse saturation current I_{CO} .

$$I_C = \beta I_B + (1 + \beta) I_{CO}$$

$$I_B = I_1 - I_0$$


$$\therefore I_C = \beta (I_1 - I_0) + (1 + \beta) I_{CO}$$

$$\text{since } \beta \gg 1$$

$$I_C = \beta (I_1 - I_0) + \beta I_{CO}$$

$$-I_C = \beta I_1 - \beta (I_0 - I_{CO})$$
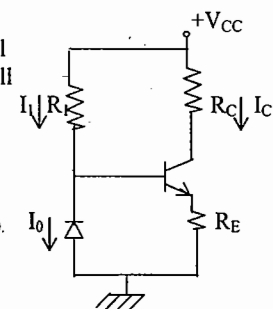
$$I_C = \beta I_1 \quad \text{Since } I_0 = I_{CO}$$




THERMISTOR COMPENSATION →


Thermistor is a temperature sensitive device having a negative temperature coefficient (ie) its resistance decreases with increase in temperature.

So,
 $T \uparrow \rightarrow R_T \downarrow \rightarrow I_T \uparrow \rightarrow I_E R_E \uparrow \rightarrow I_B \downarrow \rightarrow I_C \downarrow$
 \downarrow
 $I_C \uparrow$

Thermistors are used to minimize the increase in I_C due to change in temperature.

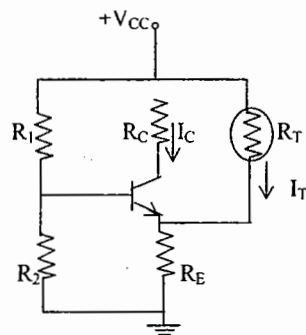
**SENSISTOR COMPENSATION →**

Sensistor is a heavily doped semiconductor device having positive temperature coefficient, (ie) its resistance increases with temperature.

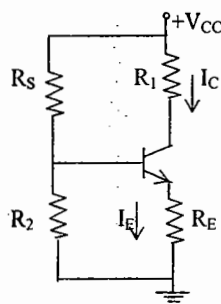**THERMAL STABILITY**

Thermal stability is the condition to avoid the thermal runaway.

The increase in I_C due to increase in temperature gives more power dissipation in the collector junction. Due to the power dissipation in the collector junction again temperature increases. So, I_C again increases. This cumulative process gives more heat at collector junction and spoils the transistor. This process is called Thermal Runway.

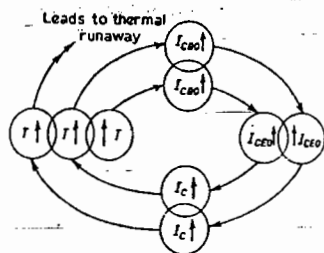**CONDITION FOR THERMAL STABILITY →**

The steady state temperature rise at collector junction is proportional to power dissipation at the junction.

$$(T_j - T_A) \propto P_D$$

where T_j -- junction temperature

T_A -- Ambient temperature

$$T_j - T_A = \theta P_D$$

Where θ thermal resistance $^{\circ}\text{C}/\text{watt}$

To get the change in power dissipation with respect to junction temperature, partially differentiate with respect to T_j

$$1 - 0 = \theta \frac{\partial P_D}{\partial T_j}$$

$$\frac{\partial P_D}{\partial T_j} = \frac{1}{\theta}$$

Condition for thermal stability is the rate at which heat is generated at collector junction should be less than the rate at which heat dissipated.

$$(ie) \quad \frac{\partial P_C}{\partial T_j} < \frac{\partial P_D}{\partial T_j}$$

$$\Rightarrow \quad \frac{\partial P_C}{\partial T_j} < \frac{1}{\theta}$$

This is the condition to avoid thermal runaway

$$\frac{\partial P_C}{\partial T_j} = \left[\frac{\partial P_C}{\partial I_C} \right] \left[\frac{\partial I_C}{\partial I_{C0}} \right] \left[\frac{\partial I_{C0}}{\partial T_j} \right] < \frac{1}{\theta}$$

Stability factor $\rightarrow 7\% \text{ per } ^{\circ}\text{C} = 0.07 I_{C0}$

OBJECTIVE QUESTIONS: SET A.

1. Thermal runaway in a transistor biased in the active region is due to

- heating of the transistor
- changes in β which increases with temperature
- base emitter voltage V_{BE} which decreases with rise in temperature
- change in reverse collector saturation current due to rise in temperature.

2. To obtain a fixed bias in CE configuration, a battery of 2V is used in the base with a series resistor R_B across the base emitter junction; given $\beta = 100$ and $V_{BE} = 0.6$ Volt, to obtain $I_C = 2\text{mA}$, the value of R_B is given by

- 700 ohms
- 7 K ohms
- 70 K ohms
- 130 K ohms


3. In the self biasing scheme or collector - to - base biasing circuit (R_F across collector to base) of a BJT, S_1 tends to unity by

- increasing R_F
- decreasing R_C
- decreasing R_F and increasing R_C
- increasing R_F and decreasing R_C

Note: R_C is collector load resistor.

4. In the circuit shown $V_{CC}=10$, $R_C=2.7\text{ K}$, $R_F=200\text{ K}$, $\beta=99$, $V_{BE}=0.6$. The operating point V_C , I_C are given by

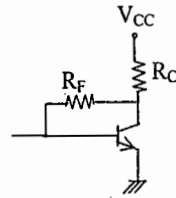- 4.6 V and 1.98 mA
- 4.7 V and 2 mA
- 5.4 V and 1.56 mA
- 4.2 V and 2.1 mA



5. In the potential divider bias (with R_{B1} and R_{B2}) to obtain base current, R_B is the equivalent base resistor and R_E the emitter resistor.

- $R_B \gg R_E$ improves S_I
- $R_B \gg R_E$ improves S_β
- $R_B \ll R_E$ improves both S_I and S_β
- R_B has no effect on the stabilization factors


6. In regard to the operating point of a transistor in the active region, and its stabilisation, following four statements are made:.

- I_{CO} doubles for every 10°C rise in temperature.
- V_{BE} increases with temperature
- Potential divider bias along with R_E stabilizes against variations in I_{CO} but not in β_0
- For good stabilization, $R_B \ll R_E$, where R_B is the equivalent base resistor of the potential divider resistors. Of these, the true statements are

- only 1,2
- only 2,3
- only 3,4
- only 4, 1

7. Circuit shows current mirror biasing for IC's. Given $V_{CC}=10$ volts, $I_{C1}=1\text{ mA}$ and $V_{BE}=0.7$ volt, the value of R is given by

- 10 K Ω
- 9.3 K Ω
- 5 K Ω
- 4.65 K Ω

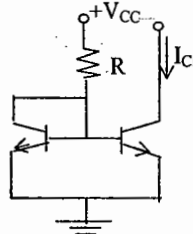

8. In a CE amplifier, the effect of an unbypassed R_E is to increase the input resistance. This happens because


- The system tends towards an ideal CVS
- Both input and output currents flow through R_E
- The fed back quantity is a voltage
- The fed back quantity is a current.

Of the above four statements the true statements are


- only 1,2
- only 3,4
- only 2,3
- only 1,4

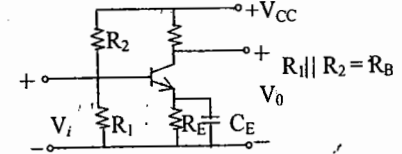9. For good stabilized biasing of the transistor of the CE amplifier shown below, the condition is

- $\frac{R_E}{R_B} \ll 1$
- $\frac{R_E}{R_B} \gg 1$
- $\frac{R_B}{R_E} \ll h_{FE}$
- $\frac{R_B}{R_E} \gg h_{FE}$



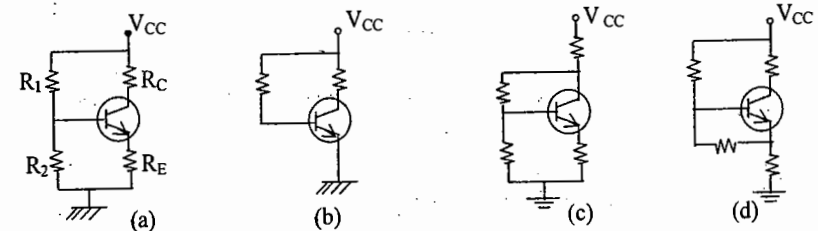10. Of the four biasing circuits shown in figure for a BJT, indicate the one which can have maximum bias stability.



11. The quiescent collector current I_C of a transistor is increased by changing the biasing resistances. As a result g_m will

- not be affected
- decrease
- increase
- increase or decrease depending on bias stability.

12. Pick out the correct statements

- DC load line is same as AC load line
- DC load line is steeper than AC load line
- AC load line is steeper than DC load line
- AC signal swing is restricted in an AC load line


13. The parameters that can be determined from a load line are

- quiescent point only
- quiescent point, Thevenin voltage, Norton current
- quiescent point, no load voltage, short circuit current, voltage drop across load
- in addition to parameters in (c) above, voltage drop across device

For Questions 14 to 17, the figure shows $V-I$ characteristic and load line of a nonlinear device in series with a load resistor

14. With reference to the figure the cut in voltage of the device is

- 0.65
- 0.1
- 0.5
- 0

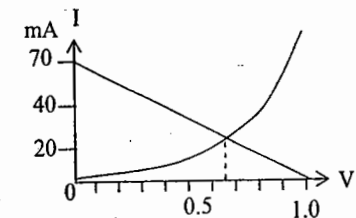

15. With reference to the above figure the quiescent current is

- 70mA,
- 0
- 20 mA
- 23mA


16. With reference to the above figure, the voltage across the non-linear device is

- 1V
- 0.65V
- 0.35V
- 0.5 V

17. With reference to the above figure, the drop across the load resistor is

- a) 0.35 V b) 0.65 V c) 1 V d) 0 V

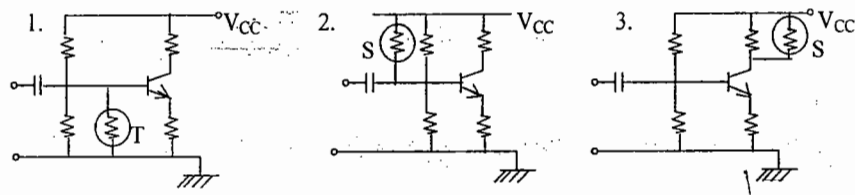18. Which of the following circuits realize self bias with compensation?




T = Thermistor, S = Sensistor

Select the correct answer using the codes given below:

- a) 2 and 3 b) 1 and 2 c) 1 and 3 d) 1, 2 and 3

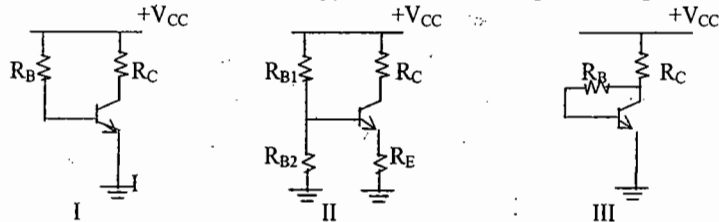
19. Three different circuits for biasing junction transistor amplifiers are given below



The correct decreasing order of preference of these circuits from the point of view of bias stabilisation is

- a) I, II, III b) III, II, I c) II, III, I d) I, III, II

 20. In the following two non-linear transistor biasing circuits, the resistors,



- a) R_A and R_B , both have negative temperature coefficients
 b) R_A and R_B , both have positive temperature coefficients
 c) R_A has negative temperature coefficient and R_B has Positive temperature coefficient
 d) R_A has positive temperature coefficient and R_B has Negative temperature coefficient.

KEY:

1. d 2. c 3. c 4. a 5. c 6. d 7. b 8. c 9. b 10. a 11. c 12. c


13. d 14. c 15. d 16. b 17. a 18. b 19. c 20. d

SET - B

01. In the circuit of the figure, assume that the transistor is in the active region. It has a large β and its base-emitter voltage is 0.7 V. The value of I_C is

(A) indeterminate since R_C is not given


(B) 1 mA (C) 5 mA (D) 10 mA

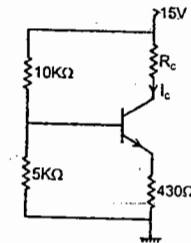

02. In the amplifier circuit shown in the figure, the values of R_1 and R_2 are such that the transistor is operating at $V_{CE} = 3$ V and $I_C = 1.5$ mA when its β is 150. For a transistor with β of 200, the operating point (V_{CE} , I_C) is

(A) (2V, 2mA) (B) (3V, 2mA)


(C) (4V, 2mA) (D) (4V, 1mA)

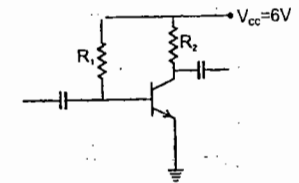

03. Assuming $V_{CEsat} = 0.2$ V and $\beta = 50$, the minimum base current (I_B) required to drive the transistor in the figure to saturation is

(A) 56 μ A (B) 140 μ A

(C) 60 μ A (D) 3 mA

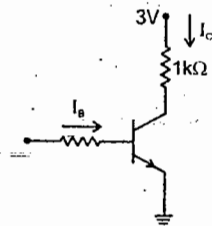


04. For an npn transistor connected as shown in the figure, $V_{BE} = 0.7$ volts.



Given that reverse saturation current of the junction at room temperature 3000 K is 10-13 A, the emitter current

(A) 30mA (B) 39mA

(C) 49mA (D) 20 mA

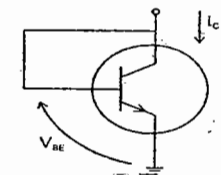

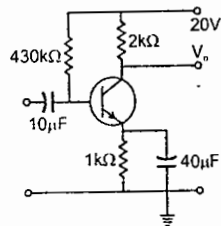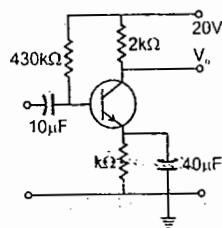
05. The circuit using a HJT with $\beta = 50$ and $V_{BE} = 0.7 \text{ V}$ is shown in the figure. The base current I_B and collector voltage V_C are respectively



- (A) $43 \mu\text{A}$ and 11.4 Volts (B) $40 \mu\text{A}$ and 16 volts
(C) $45 \mu\text{A}$ and 11 Volts (D) $50 \mu\text{A}$ and 10 Volts

06. For the BJT circuit shown, assume that the β of the transistor is very large and $V_{BE} = 0.7 \text{ V}$. The mode of operation of the BJT

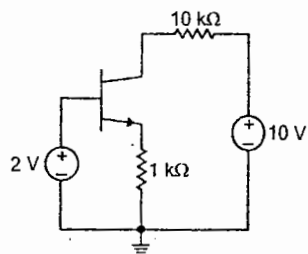- (A) cut - off
(B) saturation
(C) normal active
(D) reverse active




07. Introducing a resistor in the emitter of a common amplifier stabilizes the dc operating point against variations in

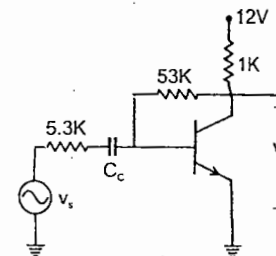- (A) only the temperature
(B) only the β of the transistor
(C) both temperature and β
(D) none of the above

Common data for Questions 08, 09 and 10.

In the transistor amplifier circuit shown in the figure below, the transistor has the following parameters: $\beta_{DC} = 60$, $V_{BE} = 0.7 \text{ V}$, $h_{ie} \rightarrow \infty$, $h_{fe} \rightarrow \infty$. The capacitance C_C can be assumed to be infinite. In the figure above, the ground has been shown. By the symbol ∇



08. Under the DC conditions, the collector - to - emitter voltage drop is

- (A) 4.8 Volts (B) 5.3 Volts (C) 6.0 Volts (D) 6.6 Volts

09. If β_C is increased by 10%, the collector - to - emitter voltage drop

- (A) increases by less than or equal to 10%
(B) decreases by less than or equal to 10%
(C) increases by more than 10%
(D) decreases by more than 10%

10. The small - signal gain of the amplifier V_C/V_S is

- (A) - 10 (B) - 5.3 (C) 5.3 (D) 10

Statement for linked answer Questions 11 & 12.

In the following transistor circuit, $V_{BE} = 0.7\text{ V}$, $r_e = 25\text{ mV}/I_E$, and β and all the capacitances are very large

11. The value of DC current I_E is

- (A) 1 mA (B) 2 mA
(C) 5 mA (D) 10 mA

12. The mid-band voltage gain of the amplifier is approximately

- (A) -180 (B) -120
(C) -90 (D) -60

13. Given figure shows a two-state small signal transistor feedback amplifier. Match the defective component in list - I with its probable effect on the circuit in list - II

List - I




- (A) Capacitor C_1 is open
(B) Capacitor C_3 is open
(C) Capacitor C_4 is open
(D) R_{c2} is shorted

List - II

- P. all dc voltages normal, v_0 increases marginally
Q. collector of TR2 is at V_{CC} , $v_0 = 0$
R. all dc voltages normal, gain of 2nd stage increase v_0 decrease
S. all dc voltages normal, $v_0 = 0$
T. all dc voltages normal, overall gain of the amplifier increases, v_0 increases
U. No change

14. The transconductance g_m of the transistor shown in figure is 10 mS. The value of the input resistance R_{IN} is

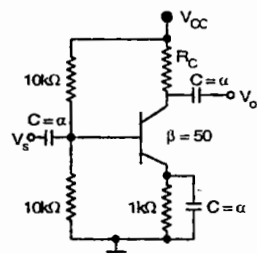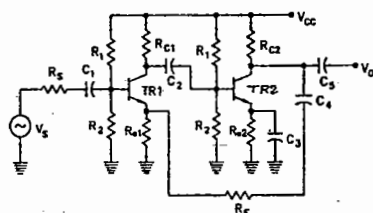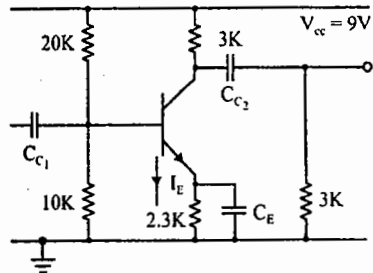- (A) 10.0 k Ω (B) 8.3 k Ω
(C) 5.0 k Ω (D) 2.5 k Ω



KEY: SET - B

- (1) D (2) A (3) A (4) C (5) B (6) B
(7) C (8) C (9) B (10) A (11) A (12) D
(13) a - S, b - R, c - T, D - Q (14) D

FET BIASING

For the field-effect transistor the relationship between input and output quantities is non-linear due to the squared term in Shockley's equation. This non-linear relationship between I_D and V_{GS} can complicate the mathematical approach to the dc analysis of FET configuration. A graphical approach may limit solutions to tenths place accuracy but it is a quicker method for most FET amplifiers.

Another distinct difference between the analysis of BJT and FET transistors is that the input controlling variable for a BJT transistor is a current level, while for the FET a voltage is the controlling variable. In both cases, however, the controlled variable on the output side is a current level that also defines the important voltage levels of the output circuit. The general relationships that can be applied to the dc analysis of all FET amplifiers are

$$\text{and } I_D = I_S \quad I_G \approx 0A$$

For JFETs and depletion-type MOSFETs Shockley's equation is applied to relate the input and output quantities:

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$


For enhancement-type MOSFETs the following equation is applicable:

$$I_D = K (V_{GS} - V_T)^2$$

JFETs and Depletion type MOSFETs:

Fixed Bias Configuration →

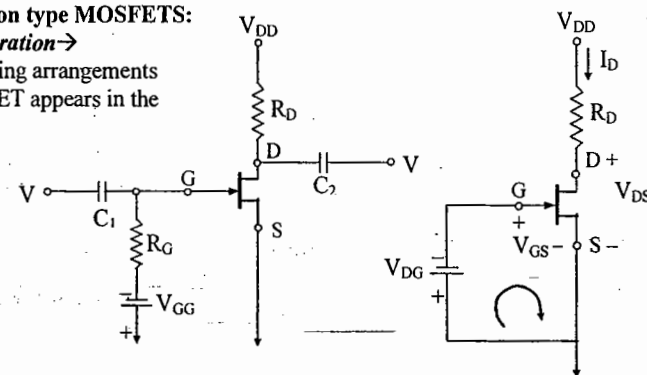The simplest of biasing arrangements for the n-channel JFET appears in the following figures



The configuration includes the ac levels V_i and V_0 and the coupling capacitors (C_1 and C_2). The coupling capacitors are "open circuits" for the dc analysis and low impedances for the ac analysis. The resistor R_G is present to ensure that V_i appears at the input to the JFET amplifier for the ac analysis.

For the dc analysis

$$I_G \approx 0A$$

$$\text{and } V_{RG} = I_G R_G = (0A) R_G = 0V$$

Applying KVL in the clockwise direction of the indicated loop will result in

$$\text{and } -V_{GG} - V_{GS} = 0 \quad V_{GS} = -V_{GG}$$

Since V_{GG} is a fixed dc supply the voltage V_{GS} is fixed in magnitude, resulting in the notation "fixed-bias configuration".

The resulting level of drain current I_D is now controlled by Shockley's equation:

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

The drain-to-source voltage of the output section can be determined by applying Kirchhoff's voltage law as follows:

$$+V_{DS} + I_D R_D - V_{DD} = 0$$

and

$$V_{DS} = V_{DD} - I_D R_D$$

For the configuration of the given figure, $V_S = 0V$

Using double-subscript notation:

$$V_{DS} = V_D - V_S$$

$$V_D = V_{DS} + V_S = V_{DS} + 0V$$

and $V_D = V_{DS}$

In addition, $V_{GS} = V_G - V_S$


and $V_G = V_{GS} + V_S = V_{GS} + 0V$

$$V_G = V_{GS}$$

Since the configuration requires two dc supplies, its use is limited.

SELF BIAS CONFIGURATION →

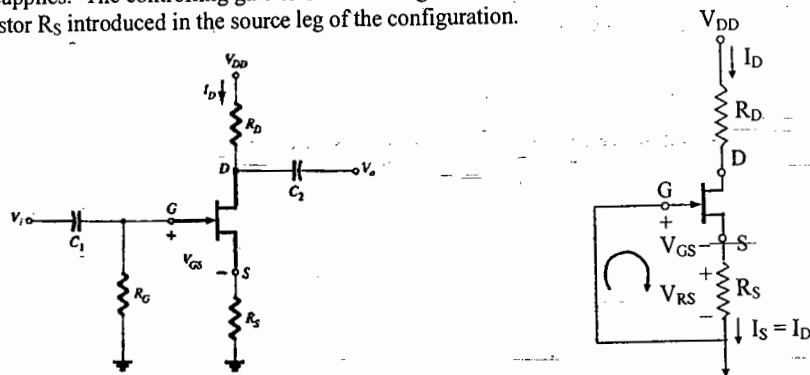The self-bias configuration eliminates the need for two dc supplies. The controlling gate-to-source voltage is now determined by the voltage across a resistor R_S introduced in the source leg of the configuration.



For the dc analysis the capacitors can again be replaced by "open circuits" and the resistor R_G replaced by a short circuit equivalent since $I_G = 0A$.

The current through R_S is the source I_S , but $I_S = I_D$ and $V_{RS} = I_D R_S$

For the indicated closed loop,

$$-V_{GS} - V_{RS} = 0$$

and $V_{GS} = -V_{RS}$

© Wiki Engineering

or $V_{GS} = -I_D R_S$

Note in this case that V_{GS} is a function of the output current I_D and not fixed in magnitude as occurred for the fixed-bias configuration.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$= I_{DSS} \left(1 - \frac{I_D R_S}{V_P} \right)^2$$

The quadratic equation can be solved for the appropriate solution for I_D

Applying Kirchhoff's voltage law to the output circuit,

$$V_{RS} + V_{DS} + V_{RD} - V_{DD} = 0$$

and $V_{DS} = V_{DD} - V_{RS} - V_{RD}$

$$= V_{DD} - I_D R_S - I_D R_D$$

but $I_D = I_S$

and $V_{DS} = V_{DD} - I_D (R_S + R_D)$

In addition:


$$V_S = I_D R_S$$

$$V_G = 0V$$

and $V_D = V_{DS} + V_S = V_{DD} - V_{RD}$

VOLTAGE-DIVIDER BIASING →

The voltage divider bias arrangement applied to BJT transistor amplifiers is also applied to FET amplifiers. The base construction is exactly the same, but the dc analysis of each is quite different. $I_G = 0A$ for FET amplifier, but the magnitude of I_B for common-emitter amplifiers can affect the dc levels of current and voltage in both the input and output circuits. I_B provided the link between input and output circuits for the BJT voltage-divider configuration while V_{GS} will do the same for the FET configuration

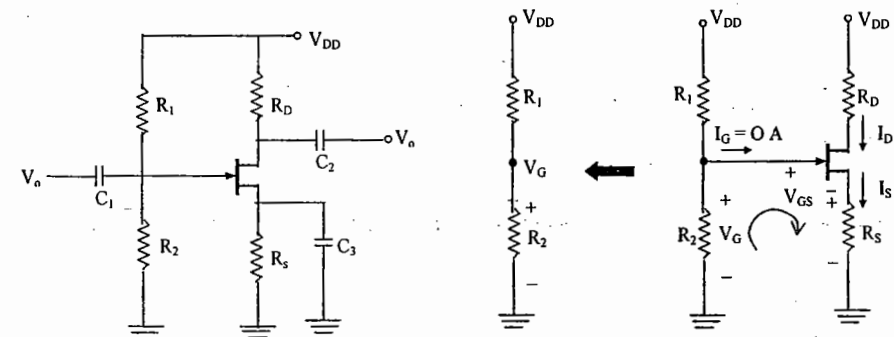

All the capacitors, including the by pass capacitor C_S , have been replaced by an "open circuit" equivalent. In addition, the source V_{DD} was separated into two equivalent sources to permit a further separation of the input and output regions of the network.

Since $I_G = 0A$, Kirchhoff's current law requires that $I_{R1} = I_{R2}$ using voltage divider rule:

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

Applying KVL in the clockwise direction to the indicated loop

$$V_G - V_{GS} - V_{RS} = 0$$

or $V_{GS} = V_G - V_{RS}$

$$V_{GS} = V_G - I_D R_S$$

Applying graphical analysis, $V_{GS} = V_G$ $I_D = 0 \text{ mA}$

$$I_D = \frac{V_G}{R_S} \quad V_{GS} = 0 \text{ V}$$

The two points defined above permit the drawing of a straight line to represent the equation. The intersection of the straight line with the transfer curve in the region to the left of the vertical axis will define the operating point and the corresponding levels of I_D and V_{GS} .

Once the quiescent values of I_{DQ} and V_{GSQ} are determined, the remaining network analysis can be performed in the usual manner. That is,

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$V_D = V_{DD} - I_D R_D$$

$$V_S = I_D R_S$$

$$I_{R1} = I_{R2} = \frac{V_{DD}}{R_1 + R_2}$$



The similarities in appearance between the transfer curves of JFETs the depletion type MOSFETs permit a similar analysis of each in the dc domain. The primary difference between the two in the fact that depletion type MOSFETs permit operating points with positive values of V_{GS} and levels of I_D that exceed I_{DSS} . In fact, for all the configurations discussed thus far, the analysis is the same if the JFET is replaced by a depletion-type MOSFET.

ENHANCEMENT TYPE MOSFETS

The transfer characteristics of the enhancement type MOSFET are quite different from those encountered for the JFET and depletion type MOSFETs resulting in a graphical solution quite different from the preceding sections. For the n-channel enhancement-type MOSFET, the drain current is zero for levels of gate-to-source voltage less than the threshold level $V_{GS(Th)}$. For levels of V_{GS} greater than $V_{GS(Th)}$, the drain current is defined by $I_D = K(V_{GS} - V_{GS(Th)})^2$ where

$$K = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(Th)})^2}$$

FEED BACK BIASING ARRANGEMENT →

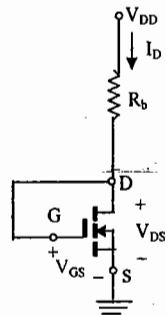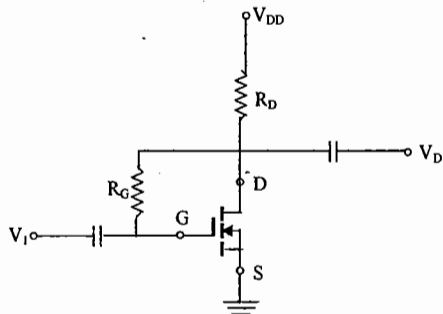

The resistor R_G brings a suitably large voltage to the gate to drive the MOSFET "on".

$I_G = 0 \text{ mA}$ and $V_{RG} = 0 \text{ V}$ for the dc equivalent network.

A direct connection now exists between drain and gate, resulting in $V_D = V_G$ and $V_{DS} = V_{GS}$.


For the output circuit, $V_{GS} = V_{DD} - I_D R_D$

Since the above equation is that of a straight line, the

points $V_{GS} = V_{DD}$ $I_D = 0 \text{ mA}$ and $I_D = \frac{V_{DD}}{R_D}$ $V_{GS} = 0 \text{ V}$

determine the two points that will define the plot on the graph.

VOLTAGE - DIVIDER BIASING ARRANGEMENT →

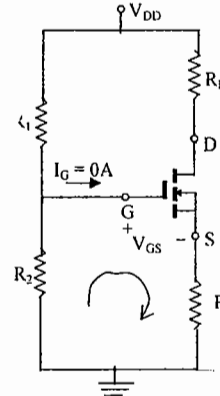

The fact that $I_G = 0 \text{ mA}$ results in the following equation for V_{GG} as derived from an application of the voltage-divider rule

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

Applying KVL around the indicated loop

$$+V_G - V_{GS} - V_{RS} = 0$$

$$V_{GS} = V_G - V_{RS}$$

$$V_{GS} = V_G - I_D R_S$$

For the output section:

$$V_{RS} + V_{DS} + V_{RD} - V_{DD} = 0$$

$$\text{and } V_{DS} = V_{DD} - V_{RS} - V_{RD}$$

$$\text{or } V_{DS} = V_{DD} - I_D (R_S + R_D)$$


since the characteristics are a plot of I_D versus V_{GS} and the above equation relates the same two variables, the two curves can be plotted on the same graph and a solution determined at their intersection. Once I_{DQ} and V_{GSQ} are known, all the remaining quantities of the network such as V_{DS} , V_D and V_S can be determined.

OBJECTIVES QUESTIONS - FET BIASING

1. An n-channel JFET, having a pinch off voltage (V_P) of $-5V$ shows a transconductance (gm) of 1mA/V when the applied gate-to-source voltage (V_{GS}) is $-3V$. Its maximum transconductance (in mA/V) is (GATE 2001, EEE)
- a) 1.5 b) 2.0 c) 2.5 d) 3.0

2. The value of R for which the PMOS transistor in figure will be biased in linear region is $+4V$ (GATE 2004, EEE)


- a) 220Ω
b) 470Ω
c) 680Ω
d) 1200Ω

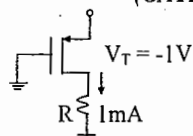

3. The action of a JFET in its equivalent circuit can best be represented as a (GATE 2003, ECE)
- a) current controlled current source b) current controlled voltage source
c) voltage controlled voltage source d) voltage controlled current source

4. The voltage gain $A_v \triangleq V_o / V_i$ of the JFET amplifier (GATE 02, ECE)

- a) +18
b) -18
c) +6
d) -6

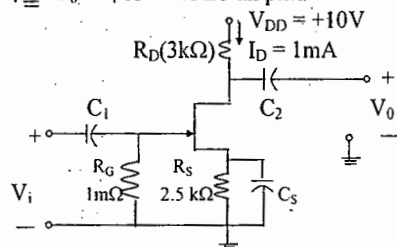


$I_{SS} = 10\text{mA}$
 $V_P = -5V$
(Assume C_1, C_2, C_3 to be very large)

5. Two identical FETs each characterized by the parameter g_m and r_d are connected in parallel. The composite FET is then characterized by the parameter. (GATE 98, ECE)
- a) $g_m/2$ and $2r_d$ b) $g_m/2$ and $r_d/2$ c) $2g_m$ and $r_d/2$ d) $2g_m$ and $2r_d$


06. In the MOSFET amplifier, the signal outputs V_1 and V_2 obey the relationship (GATE 98, ECE)

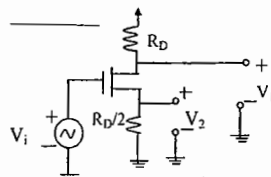- a) $V_1 = V_2 / 2$
b) $V_1 = -V_2 / 2$
c) $V_1 = 2V_2$
d) $V_1 = -2V_2$



7. The given figure shows a composite transistor continuity of a MOSFET and a bipolar transistor in cascade. The MOSFET has a transconductance g_m of 2mA/V and the bipolar transistor has β (Δh_{fe}) of 99. The overall transconductance of the composite transistor is (IES 99, ECE)

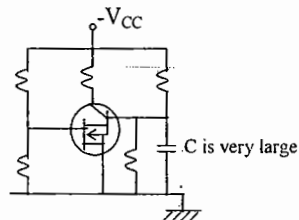- a) 198mA/V
b) 19.8mA/V
c) 1.98A/V
d) 198A/V



8. For an n-channel JFET, having drain-source voltage constant if the gate-source Voltage is increased (more negative) pinch-off would occur for
- a) High values of drain current b) Saturation values of drain current
c) Zero drain current d) Gate current equal to drain current

9. In modern MOSFETs, the material used for the gate is
- a) High quality silicon b) High purity silica
c) Heavily doped polycrystalline silicon d) Epitaxial grown silicon

10. The pinch-off voltage of a JFET is 5.0 volts. Its "cut-off" voltage is
- a) $(5.0)^{1/2}$ b) $2.5V$ c) $5.0V$ d) $(5.0)^{3/2}$

11. The transconductance g_m of a FET in the saturation region equals:

- a) $\frac{-2I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right)$ b) $\frac{-2I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right)^2$
c) $2I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^{1/2}$ d) $\frac{1}{V_P (I_{DSS} - I_{DS})^{1/2}}$

12. Consider the following statements:

Threshold voltage of a MOSFET can be lowered by

- 1) Using a thinner gate oxide 2) Reducing the substrate connection

- 3) Increasing the substrate connection

Of these statements:

- a) 3 alone is correct b) 1 and 2 are correct
c) 1 and 3 are correct d) 2 alone is correct

13. Consider the following devices:

1. BJT in CB mode 2. BJT in CE mode 3. JFET 4. MOSFET

The correct sequence of the devices in increasing order of their input impedances is:

- a) 1,2,3,4 b) 2,1,3,4 c) 2,1,4,3 d) 1,3,2,4

14. Match the items given in List- I (structures/characteristics) with List- II (Reasons) in respect of JFET and Select the correct answer using the codes given below the lists:

List-I

- A. N-channel JFET is better than P-channel JFET
B. Channel is wedge shaped
C. Channel is not completely closed at pinch-off
D. Input impedance is high

List-II


1. Reverse bias increases the channel
2. High electric field near the drain and directed towards source
3. Low leakage current at the gate terminal
4. Better frequency performance

Code:

- a) A-4, B-1, C-2, D-3
c) A-3, B-1, C-2, D-4

- b) A-4, B-2, C-1, D-3
d) A-3, B-2, C-1, D-4

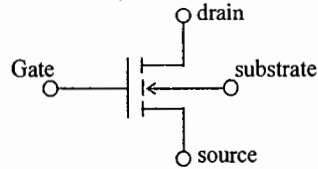15. The below Fig. Shows the circuit symbol of




- a) FET b) PMOS FET c) MOS FET d) NMOS FET

16. The output current versus input voltage transfer characteristic of an n-channel JFET is such that there is

- a) Zero current flow at zero input voltage bias
b) Current flow only when a positive input threshold voltage is crossed
c) Current flow only when a negative input cut-off voltage bias is crossed
d) No cut-off input voltage

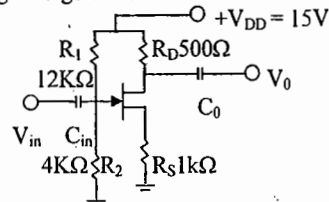17. A JFET circuit using voltage-divider bias is shown in fig. The gate voltage is



- a) 3.55V b) 3.65V c) 3.75V d) 3.85V

18. A JFET has a potential divider bias arrangement, if the resistor between the gate and power supply terminal is removed. The JFET will

- a) continue to work as an amplifier
b) have a forward bias gate w.r.t. source
c) not work as an amplifier but will work as switch
d) immediately burn out

19. An n-channel JFET has I_{DS} whose value is

- a) maximum for $V_{GS}=0$, and minimum for V_{GS} = negative and large
b) minimum for $V_{GS}=0$, and maximum for V_{GS} = negative and large
c) maximum for $V_{GS}=0$, and minimum for V_{GS} = positive and large
d) minimum for $V_{GS}=0$, and maximum for V_{GS} = positive and large

KEY: 1. c 2. d 3. d 4. d 5. c 6. a 7. d 8. c 9. c
10. c 11. a 12. c 13. a 14. a 15. d 16. c 17. c 18. a
19. a

Chapter - 3

SMALL SIGNAL MODELING & ANALYSIS

One of our first concerns in the sinusoidal ac analysis of transistor networks is the magnitude of the input signal. It will determine whether small signal or large signal techniques should be applied. There is no set dividing line between the two, but the application, and the magnitude of the variables of interest relative to the scales of the device characteristics, will usually make it quite clear which method is appropriate.

There are two models commonly used in the small-signal ac analysis of transistor networks. The r_e model and the hybrid equivalent model.


It is indeed fortunate that transistor small signal amplifiers can be considered linear for most applications, permitting the use of the superposition theorem to isolate the dc analysis from the ac analysis.

BJT TRANSISTOR MODELING →

A model is the combination of circuit elements, properly chosen, that best approximates the actual behavior of a semi conductor device under specific operating conditions. Once the ac equivalent circuit has been determined the graphic symbol of the device can be replaced in the schematic by this circuit and the basic methods of ac circuit analysis (mesh analysis, nodal analysis, and Thevenin's theorem) can be applied to determine the response of the circuit. The r_e model equivalent circuit is derived directly from the operating conditions of the transistor while the hybrid equivalent circuit suffers from being limited to a particular set of operating conditions if it is to be considered accurate. In turn, however, the r_e model fails to account for the output impedance level of the device and the feedback effect from output to input.

The ac equivalent of a network is obtained by setting all dc sources to zero and replacing them by a short circuit equivalent

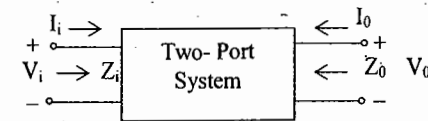THE IMPORTANT PARAMETERS: Z_i , Z_o , A_v , A_i




Input impedance, $Z_i \rightarrow$

For the input side, the input impedance Z_i is defined by Ohm's law as the following:

$$Z_i = \frac{V_i}{I_i}$$

For small-signal analysis, once the input impedance has been determined the same numerical value can be used for changing levels of applied signals. The input impedance of a BJT transistor amplifier is purely resistive in nature, and depending on the manner, in which the transistor is employed, can vary from a few ohms to megaohms.

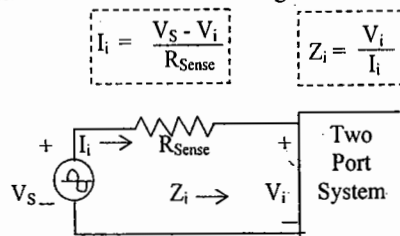The input impedance is then determined in the following manner:



The level of the input impedance can have a significant impact on the level of signal that reaches the system.


Output Impedance, $Z_0 \rightarrow$

The output impedance is determined at the output terminals looking back into the system with the applied signal set to zero.

The output impedance is determined

$$\text{by } I_0 = \frac{V - V_0}{R_{\text{Sense}}}$$

$$\text{and } Z_0 = V_0 / I_0$$

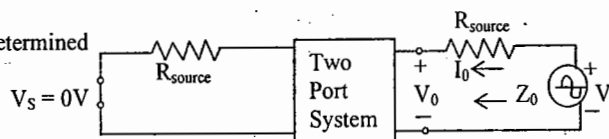

The output impedance of a BJT amplifier is resistive in nature and depending on the configuration and the placement of the resistive elements, Z_0 , can vary from a few ohms to a level that can exceed $2M\Omega$.

An ohmmeter cannot be used to measure the small signal ac input and output impedance since the ohmmeter operates in the dc mode.

Voltage Gain, $A_V \rightarrow$

One of the most important characteristics of an amplifier is the small signal ac voltage gain as determined by $A_V = V_0 / V_i$

$$\text{The no load voltage gain, } A_{VNL} = \frac{V_0}{V_i} \Big|_{R_L = \infty \Omega}$$

For transistor amplifiers, the no load voltage gain is greater than the loaded voltage gain
For the system having a source resistance R_s ,

$$A_{VS} = \frac{V_0}{V_S} = \frac{Z_i}{Z_i + R_S} A_{VNL}$$

Depending on the configuration, the magnitude of the voltage gain for a loaded single-stage transistor amplifier typically ranges from just less than 1 to a few hundred. A multi Stage system, however, can have a voltage gain in the thousands.


$$\text{Current Gain, } A_i \rightarrow A_i = \frac{I_0}{I_i}$$

For BJT amplifiers, the current gain typically ranges from a level just less than 1 to a level that may exceed 100.

$$\text{For the loaded situation } I_i = \frac{V_i}{Z_i} \text{ and } I_0 = \frac{-V_0}{R_L}$$

$$A_i = \frac{I_0}{I_i} = \frac{-V_0 / R_L}{V_i / Z_i} = \frac{-V_0}{V_i} \frac{Z_i}{R_L}$$

$$A_i = -A_V Z_i / R_L$$

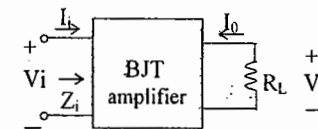


Phase Relationship \rightarrow

The phase relationship between input and output sinusoidal signals is important for a variety of practical reasons. Fortunately, however, for the typical transistor amplifier at frequencies that permit ignoring the effects of the reactive elements, the input and output signals are either 180° out of phase or in phase.

THE r_e TRANSISTOR MODEL \rightarrow

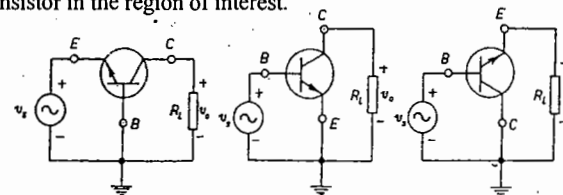The r_e model employs a diode and controlled current source to duplicate the behaviour of a transistor in the region of interest.



Common Base Configuration:

One junction of an operating transistor is forward biased while the other is reverse biased. The forward biased junction will behave much like a diode. For the base to emitter junction of the transistor the diode equivalence between the same two terminals seems to be quite appropriate. For the output side, $I_c \cong I_e$ (as derived from $I_c = \alpha I_e$) for the range of values of V_{CE} . The current source establishes the fact that $I_c = \alpha I_e$ with the controlling current I_e appearing in the input side of the equivalent circuit. We have therefore established an equivalence at the input and output terminals with the current-controlled source, providing a link between the two.

$$\text{The ac resistance of the diode, } r_e = \frac{26mV}{I_E}$$

Due to the isolation that exists between input and output circuits it should be fairly obvious that the input impedance $Z_i = r_e$

CB configuration: Typical values of Z_i range from a few ohms to a maximum of about 50 Ω .
The output impedance $Z_o \approx \infty \Omega$.

In actuality for the CB configuration, typical values of Z_o are in the mega ohm range.
In general, for the common base configuration the input impedance is relatively small and the output impedance quite high.

$$\text{Voltage gain, } A_v = \frac{V_o}{V_i} = \frac{-(I_o R_L)}{(I_c r_e)} = \frac{-(-I_c) R_L}{(I_c r_e)} = \frac{\alpha I_c R_L}{I_c r_e}$$

$$A_v = \frac{\alpha R_L}{r_e} \approx \frac{R_L}{r_e}$$

Current gain,

$$A_i = \frac{I_o}{I_i} = \frac{-I_c}{I_c} = \frac{-\alpha I_c}{I_c}$$

V_o and V_i are in phase for CB configuration

$$A_i = -\alpha \approx -1$$

CB

Common Emitter Configuration:

The controlled - current source is still connected between the collector and base terminals and the diode between the base and emitter terminals. In this configuration, the base current is the input current, while the output current is still I_c .

$$I_c = \beta I_b$$

The current through the diode $I_e = I_c + I_b = \beta I_b + I_b$

$$I_e = (\beta + 1) I_b$$

However, since the ac beta is typically much greater than 1,

$$I_e \approx \beta I_b$$

$$\text{Input impedance, } Z_i = \frac{V_i}{I_i} = \frac{-V_{be}}{I_b} \approx \frac{\beta I_b r_e}{I_b}$$

$$Z_i \approx \beta r_e$$

In other words, a resistive element in the emitter leg is reflected into the input circuit by a multiplying factor β .

Output impedance: $Z_o = r_o$. If the contribution due to r_o is ignored the output

impedance is defined by $Z_o = \infty \Omega$.

$$\text{Voltage gain, } A_v = \frac{V_o}{V_i}$$

$$= -R_L / r_e$$

$$r_o = \infty \Omega$$

The resulting minus sign for the voltage gain reveals that the output and input voltages are 180° out of phase.


$$\text{Current gain, } A_i = \frac{I_o}{I_i} = \frac{I_c}{I_b} = \beta \frac{I_b}{I_b}$$

$$\text{and } A_i = \beta$$

$$r_o = \infty \Omega$$

Common collector configuration: For the common collector configuration, the model defined for the common - emitter configuration is normally applied.

THE HYBRID EQUIVALENT MODEL

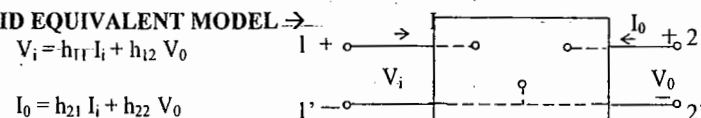

The parameter relating the four variables are called h - parameters from the word "hybrid". The term hybrid was chosen because the mixture of variables (V and I) in each equation results in a "hybrid" set of units of measurements for the h - parameters.

$$h_{11} = \frac{V_i}{I_i} \bigg|_{V_o = 0} \text{ ohms}$$

The ratio indicates that the parameter h_{11} is an impedance parameter with the units of ohms. Since it is the ratio of the input voltage to the input current with the output terminals shorted, it is called the short circuit input impedance parameter.

$$h_{12} = \frac{V_i}{V_o} \bigg|_{I_i = 0} \text{ unit-less.}$$

The parameter h_{12} , therefore, is the ratio of the input voltage to the output voltage with the input current equal to zero. It has no units since it is a ratio of voltage levels and is called the open - circuit reverse transfer voltage ratio parameter.

$$h_{21} = \frac{I_o}{I_i} \bigg|_{V_o = 0} \text{ unit-less}$$

The parameter h_{21} is the ratio of the output current to the input current with the output terminals shorted. This parameter has no units since it is the ratio of current levels. It is formally called the short - circuit forward transfer current ratio parameter.

$$h_{22} = \frac{I_o}{V_o} \bigg|_{I_i = 0} \text{ Siemens}$$

Since it is the ratio of the output current to the output voltage, it is the output conductance parameter and is measured in Siemens(S). It is called the open circuit output admittance parameter.

Apply Kirchoff's voltage law "in reverse" to find the input circuit. Since the parameter h_{11} has the unit ohm, it is represented by a resistor. The quantity h_{12} is dimensionless and therefore simply appears as a multiplying factor of the "feed back" term in the input circuit.


Apply Kirchhoff's current law 'in reverse' to obtain the output circuit. Since h_{22} has the units of admittance, which for the transistor model is conductance, it is represented by the resistor symbol. Whose value is equal to h_0 .

h_{11} = input resistance $\rightarrow h_i$


h_{12} = reverse transfer voltage ratio $\rightarrow h_r$

h_{21} = forward transfer current ratio $\rightarrow h_f$

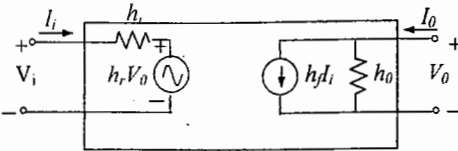h_{22} = output conductance $\rightarrow h_0$



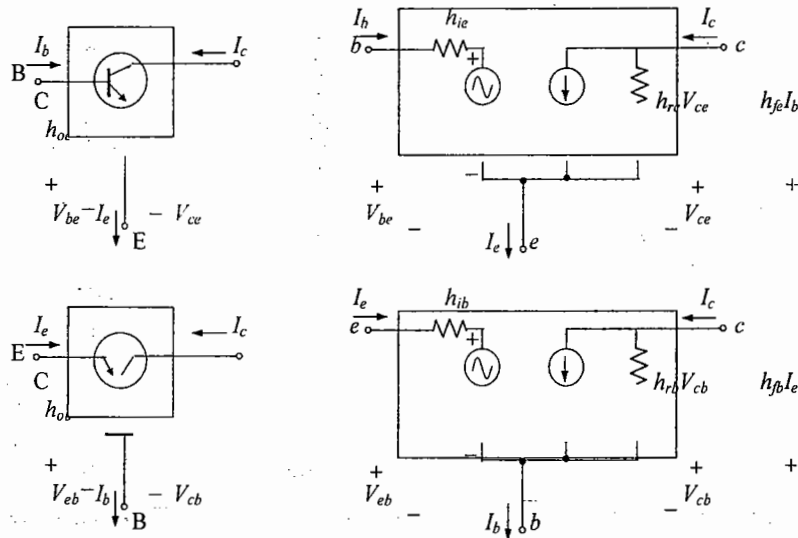The above circuit is applicable to any linear three terminal electronic device or system with no internal independent sources. For the transistor, therefore, even though it has three basic configurations, they are all three-terminal configurations, so that the resulting equivalent circuit will have the same format. The h parameter, however, will change with each configuration.




For the CE configuration, $I_i = I_b$, $I_o = I_c$ and through an application of Kirchhoff's current law, $I_e = I_b + I_c$. The input voltage is now V_{be} with the output voltage V_{ce} .

For the CB configuration, $I_i = I_e$, $I_o = I_c$ with $V_{eb} = V_i$ and $V_{cb} = V_o$. The above networks are applicable for pnp as well npn transistors.

For the CE and CB configurations the magnitude of h_r and h_0 is often such that the results obtained for the important parameter such as Z_i , Z_o , A_v and A_i are only slightly affected if they (h_r and h_0) are not included in the model.

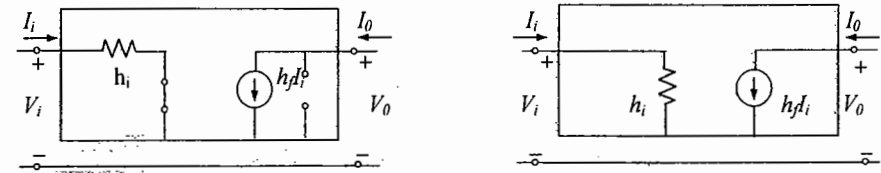Since h_r is normally a relatively small quantity, its removal is approximated by $h_r \approx 0$ and $h_r V_o = 0$, resulting in a short circuit equivalent for the feed back element. The resistance determined by $1/h_0$ is often large enough to be ignored in comparison to a parallel load permitting its replacement by an open-circuit equivalent for the CE and CB models.



Also note the relationship between the hybrid and r_e - models.

$$h_{ie} = \beta r_e$$

$$\text{and } h_{fe} = \beta_{ac}$$

$$h_{ib} = r_e$$

and $h_{ob} = -\alpha \approx -1$. The minus sign accounts for the fact that the current source of the standard hybrid model is putting down rather than in the actual direction in the r_e model.

The hybrid parameter h_{fe} (β_{ac}) is the least sensitive of the hybrid parameters to a change in collector circuit. Assuming, therefore that $h_{fe} = \beta$ is a constant for the range of interest is a fairly good approximation. It is $h_{ie} = \beta r_e$ that will vary significantly with I_c and should be determined at operating levels, since it can have a real impact on the gain levels of a transistor amplifier.

The approximate relations between the parameters are given below:

Common - Emitter Configuration

$$h_{ie} \approx \frac{h_{ib}}{1 + h_{ib}} \approx \beta r_e$$

$$h_{re} \approx \frac{h_{ib} h_{ob}}{1 + h_{ib}} - h_{rb}$$

$$h_{fe} \approx \frac{-h_{ib}}{1 + h_{ib}} \approx \beta$$

$$h_{oe} \approx \frac{h_{ob}}{1 + h_{ib}}$$

Common-Base Configuration

$$h_{ib} \approx \frac{h_{ie}}{1 + h_{fe}} \approx \frac{-h_{ie}}{h_{fe}} \approx r_e$$

$$h_{rb} \approx \frac{h_{ie} h_{oe}}{1 + h_{fe}} - h_{re} \approx h_{re} - 1 - \frac{h_{ie} h_{oe}}{h_{fe}}$$

$$h_{fb} \approx \frac{-h_{fe}}{1 + h_{fe}} \approx \frac{-(1 + h_{fe})}{h_{fe}} \approx -\alpha$$

$$h_{ob} \approx \frac{h_{oe}}{1 + h_{fe}} \approx \frac{-h_{oe}}{h_{fe}}$$

Common-Collector Configuration

$$h_{ic} \cong \frac{h_{ib}}{1 + h_{fb}} \cong \beta r_e$$

$$h_{rc} \cong 1$$

$$h_{fe} \cong \frac{-1}{1 + h_{fb}} \cong -\beta$$

$$h_{oc} \cong \frac{h_{ob}}{1 + h_{fb}}$$

Characteristics of Common Base Amplifier

- Current gain is less than unity and its magnitude decreases with the increase of load resistance R_L
- Voltage gain A_v is high for normal values of R_L
- The input resistance R_i is the lowest of all the three configurations, and
- The output resistance R_o is the highest of all the three configurations.

Applications The CB amplifier is not commonly used for amplification purpose. It is used for

- matching a very low impedance source
- as a non-inverting amplifier with voltage gain exceeding unity
- for driving a high impedance load
- as a constant current source

Characteristics of Common Emitter Amplifier

- The current gain A_i is high for $R_L (< 10K\Omega)$
- The Voltage gain is high for normal values of load resistance R_L
- The input resistance R_i is medium, and
- The output resistance R_o is moderately high.

Applications Of the three configurations CE amplifier alone is capable of providing both voltage gain and current gain. Further the input resistance R_i and the output resistance R_o are moderately high. Hence CE amplifier is widely used for amplification purpose.

Characteristics of Common Collector Amplifier

For low value of $R_L (< 10K\Omega)$ the current gain A_i is high and almost equal to that of a CE amplifier,

- The voltage gain A_v is less than unity,
- The input resistance is the highest of all the three configurations, and
- The output resistance is the lowest of all the three configurations

Applications The CC amplifier is widely used as a buffer stage between a high Impedance source and a low impedance load. The CC amplifier is called the Emitter Follower:

FET SMALL SIGNAL MODEL:-

The ac analysis of a FET configuration requires that a small signal ac model for the FET be developed.

The gate - to - source voltage controls the drain - to - source (channel) current of an FET through a relationship known as Shockley's equation:

$$I_D = I_{DSS} (1 - V_{GS} / V_p)^2$$

The change in collector current that will result from a change in gate - to - source voltage can be determined using the transconductance factor g_m :

$$\Delta I_D = g_m \Delta V_{GS}$$

Solving for g_m we have:


$$g_m = \Delta I_D / \Delta V_{GS}$$

g_m is actually the slope of the transfer characteristics at the point of operation. That is,

$$g_m = m = \Delta y / \Delta x = \Delta I_D / \Delta V_{GS}$$

The slope, and therefore g_m , increase as we progress from V_p to I_{DSS} . Or, in other words, as V_{GS} approaches 0V, the magnitude of g_m increases.

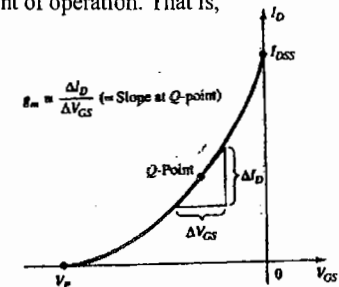An alternative approach to determine g_m employs the fact that the derivative of a function at a point is equal to the slope of the tangent line drawn at that point.



$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} \Big|_{Q-pt} = \frac{d I_D}{d V_{GS}} \Big|_{Q-pt} = \frac{d}{d V_{GS}} [I_{DSS} (1 - V_{GS} / V_p)^2]$$

$$= I_{DSS} \frac{d}{d V_{GS}} (1 - \frac{V_{GS}}{V_p})^2$$

$$= 2 I_{DSS} [1 - \frac{V_{GS}}{V_p}] \frac{d}{d V_{GS}} (1 - \frac{V_{GS}}{V_p})$$

$$= 2 I_{DSS} [1 - \frac{V_{GS}}{V_p}] \frac{d}{d V_{GS}} (1 - \frac{1}{V_p} \cdot \frac{d V_{GS}}{d V_{GS}})$$

$$= 2 I_{DSS} [1 - \frac{V_{GS}}{V_p}] [0 - \frac{1}{V_p}]$$

$$\text{and } g_m = \frac{2 I_{DSS}}{|V_p|} [1 - \frac{V_{GS}}{V_p}]$$

where $|V_p|$ denotes magnitude only to ensure a positive value for g_m .

Maximum value of g_m for JFET in which I_{DSS} and V_p are specified is $g_m = \frac{2 I_{DSS}}{|V_p|} (1 - \frac{0}{V_p})$

$$g_{m0} = \frac{2 I_{DSS}}{|V_p|}$$

$$g_m = g_{m0} (1 - \frac{V_{GS}}{V_p})$$

A mathematical relationship between g_m and the dc bias current I_D can be derived by noting that Shockley's equation can be written in the following form:

$$1 - \frac{V_{GS}}{V_p} = \sqrt{\frac{I_D}{I_{DSS}}}$$

$$\therefore g_m = g_{m0} (1 - \frac{V_{GS}}{V_p}) = g_{m0} \sqrt{\frac{I_D}{I_{DSS}}}$$

Note if $I_D = I_{DSS}$, $g_m = g_{m0}$

$$I_D = \frac{I_{DSS}}{2}, \quad g_m = 0.707 g_{m0}$$

$$I_D = \frac{I_{DSS}}{4}, \quad g_m = 0.5 g_{m0}$$

Input Impedance $Z_i \rightarrow$ The input impedance of all commercially available FETs is sufficiently large to assume that the input terminals approximate an open circuit. In equation form,

$$Z_i (\text{FET}) = \infty \Omega$$

Output impedance $Z_o \rightarrow$


$$Z_o (\text{FET}) = r_d = \left. \frac{\Delta V_{DS}}{\Delta I_D} \right|_{V_{GS} = \text{constant}}$$

The output impedance is defined on the characteristics as the slope of the horizontal characteristic curve at the point of operation.

FET AC Equivalent Circuit \rightarrow

The control of I_D by V_{GS} is included as a current source $g_m V_{gs}$ connected from drain to source. The current source has its arrow pointing from drain to source to establish a 180° phase shift between output and input voltages.


The input impedance is represented by the open circuit at the input terminals and the output impedance by the resistor r_d from drain to source. Note that the gate to source voltage is now represented by V_{gs} to distinguish it from dc levels. The source is common to both input and output circuits while the gate and drain terminals are only in "touch" through the controlled current source $g_m V_{gs}$.

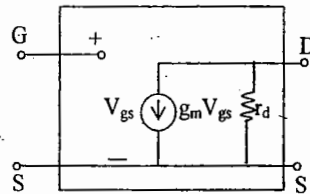

OBJECTIVES SET - A

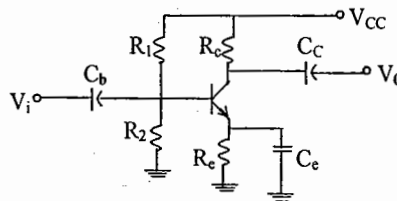1. In the transistor amplifier shown in the figure, the ratio of small signal voltage gain when the emitter resistor R_e is bypassed by the capacitor C_e to when it is not bypassed, (assuming simplified approximate h-parameter model for transistor, is

- 1
- h_{fe}
- $\frac{(1 + h_{fe}) R_e}{h_{ie}}$
- $1 + \frac{(1 + h_{fe}) R_e}{h_{ie}}$




2. One of the applications of current mirror is

- output current limiting
- obtaining a very high current gain
- current feed back
- temperature stabilized biasing

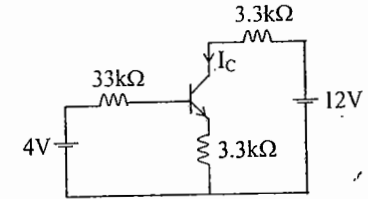
3. In the circuit, assume that the transistor has $h_{FE} = 99$ and $V_{BE} = 0.7$ V. The value of collector current I_C of the transistor is approximately

- $[3.3 / 3.3]$ mA
- $[3.3 / (3.3 + 0.33)]$ mA
- $[3.3 / 33]$ mA
- $[3.3 / (33 + 3.3)]$ mA




4. The transconductance g_m of the transistor shown is 10 mS. The value of the input resistance R_{in} is

- 10.0 kΩ
- 8.3 kΩ
- 5.0 kΩ
- 2.5 kΩ

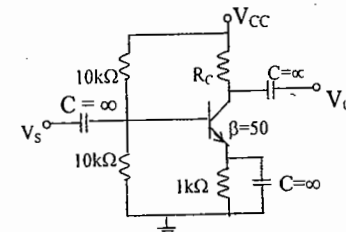

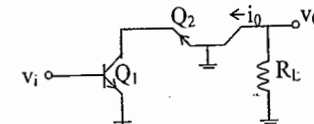5. In the CASCODE amplifier, if the common emitter stage (Q_1) has a transconductance g_{m1} , and the common base stage (Q_2) has a transconductance g_{m2} , then the overall transconductance is

- g_{m1}
- g_{m2}
- $g_{m1}/2$
- $g_{m2}/2$




6. The f_T of a BJT is related to its g_m , C_π and C_μ as follows :

- $f_T = \frac{C_\pi + C_\mu}{g_m}$
- $f_T = \frac{2\pi(C_\pi + C_\mu)}{g_m}$
- $f_T = \frac{g_m}{C_\pi + C_\mu}$
- $f_T = \frac{g_m}{2\pi(C_\pi + C_\mu)}$

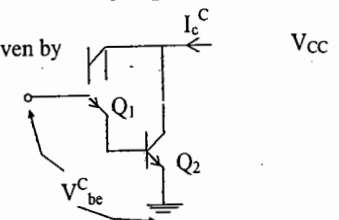7. A Darlington stage is shown. If the transconductance of Q_1 is g_{m1} and Q_2 is g_{m2} , then the

overall transconductance $g_{mc} = \left(\frac{\Delta I_C}{\Delta V_{be}} \right)$ is given by

- g_{m1}
- $0.5 g_{m1}$
- g_{m2}
- $0.5 g_{m2}$



8. For a bipolar transistor, h_{oe} has the dimensions of
 (a) Ohms, (b) Siemens, (c) Amperes, (d) mhos,
9. The common-emitter leakage current of a bipolar transistor is high, if
 (a) the temperature is high, (b) the temperature is low,
 (c) V_{CE} is high, (d) h_{re} is high, (e) the frequency is high.
10. The h-parameter model is more commonly used because
 (a) the h-parameters can be measured more accurately,
 (b) the h-parameters do not vary with frequency,
 (c) the analysis, using the h-parameters, gives the same expressions for the performance measures for all the configurations,
 (d) the h-parameter model is an accurate representation of the transistor mechanism.
11. The potential divider bias is more commonly used because it
 (a) uses minimum circuit components.
 (b) uses only one battery,
 (c) does not reduce the input and output impedances drastically,
 (d) stabilises the collector current.
12. The common collector circuit has a voltage gain which is
 (a) much higher than unity, (b) equal to unity, –
 (c) slightly less than unity, (d) far less than unity.
13. The circuit, having the lowest input impedance, is
 (a) a C-E circuit, (b) a C-B circuit, (c) a C-C circuit, (d) none of the above.
14. The approximate C-E h-parameter model can be used for analysis when
 (a) h_{re} is very small (b) h_{oe} is very small
 (c) R_L is very small (d) h_{re} and ($h_{oe} R_L$ are very small)
15. In an R-C coupled amplifier, if the emitter by-pass capacitor C_e is disconnected, the mid-band gain of the stage will
 (a) increase (b) decrease (c) remain unchanged (d) become unstable.

16. The common-base stage is not used for a cascaded chain AF amplifiers because of its
 (a) low input resistance (b) low-current gain
 (c) high-output resistance (d) zero phase-shift for the signal
17. In an R-C coupled amplifier, the low frequency response will be improved by
 (a) decreasing the value of the coupling capacitor
 (b) increasing the value of the coupling capacitor
 (c) removing the coupling capacitor
 (d) none of the above.
18. The short-circuit current gain-bandwidth product of a transistor changes with change in
 (a) the configuration (b) the operating collector current
 (c) the value of load impedance (d) the value of source impedance

Key- SET A

1. 2.d 3.b 4.c 5.a 6.d 7.a 8.b 9.a 10.d 11.d 12.b
 13.b 14.d 15.b 16.a 17.c 18.b

SET - B

01. Choose the correct match for input resistance of various amplifier configurations shown below


Configuration	Input resistance
CB: Common Base	LO: Low
CC: Common Collector	MO: Moderate
CE: Common emitter	HI: High

- (A) CB – LO, CC – MO, CE – HI –
 (B) CB – LO, CC – HI, CE – MO
 (C) CB – MO, CC – HI, CE – LO
 (D) CB – HI, CC – LO, CE – MO

02. The transistor in the amplifier shown has following parameters:

$h_{fe} = 100$, $h_{ie} = 2 \text{ K}\Omega$, $h_{re} = 0$, $h_{oe} = 0.5 \text{ m mhos}$,
 The output impedance is

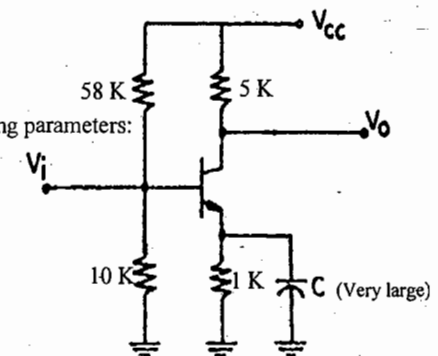- (A) $20 \text{ K}\Omega$ (B) $16 \text{ K}\Omega$
 (C) $5 \text{ K}\Omega$ (D) $4 \text{ K}\Omega$



03. The configuration of a CASCODE amplifiers is

- (A) CE – CE (B) CE – CB (C) CC – CB (D) CC – CC


KEY: (1) B (2) D (3) B

Chapter: 4

FREQUENCY RESPONSE

The frequency of the applied signal can have a pronounced effect on the response of a single or multistage network. At low frequencies we shall find that the coupling and bypass capacitors can no longer be replaced by the short circuit approximation because of the increase in reactance of these elements. The frequency-dependent parameters of the small signal equivalent circuits and the stray capacitive elements associated with the active device and the network will limit the high-frequency response of the system. An increase in the number of stages of a cascaded system will also limit both the high and low-frequency responses.

For the RC coupled amplifiers the drop at low frequencies is due to the increasing reactance of C_C , C_S , or C_E , while its upper frequency limit is determined by either the parasitic capacitive elements of the network and frequency dependence of the gain of the active device. For the direct coupled amplifier, there are no coupling or bypass capacitors to cause a drop in gain at low frequencies. As the figure indicates, it is a flat response to the upper cutoff frequency which is determined by either the parasitic capacitances of the circuit or the frequency dependence of the gain of the active device.

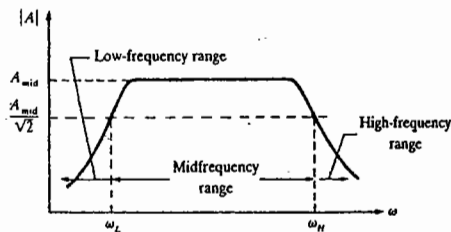

There is a band of frequencies in which the magnitude of the gain is either equal or relatively close to the mid band value. To fix the frequency boundaries of relatively high gain, $0.707 A_{v\text{mid}}$ is chosen to be the gain at the cutoff levels. The corresponding frequencies (f_L) and (f_H) are generally called the corner, cutoff, break, or half power frequencies. The multiplier 0.707 was chosen because at this level the output power is half the mid band power output, that is, at mid frequencies,

$$P_{0\text{mid}} = \frac{|V_0|^2}{R_0} = \frac{|A_{v\text{mid}} V_i|^2}{R_0}$$

and at the half-power frequencies,

$$P_{0\text{HPF}} = \frac{|0.707 A_{v\text{mid}} V_i|^2}{R_0} = 0.5 \frac{|A_{v\text{mid}} V_i|^2}{R_0}$$

$$\text{and } P_{0\text{HPF}} = 0.5 P_{0\text{mid}}$$

The band width of each system is determined by f_1 and f_2 ,

$$\text{Band width} = BW = f_2 - f_1$$

A decibel plot can be obtained by applying

$$\left| \frac{A_v}{A_{v\text{mid}}} \right|_{\text{dB}} = 20 \log_{10} \frac{A_v}{A_{v\text{mid}}}$$


It should be understood that most amplifiers introduce a 180° phase shift between input and output signals only in the midband region. At low frequencies there is a phase shift such that V_0 lags V_i by an increased angle. At high frequencies the phase shift will drop below 180° .

Low Frequency Response – BJT Amplifier

The analysis here will employ the loaded voltage – divider BJT bias configuration, but the results can be applied to any BJT configuration. For the following network, the capacitors C_S , C_C and C_E will determine the low frequency response.

C_c : Since C_c is normally connected between the applied source and the active device, the general form of the RC configuration is established by the following network. The total resistance is now $R_S + R_i$ and the cut off frequency is
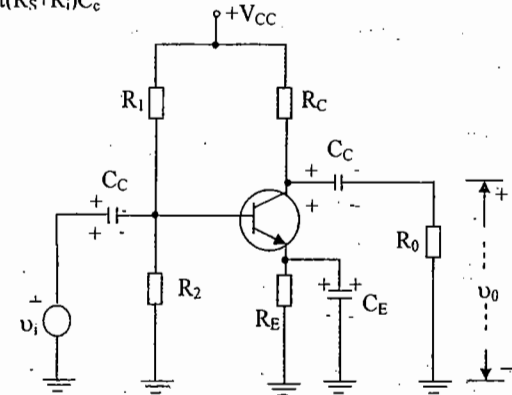
$$f_{Ls} = \frac{1}{2\pi(R_S + R_i)C_c}$$



At mid-or high frequencies the reactance of the capacitor will be sufficiently small to permit a short circuit approximation for the element. The voltage V_i will then be related to V_s by


$$\left| \frac{V_i}{V_s} \right|_{\text{mid}} = \frac{R_i}{R_i + R_S}$$

At f_{Ls} the voltage V_i will be 70.7% of the value determined by above equation assuming that C_c is the only capacitive element controlling the low frequency response.

The voltage V_i applied to the input of the active device can be calculated using the voltage-divider Rule:

$$V_i = \frac{R_i V_s}{R_S + R_i - jX_{C_c}}$$

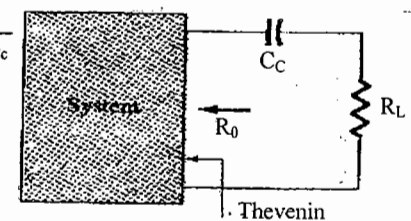C_C : Since the coupling capacitor is normally connected between the output of the active device and the applied load, the R-C configuration that determines the low cutoff frequency due to C_C appears as shown




The total series resistance is now $R_0 + R_L$ and the cutoff frequency due to C_C is determined by

$$f_{LC} = \frac{1}{2\pi(R_0 + R_L)C_C}$$

Ignoring the effects of C_S and C_E , the output voltage V_0 will be 70.7% of its mid band value at f_{LC} .
Where $R_0 = R_D || r_d$

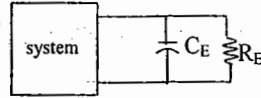C_E : To determine f_{LE} the network "seen" by C_E must be determined



Once the level of R_E is established, the cutoff frequency due to C_E can be determined using the following

equation:
$$f_{LE} = \frac{1}{2\pi R_E C_E}$$


At f_{LE} the gain will be 3db below the mid band value determined with R_E "shorted out".

Although each will affect the gain $A_V = V_0/V_i$ in a similar frequency range, the highest low frequency cut off determined by C_S , C_C or C_E will have the greatest impact since it will be the last encountered before the midband level.

Low Frequency Response – FET Amplifier

The analysis of the FET amplifier in the low-frequency region will be quite similar to that of the BJT amplifier. There are again three capacitors of primary concern:


C_G , C_C and C_S .

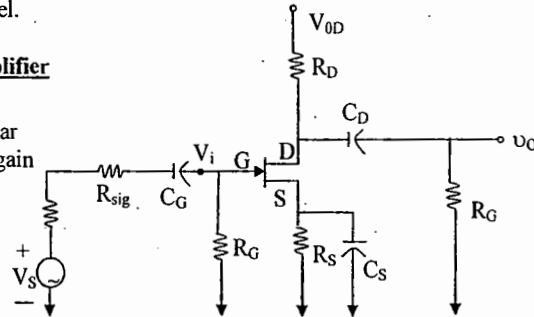

C_G : For the coupling capacitor between the source and the active device the ac equivalent network is as shown

The cutoff frequency determined by C_G will then be
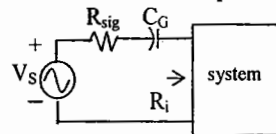
$$f_{LG} = \frac{1}{2\pi(R_{sig} + R_i)C_G} \quad \text{Also } R_i = R_G$$



Typically, $R_G \gg R_{sig}$ and the lower cutoff frequency will be determined primarily by R_G and


C_G . The fact that R_G is so large permits a relatively low level of C_G while maintaining a low

cutoff frequency level for f_{LG} .

C_C : For the coupling capacitor between the active device and the load the network is as shown:

The resulting cutoff frequency is

$$f_{LC} = \frac{1}{2\pi(R_0 + R_L)C_C}, \quad \text{where } R_0 = R_D || r_d$$

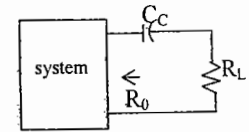


C_S : For the source capacitor C_S The cutoff frequency is

$$f_{LS} = \frac{1}{2\pi R_{eq} C_S}$$

$$\text{Where, } R_{eq} = \frac{R_S}{1 + R_S [(1 + g_m r_d) / (r_d + R_D || R_L)]}$$

Which for $r_d \approx \infty \Omega$ becomes

$$R_{eq} = \frac{R_S}{1 + R_S g_m} = R_S || \frac{1}{g_m}$$

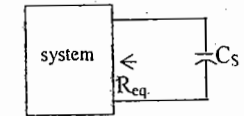

Miller Effect Capacitance \rightarrow

In the high frequency region the capacitive elements of importance are the inter electrode (between terminals) capacitances internal to the active device and the wiring capacitance between leads of the network. The large capacitors of the network that controlled the low-frequency response have all been replaced by their short-circuit equivalent due to their very low reactance levels.

For inverting amplifiers (phase shift of 180° between input and output resulting in a negative value for A_V) the input and output capacitances are increased by a capacitance level sensitive to the inter electrode capacitance between the input and output terminals of the device C_f and the gain of the amplifier. C_f is the "feedback" capacitance.

Miller input capacitance \rightarrow

Applying KCL gives $I_i = I_1 + I_2$

Using ohm's law yields

$$I_1 = \frac{V_i}{Z_i}, \quad I_2 = \frac{V_i}{R_f}$$



$$\text{and } I_2 = \frac{V_i - V_0}{X_{Cf}} = \frac{V_i - A_V V_i}{X_{Cf}} = \frac{(1 - A_V)V_i}{X_{Cf}}$$

Substituting, we obtain

$$\frac{V_i}{Z_i} = \frac{V_i}{R_i} + \frac{(1 - A_V)V_i}{X_{Cf}}$$

$$\text{and } \frac{1}{Z_i} = \frac{1}{R_i} + \frac{1}{X_{Cf}(1 - A_V)}$$
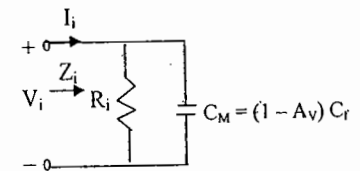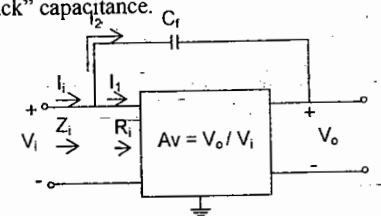
$$\frac{1}{\omega(1 - A_V)C_f} = X_{CM}$$




$$\text{and } \frac{1}{Z_i} = \frac{1}{R_i} + \frac{1}{X_{cm}}$$

In general, therefore, the Miller effect input capacitance is defined by: $C_{Mi} = (1 - A_v)C_f$

For any inverting amplifier the input capacitance will be increased by Miller effect capacitance.

Miller output Capacitance →

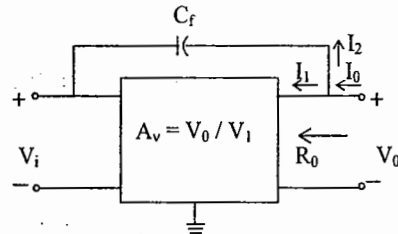

The Miller effect will also increase the level of output capacitance, which must also be considered when the high-frequency cutoff is determined. Applying KCL will result in

$$I_0 = I_1 + I_2$$

$$\text{With } I_1 = \frac{V_o}{R_o} \quad \text{and } I_2 = \frac{(V_o - V_i)}{X_{Cf}}$$

The resistance R_o is usually sufficiently large to permit ignoring the first term of the equation compared to the second term and assuming that

$$I_0 \cong \frac{(V_o - V_i)}{X_{Cf}}$$

Substituting $V_i = V_o / A_v$ from $A_v = V_o / V_i$ will result in

$$I_0 = \frac{V_o - V_o / A_v}{X_{Cf}} = \frac{V_o (1 - 1/A_v)}{X_{Cf}}$$

$$\text{and } \frac{I_0}{V_o} = \frac{1 - 1/A_v}{X_{Cf}}$$

$$\begin{aligned} \text{(or)} \quad \frac{V_o}{I_0} &= \frac{X_{Cf}}{1 - 1/A_v} \\ &= \frac{1}{\omega_{Cf} (1 - 1/A_v)} \\ &= \frac{1}{\omega_{C_{Mo}}} \end{aligned}$$

resulting in the following equation for the Miller output capacitance:


$$C_{Mo} = (1 - 1/A_v) C_f$$

For the usual situation where $|A_v| \gg 1$


$$C_{Mo} \cong C_f$$

High Frequency Response – BJT Amplifier →

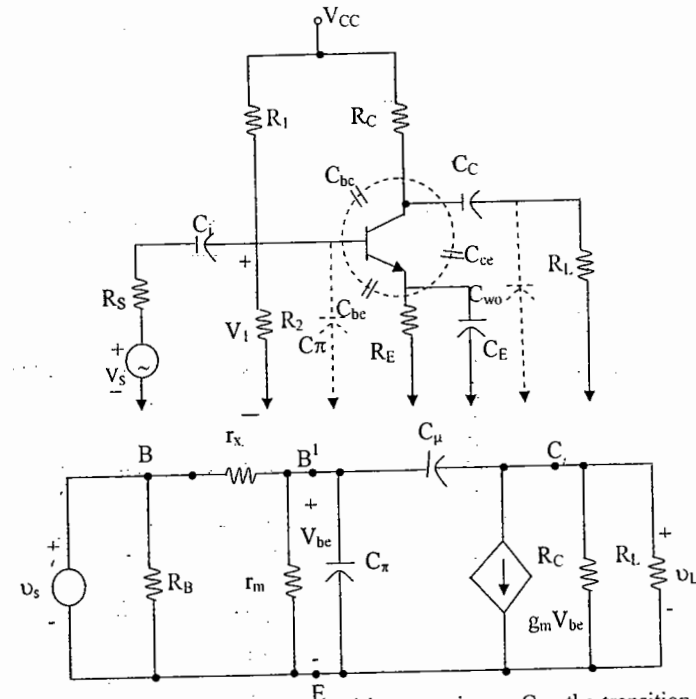At the high-frequency end there are two factors that will define the -3dB point: the network capacitance (parasitic and introduced) and the frequency dependence of $h_{fe}(\beta)$.



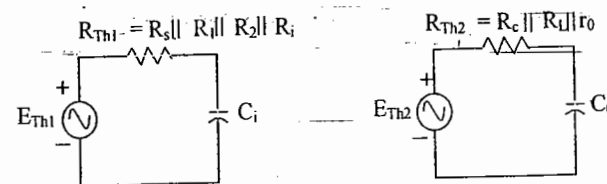The capacitance C_i includes the input wiring capacitance C_{wi} , the transition capacitance C_{be} and the Miller capacitance C_{Mi} . The capacitance C_o includes the output wiring capacitance C_{wo} , the parasitic capacitance C_{ce} , and the output Miller Capacitance C_{Mo} . The Thevenin equivalent circuit for the input and output networks are



For the network the -3dB frequency is defined by $f_{Hi} = \frac{1}{2\pi R_{Th1} C_i}$

$$\text{with } R_{Th1} = R_s \parallel R_1 \parallel R_2 \parallel R_i$$

$$\text{and } C_i = C_{wi} + C_{be} + C_{Mi} = C_{wi} + C_{be} + (1 - A_v) C_{be}$$

At very high frequencies the effect of C_i is to reduce the total impedance of the parallel combination of R_1 , R_2 , R_i and C_i . The result is a reduced level of voltage across C_i —a reduction in I_b and gain for the system.

For the output network, $f_{H0} = \frac{1}{2\pi R_{Th2} C_0}$


$$\text{with } R_{Th2} = R_D \parallel R_L \parallel r_d$$

$$\text{and } C_0 = C_{w0} + C_{ce} + C_{M0}$$

At very high frequencies the capacitive reactance of C_0 will decrease and consequently reduce the total impedance of the output parallel branches.


The frequencies f_{Hi} and f_{Ho} will each define a -6dB/octave asymptote. The lowest frequency would be the determining factor.

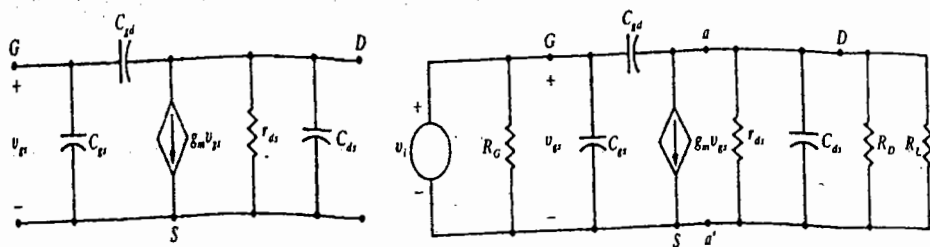High Frequency Response - FET Amplifier →



At high frequencies C_i will approach a short-circuit equivalent and V_{gs} will drop in value and reduce the overall gain. At frequencies where the C_0 approaches its short circuit equivalent the parallel output voltage V_0 will drop in magnitude.

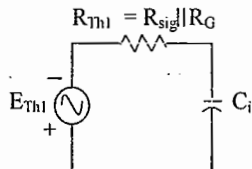The cutoff frequencies defined by the input and output circuits can be obtained by first finding the Thevenin equivalent circuits.



For the input circuit,

$$f_{Hi} = \frac{1}{2\pi R_{Th1} C_i}$$

$$\text{and } R_{Th1} = R_{sig} \parallel R_G$$

$$\text{with } C_i = C_{wi} + C_{gs} + C_{Mi}$$

$$\text{and } C_{Mi} = (1 - A_v) C_{gd}$$

and for the output circuit,


$$f_{Ho} = \frac{1}{2\pi R_{Th2} C_0}$$

$$\text{with } R_{Th2} = R_D \parallel R_L \parallel r_d$$

$$\text{and } C_0 = C_{w0} + C_{ds} + C_{M0}$$

$$\text{and } C_{M0} = \left(1 - \frac{1}{A_v}\right) C_{gd}$$

Multistage Frequency Effects

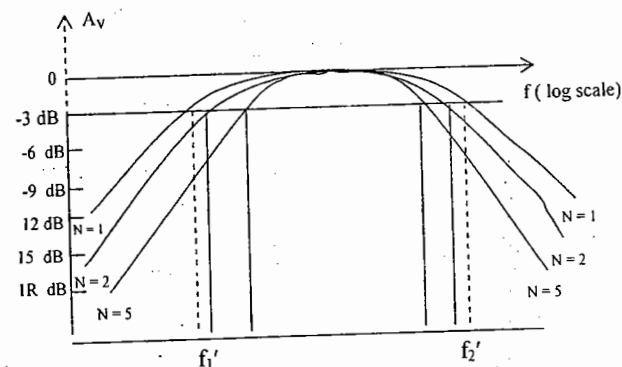

For n stages

$$A_{v \text{ low (overall)}} = A_{v1 \text{ low}} \times A_{v2 \text{ low}} \times A_{v3 \text{ low}} \dots \times A_{vn \text{ low}}$$

$$A_{v \text{ low (overall)}} = (A_{v1 \text{ low}})^n, \text{ for identical stages.}$$

$$\text{Or } \frac{A_{v1 \text{ low (overall)}}}{A_{v \text{ mid}}} = \left(\frac{A_{v1 \text{ low}}}{A_{v \text{ mid1}}} \right)^n = \frac{1}{(1 - j f_1/f)^n}$$

Setting the magnitude of this result equal to $\frac{1}{\sqrt{2}}$ (-3dB level) results in

$$f_1' = \frac{f_1}{\sqrt{2^{1/n} - 1}}$$

In a similar manner, it can be shown that for the high frequency region,

$$f_2' = \sqrt{(2^{1/n} - 1)} f_2$$

A decrease in bandwidth is not always associated with an increase in the number of stages if the midband gain can remain fixed and independent of the number of stages.

OBJECTIVE QUESTIONS SET - A

- Generally, the gain of a transistor amplifier falls at high frequencies due to the
 - internal capacitance of the device
 - coupling capacitor at the input
 - skin effect
 - coupling capacitor at the output
- The current gain of a bipolar transistor drops at high frequencies because of
 - transistor capacitances
 - high current effects in the base
 - parasitic inductive elements
 - the Early effect
- A multistage amplifier has a low pass response with three real poles at $s = -\omega_1, -\omega_2$ and $-\omega_3$. The approximate overall bandwidth 'B' of the amplifier will be given by
 - $B = \omega_1 + \omega_2 + \omega_3$
 - $1/B = 1/\omega_1 + 1/\omega_2 + 1/\omega_3$
 - $B = (\omega_1 + \omega_2 + \omega_3)^{1/3}$
 - $B = \sqrt{\omega_1^2 + \omega_2^2 + \omega_3^2}$
- Which of the following components control the low frequency of the RC coupled amplifier?
 - wiring capacitance
 - parasitic capacitance of transistor
 - coupling capacitors
 - emitter bypass capacitance

select the correct answer using the codes given below:


 - 1 and 2
 - 2 and 3
 - 3 and 4
 - 1, 2 and 4
- The CE current gain – bandwidth product of a transistor (f_T) is defined as the frequency at which
 - Alpha of the transistor falls by 3 dB
 - Beta of the transistor falls by 3dB
 - Beta of the transistor falls to unity
 - Power gain of the transistor falls to unity
- Consider the following statements in respect of the transistor R-C coupled amplifier:
 - The low frequency response is determined by the transistor junction capacitors.
 - The high frequency response is limited by coupling capacitors
 - The Miller capacitance reduces the gain at high frequencies
 - As the gain is increased the bandwidth gets reduced.

Which of these statements are correct?

 - 1 and 2
 - 2 and 3
 - 3 and 4
 - 1 and 4

SET - B

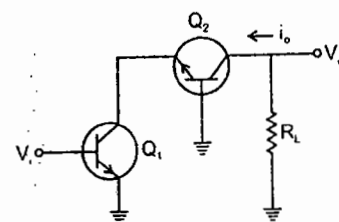01. In the cascode amplifier shown in the figure, if the common – emitter stage (Q_1) has a transconductance g_{m1} , and the common base stage (Q_2) has a transconductance g_{m2} , then the overall transconductance of the cascode amplifier is



- (A) g_{m1} (B) g_{m2} (C) $\frac{G_{m1}}{2}$ (D) $\frac{G_{m2}}{2}$

02. An npn transistor (with $C = 0.3$ pF) has a unity – gain cutoff frequency f_T of 400 MHz at a dc bias current $I_C = 1$ mA. The value of its C_μ (in pF) is approximately ($V_T = 26$ mV)

- (A) 15 (B) 30 (C) 50 (D) 96

03. An amplifier is assumed to have a single-pole high-frequency transfer function. The rise time of its output response to a step function input is 35 nsec. The upper -3 dB frequency (in MHz) for the amplifier to a sinusoidal input is approximately

- (A) 4.55 (B) 10 (C) 20 (D) 28.6

04. The current gain of the bipolar transistor drops at high frequencies because of
(A) transistor capacitances
(B) high current effects in the base
(C) parasitic inductive elements
(D) the Early effect

05. The current gain of BJT is
(A) $g_m r_o$ (B) $\frac{g_m}{r_o}$
(C) $g_m r_\pi$ (D) $\frac{g_m}{r_\pi}$

06. An npn BJT has $g_m = 38$ mA/V, $C_\mu = 10^{-14}$ F, $C_\pi = 4 \times 10^{-13}$ F, and DC current gain $\beta_0 = 90$. For this transistor f_T and f_β are

- (A) $f_T = 1.64 \times 10^8$ Hz and $f_\beta = 1.47 \times 10^{10}$ Hz

- (B) $f_T = 1.47 \times 10^{10}$ Hz and

$$f_\beta = 1.64 \times 10^8 \text{ Hz}$$






- (C) $f_T = 1.33 \times 10^{12}$ Hz and

$$f_\beta = 1.47 \times 10^{10} \text{ Hz}$$

- (D) $f_T = 1.47 \times 10^{10}$ Hz and

$$f_\beta = 1.33 \times 10^{12} \text{ Hz}$$

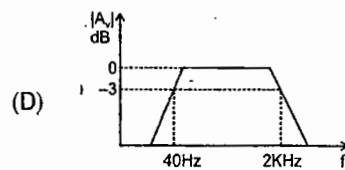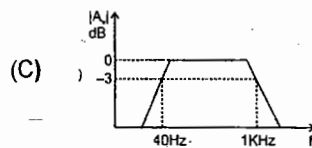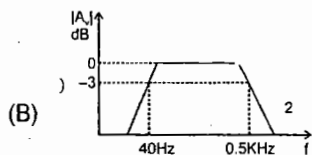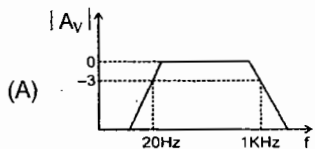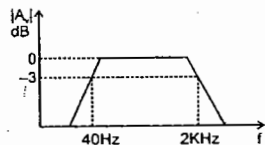07. Three identical RC – coupled transistor amplifiers are cascaded. If each of the amplifiers has a frequency response as shown in the figure, the overall frequency response is as given in



08. Generally, the gain of a transistor amplifier falls at high frequencies due to the
- (A) internal capacitances of the device
- (B) coupling capacitor at the input
- (C) skin effect
- (D) coupling capacitor at the output

09. Three identical amplifiers with each one having a voltage gain of 50, input resistance of 1 K Ω and output resistance of 250 Ω , are cascaded. The open circuit voltage gain of the combined amplifier is
- (A) 49 dB (B) 51 dB
- (C) 98 dB (D) 102 dB

10. A bipolar transistor is operating in the active region with a collector current of 1mA. Assuming that the β of the transistor is 100 and the thermal voltage (V_T) is 25mV, the transconductance (g_m) and the input resistance (r_π) of the transistor in the common emitter configuration, are
- (A) $g_m = 25\text{mA/V}$ and $r_\pi = 15.625\text{ k}\Omega$
- (B) $g_m = 40\text{mA/V}$ and $r_\pi = 4.0\text{ k}\Omega$
- (C) $g_m = 25\text{mA/V}$ and $r_\pi = 2.5\text{ k}\Omega$
- (D) $g_m = 40\text{mA/V}$ and $r_\pi = 2.5\text{ k}\Omega$

11. The cascode amplifier is a two stage configuration of
- (A) CC – CB (B) CE – CB
- (C) CB – CC (D) CE – CC



KEY: SET B

- (1) A (2) A (3) B (4) A (5) C
- (6) B (7) A (8) A (9) C (10) D
- (11) B


Chapter: 5

OPERATIONAL AMPLIFIER AND APPLICATIONS

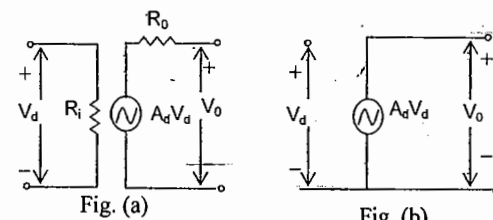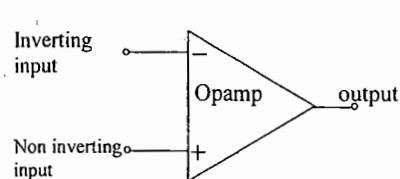An operation amplifier is a very high gain amplifier having very high input impedance and low output impedance. The basic circuit is made using a difference amplifier having two inputs (plus and minus) and at least one output.



A plus (+) input produces an output that is in phase with the signal applied, while an input to the minus(-) input results in an opposite polarity output. The ac equivalent circuit of the op-amp is shown. The signal applied between input terminals sees an input impedance, R_i , typically very high. The output voltage is shown to be the amplifier gain times the input signal taken through the output impedance, R_o , which is typically very low. An ideal op amp circuit would have infinite input impedance, zero output impedance, and an infinite voltage gain.

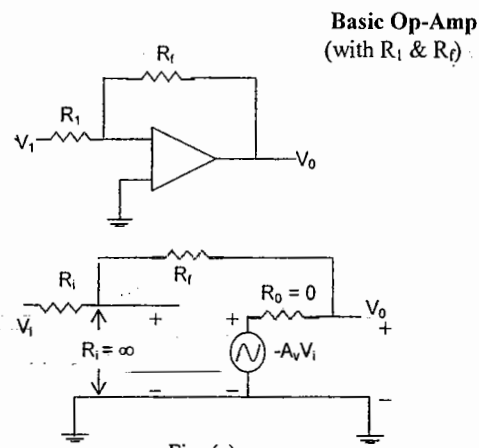

The circuit shown provides operation as a constant-gain multiplier. An input signal, V_i , is applied through resistor R_i to the minus input. The output is then connected back to the same minus input through resistor R_f . The plus input is connected to ground. Since the signal V_i is essentially applied to the minus input, the resulting output is opposite in phase to the input signal. If we use the ideal op-amp equivalent circuit, replacing R_i by an infinite resistance and R_o by zero resistance, the ac equivalent circuit is shown in fig(b). The circuit is then redrawn, from which circuit analysis is carried out.

$$V_i = \frac{R_f}{R_f + (1 + A_v)R_i} V_i \quad \text{If } A_v \gg 1 \text{ and } A_v R_i \gg R_f, \text{ as is usually true, then } V_i = \frac{R_f}{A_v R_i} V_i$$

$$V_o = -A_v V_i \cdot \frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

Unity gain: If $R_f = R_1$, $V_0 / V_1 = -1$, so that the circuit provides a unity voltage gain with 180° phase inversion.

Constant Magnitude Gain: If R_f is some multiple of R_1 , the overall amplifier gain is a constant. If we select, precise resistor values for R_f and R_1 , we can obtain a wide range of gains, the gain being as accurate as the resistors used and is only slightly affected by temperature and other circuit factors.

Virtual Ground: The fact that $V_i \approx 0V$ leads to the concept that at the amplifier input there exists a virtual short circuit or virtual ground. The concept of a virtual short implies that although the voltage is nearly $0V$, there is no current through the amplifier input to ground. Current only goes through resistors R_1 and R_f .

Differential and common mode operation

One of the important features of a differential circuit connection, as provided in an op-amp, is the circuit's ability to greatly amplify signals that are opposite at the two inputs, while only slightly amplifying signals that are common to both inputs.

Differential Inputs: when separate inputs are applied to the op-amp, the resulting difference signal is the difference between the two inputs.

$$V_d = V_{i1} - V_{i2}$$

Common Inputs: When both input signals are the same a common signal element due to the two inputs can be defined as the average of the sum of the two signals.

$$V_c = 1/2 (V_{i1} + V_{i2})$$

Output Voltage: Since any signals applied to an op-amp in general have both in-phase and out of phase components, the resulting output can be expressed as

$$V_0 = A_d V_d + A_c V_c$$

Where

V_d = difference voltage

V_c = common voltage

A_d = differential gain of the amplifier

A_c = common-mode gain of the amplifier

Opposite polarity inputs: If opposite polarity inputs applied to an op-amp are ideally opposite signals,

$$V_{i1} = -V_{i2} = V_s, \quad V_d = V_{i1} - V_{i2} = V_s - (-V_s) = 2V_s$$

$$V_c = 1/2 (V_{i1} + V_{i2}) = 1/2 [V_s + (-V_s)] = 0$$

$$V_0 = A_d V_d + A_c V_c = A_d (2V_s) + 0 = 2A_d V_s$$

This shows that when the inputs are ideal opposite signals (no common element), the output is the differential gain times twice the input signal applied to one of the inputs.

Same Polarity Inputs: If the same polarity inputs are applied to an op-amp, $V_{i1} = V_{i2} = V_s$, $V_d = V_{i1} - V_{i2} = V_s - V_s = 0$, $V_c = 1/2 (V_{i1} + V_{i2}) = 1/2 (V_s + V_s) = V_s$

$$V_0 = A_d V_d + A_c V_c = A_d (0) + A_c V_s = A_c V_s$$

This shows that when the inputs are ideal in-phase signals (no difference signal), the output is the common-mode gain times the input signal, V_s , which shows that only common-mode operation, occurs.

Common-Mode Rejection Ratio: $CMRR = \frac{A_d}{A_c}$, $CMRR (\log) = 20 \log_{10} \frac{A_d}{A_c}$

It should be clear that the desired operation will have A_d very large with A_c very small. That is, the signal components of opposite polarity will appear greatly amplified at the output, whereas the signal components that are in phase will mostly cancel out so that the common mode gain, A_c , is very small. Ideally, the value of the CMRR is infinite. Practically, the larger the value of CMRR, the better the circuit operation.


$$V_0 = A_d V_d + A_c V_c = A_d V_d \left(1 + \frac{A_c V_c}{A_d V_d} \right) = A_d V_d \left(1 + \frac{1}{CMRR} \frac{V_c}{V_d} \right)$$

PRACTICAL OP-AMP CIRCUITS

Inverting Amplifier:

The output is obtained by multiplying the input by a fixed or constant gain, set by the input resistor (R_1) and feedback resistor (R_f) – this output also being inverted from the input.

$$v_0 = -\frac{R_f}{R_1} v_s$$

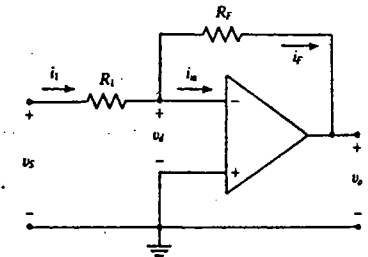


Non-inverting Amplifier:

It should be noted that the inverting amplifier connection is more widely used because it has better frequency stability.

$$v_1 = \frac{R_1}{R_1 + R_2} v_0$$
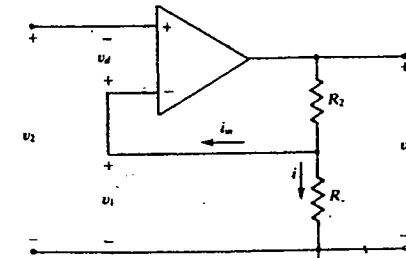
$$\frac{v_0}{v_1} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1}$$




Unity follower :-

The unity-follower circuit, provides a gain of unity(1) with no polarity or phase reversal.

$$V_0 = V_s$$

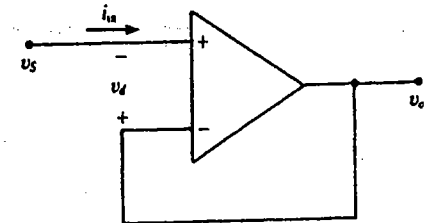
and the output is of the same polarity and magnitude as the input.



Summing Amplifier:


The circuit shows a three-input summing amplifier, which provides a means of algebraically summing (adding) three voltages, each multiplied by a constant-gain factor.
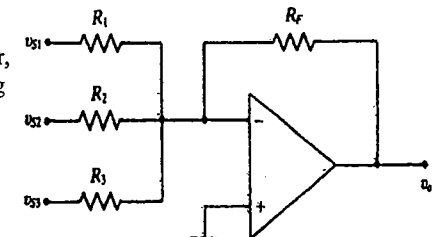
$$v_0 = - \left[\frac{R_f}{R_1} v_{s1} + \frac{R_f}{R_2} v_{s2} + \frac{R_f}{R_3} v_{s3} \right]$$




In other words, each input adds a voltage to the output multiplied by its separate constant-gain multiplier.

Voltage Subtraction:

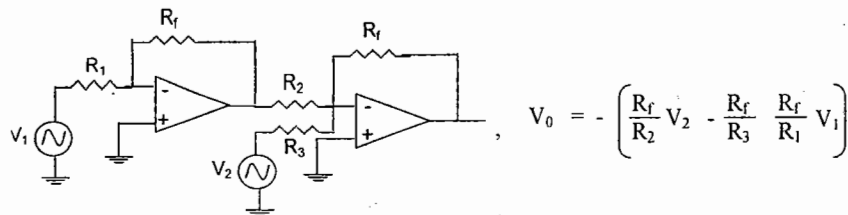

Integrator:

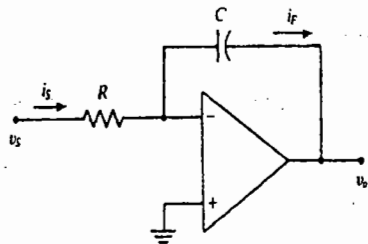If the feedback component used is a capacitor, the resulting connection is called an integrator.



$$X_C = \frac{1}{j\omega C} = \frac{1}{sC}, \quad \frac{V_0}{V_s} = \frac{-1}{sCR}$$


$$v_0(t) = -\frac{1}{RC} \int v_s(t) dt$$

More than one input may be applied to an integrator with the resulting operation given by

$$v_0(t) = - \left[\frac{1}{R_1 C} \int v_1(t) dt + \frac{1}{R_2 C} \int v_2(t) dt + \frac{1}{R_3 C} \int v_3(t) dt \right]$$


Differentiator :

$$v_0(t) = -RC \frac{dv_s}{dt}(t)$$

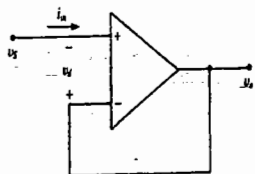

Voltage Buffer:

$$V_0 = V_s$$

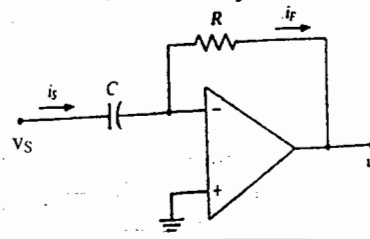


A voltage buffer circuit provides a means of isolating an input signal from a load by using a stage having unity voltage gain, with no phase or polarity inversion, and acting as an ideal circuit with very high input impedance and low output impedance.



ACTIVE FILTERS

A filter circuit can be constructed using passive components: resistors and capacitors. An active filter additionally uses an amplifier to provide voltage amplification and signal isolation or buffering.


A filter that provides a constant output from dc upto a cutoff frequency f_{OH} and then passes no signal above that frequency is called an ideal low-pass filter. A filter that provides or passes signals above a cut off frequency f_{OL} is a high pass filter. When the filter circuit passes signals that are above one ideal cut off frequency and below a second cut off frequency, it is called a band pass filter.

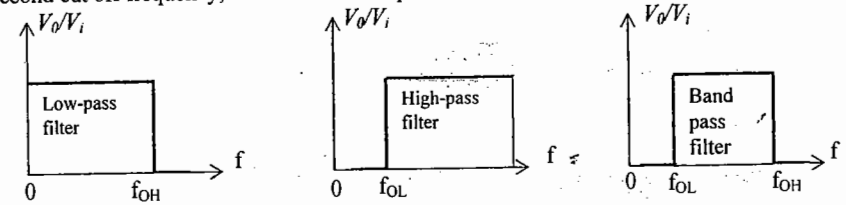

Low pass filter:

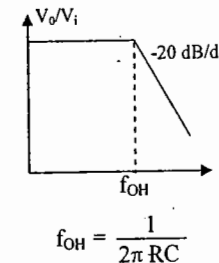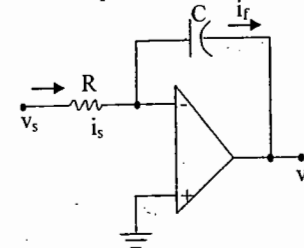


High Pass filter:

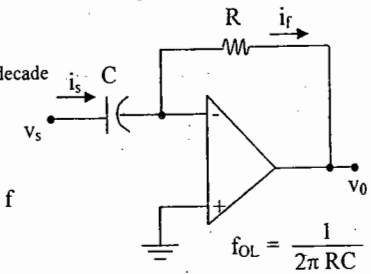

$$f_{OL} = \frac{1}{2\pi RC}$$

Band pass filter:

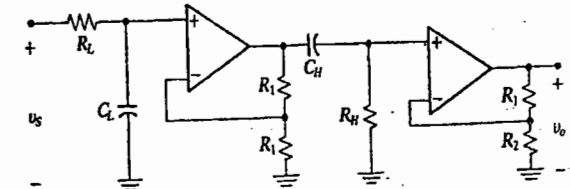

The figure shows a band pass filter using two stages, the first a high pass filter and the second a low pass filter, the combined operation being the desired band pass response.

$$f_{OL} = \frac{1}{2\pi R_L C_L} \quad f_{OH} = \frac{1}{2\pi R_H C_H}$$


OP AMP SPECIFICATIONS

Offset currents and Voltages: While the Op-amp output should be 0V when the input is 0V, in actual operation there is some offset voltage at the output.

The output offset voltage can be affected by two separate circuit conditions. These are : 1) an input offset voltage, V_{IO} and 2) an offset current due to the difference in currents resulting at the plus (+) and minus(-) inputs.

$$V_{0(\text{offset})} = V_{IO} \frac{R_i + R_f}{R_i}$$

$$V_{0(\text{offset})} = I_{IO} R_f$$

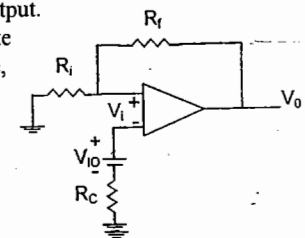


Input Bias current, I_{IB} :

A parameter related to I_{IO} and the separate input bias currents I_{IB}^+ and I_{IB}^- is the average bias current defined as

$$I_{IB} = \frac{I_{IB}^+ + I_{IB}^-}{2}, \quad I_{IB}^+ > I_{IB}^-, \quad I_{IB}^+ = I_{IB} + \frac{I_{IO}}{2}, \quad I_{IB}^- = I_{IB} - \frac{I_{IO}}{2}$$

Gain Band width: Because of the internal compensation circuits included in an op amp, the voltage gain drops off as frequency increases.

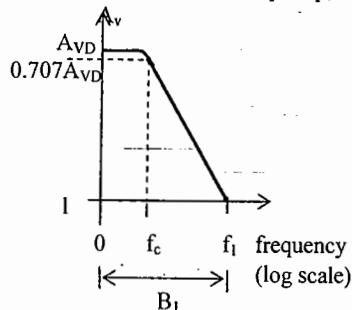A frequency of interest is where the gain drops by 3dB, this being the cutoff frequency of the op-amp, f_c . The unity gain frequency f_1 and cutoff frequency are related by $f_1 = A_{VD}f_c = \text{gain} \times \text{BW}$ where A_{VD} is differential voltage gain. Slew Rate, SR is maximum rate at which amplifier output can change in volts per μs .



$$SR = \frac{\Delta V_0}{\Delta t} \text{ V}/\mu\text{s}$$

Maximum Signal Frequency: Let $V_0 = K \sin 2\pi ft$

The maximum voltage rate of change can be shown to be signal maximum rate of change = $2\pi fK \text{ V/s}$. To prevent distortion at the output the rate of change must also be less than the slew rate, i.e.,


$$2\pi fK \leq SR \quad \omega \leq \frac{SR}{K} \text{ rad/sec}$$

OBJECTIVES SET - A

1. An ideal OPAMP is used to make an inverting amplifier. The two input terminals of the OPAMP are at the same potential because
 - a) the two input terminals are directly shorted internally
 - b) the input impedance of the OPAMP is infinity
 - c) the open loop gain of the OPAMP is infinity
 - d) CMRR is infinity

2. An analog comparator is a high-gain amplifier whose output is always either positive or in negative saturation. TRUE / FALSE

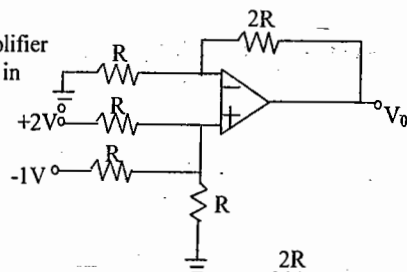
3. Figure shows a non inverting op-amp summer. $V_0 = \dots\dots\dots$



5. A non inverting op-Amp is shown. V_0 is equal to


- a) $(3/2) \sin(100t)$
- b) $3 \sin(100t)$
- c) $2 \sin(100t)$
- d) None of the above

$$v = (2 + \sin 100t) \text{ V}$$

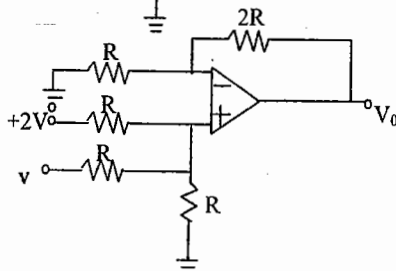


6. Let the magnitude of the gain in the inverting OP-Amp amplifier circuit shown in fig be x with switch S open. When the switch S is closed, the magnitude of gain becomes

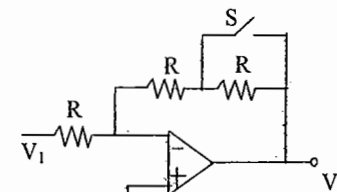- (a) $x/2$
- (b) $-x$
- (c) $2x$
- (d) $-2x$



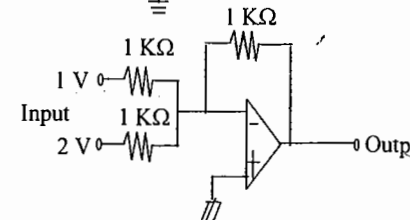8. The circuit shown in figure acts as a _____. For the given inputs, its output voltage is ____.



9. An op-amp has an open loop gain of 10^5 and an open loop upper cutoff frequency of 10Hz. If this op-amp is connected as an amplifier with a closed loop gain of 100, then the new upper cutoff frequency is


- a) 10 HZ
- b) 100 HZ
- c) 10 KHZ
- d) 100 KHZ

10. An op-amp, having a slew rate of $62.8 \text{ V}/\mu\text{sec}$, is connected in a voltage follower configuration. If the maximum amplitude of the input sinusoidal is 10V, then the minimum frequency at which the slew rate limited distortion would set in at the output is

- a) 1.0 MHz
- b) 6.28 MHz
- c) 10.0 MHz
- d) 62.8 MHz.


11. For the circuit of figure with an ideal operational amplifier, the maximum phase shift of the output V_{out} with reference to the input V_{in} is

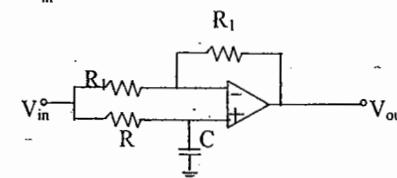- a) 0°
- b) -90°
- c) $+90^\circ$
- d) $\pm 180^\circ$




12. Assuming the op-Amp to be ideal, the gain V_{out} / V_{in} in the circuit shown is

- a) -1
- b) -20
- c) -100
- d) -120

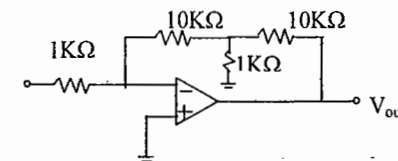


13. In the active filter circuit shown if $Q=1$, a pair of poles will be realized with ω_0 equal to

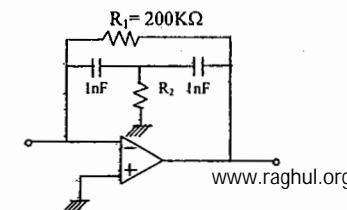- a) 1000 rad/s
- b) 100 rad/s
- c) 10 rad/s
- d) 1 rad/s



14. The input resistance R_{IN} ($=V_X/I_X$) of the circuit is-

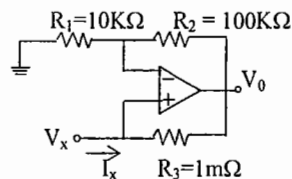- a) +100 K Ω
 b) -100 K Ω
 c) +1 M Ω
 d) -1M Ω




15. If the differential voltage gain and the common mode voltage gain of a differential amplifier are 48dB and 2dB respectively, then its common mode rejection ratio is -
 a) 23 dB b) 25 dB c) 46 dB d) 50 dB

16. A 741-type op-Amp has a gain-band width product of 1MHz. A non inverting amplifier using this op-Amp and having a voltage gain of 20dB will exhibit a -3dB bandwidth of
 a) 50 KHz b) 100 KHz c) 1000/17 KHz d) 1000/7.07 KHz

17. An amplifier using an op Amp with a slew rate $SR = 1$ V/ μ sec has a gain of 40 dB. If this amplifier has to faithfully amplify sinusoidal signals from dc to 20 KHz without introducing any slew rate induced distortion, then the input signal level must not exceed
 a) 795 mV b) 395 mV c) 79.5 mV d) 39.5 mV


18. If the op - amp is ideal, then V_0 is

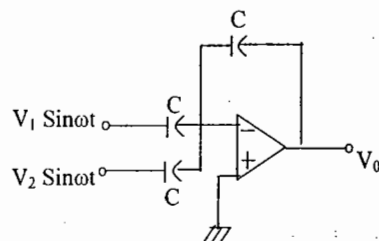- a) zero
 b) $(V_1 - V_2) \sin \omega t$
 c) $-(V_1 + V_2) \sin \omega t$
 d) $(V_1 + V_2) \sin \omega t$



19. Assume that the op - amp is ideal. If V_i is a triangular wave, the V_0 will be

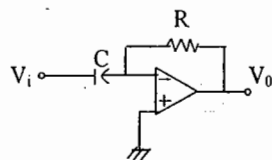- a) square wave
 b) triangular wave
 c) parabolic wave
 d) sine wave



KEY:

1. c, d 2. true 3. 1V 4. V_0 5. b 6. c 7. c 8. summer, -3V
 9. c 10. a 11. d 12. d 13. a 14. b 15. c 16. b 17. c 18. c 19. a

SET - B


01. In a single-stage differential amplifier, the output offset voltage is basically dependent on the mismatch of

- (a) V_{BE} , I_B and β (b) V_{BE} and I_B
 (c) I_B and β (d) V_{BE} and β

02. A second -order band-pass active filter can be obtained by cascading a low-pass second order section having cutoff frequency f_{OH} with a high-pass second- order section having cut off frequency f_{OL} , provided


- (a) $f_{OH} > f_{OL}$ (b) $f_{OH} < f_{OL}$
 (c) $f_{OH} = f_{OL}$ (d) $f_{OH} \leq f_{OL}$

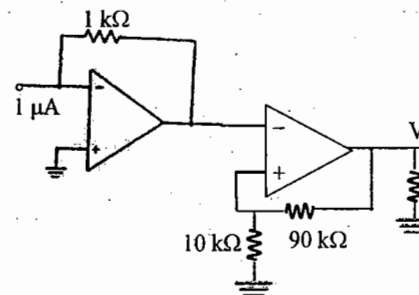03. The output voltage V_0 of the given circuit is



- (a) -100 V (b) -100 mV
 (c) 10 V (d) -10 mV

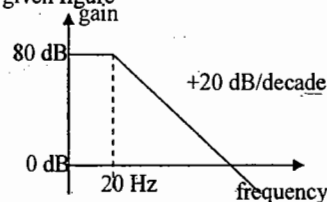
04. The voltage gain verses frequency curve of an Op-Amp is shown in the given figure



The gain-bandwidth product of the Op-Amp is

- (a) 200 Hz (b) 200 MHz
 (c) 200 kHz (d) 2 MHz

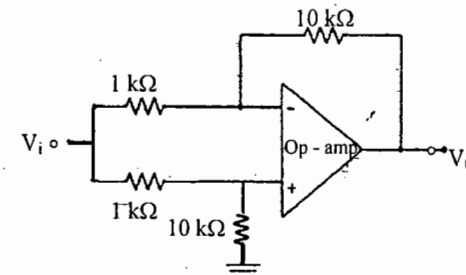05. The V_0 of the Op-Amp circuit shown in the given figure is



- (a) $11 \cdot V_i$ (b) $10 \cdot V_i$
 (c) V_i (d) 0

06. Consider the following statements:
 A totem pole configuration used in the output stage of an Op-Amp has the advantage of using

1. only n-p-n BJTs
 2. complimentary symmetrical pair of transistors
 3. only one transistor


Which of these statements is/ are correct?

- (a) 1 alone (b) 2 alone
 (c) 3 alone (d) 1 and 3

07. A 1 ms pulse can be stretched to 1 Sec pulse by using


- (a) an astable multivibrator
 (b) a monostable multivibrator
 (c) a bistable multivibrator
 (d) a Schmitt trigger circuit

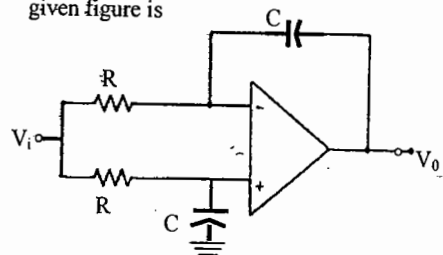08. The Op-Amp circuit shown in the given figure is



- (a) a high-pass circuit
- (b) a low-pass circuit
- (c) a band-pass circuit
- (d) an all-pass circuit

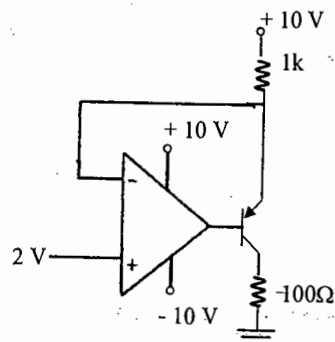09. In the circuit shown in the given figure, the current flowing through resistance of $100\ \Omega$ would be



- (a) 8 mA
- (b) 10 mA
- (c) 20 mA
- (d) 100 mA

10. In a 741 Op-Amp, there is 20 dB/decade fall-off starting at a relatively low frequency. This is due to the

- (a) applied load
- (b) internal compensation
- (c) impedance of the source
- (d) power dissipation in the chip

© Wiki Engineering

11. The input differential stage Op-Amp 741 is biased at about $10\ \mu\text{A}$ current. Such a low current of the input stage gives

- (a) high CMRR
- (b) high differential gain
- (c) low differential gain
- (d) high input impedance

Which of these are correct?

- (a) 1 and 2
- (b) 1, 2 and 4
- (c) 3 and 4
- (d) 1, 2, 3 and 4

12. In a circuit, if the open loop gain is 10^6 and output voltage is 10 volt, the differential voltage should be

- (a) $10\ \mu\text{V}$
- (b) $0.1\ \text{V}$
- (c) $100\ \mu\text{V}$
- (d) $1\ \mu\text{V}$

13. An operational amplifier possesses

- (a) very large input resistance and very large output resistance
- (b) very small input resistance and very small output resistance
- (c) very large input resistance and very small output resistance
- (d) very small input resistance and very output

14. Consider the following statements:


In order to generate square wave from a sinusoidal input signal one can use

1. Schmitt trigger circuit
2. Clippers and amplifiers
3. Monostable multivibrators

Which of the above statements is/are correct?

- (a) 1 along
- (b) 1 and 2
- (c) 2 and 3
- (d) 1, 2 and 3

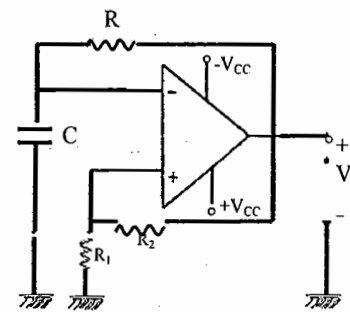15. An op-amp circuit is shown in the figure
The output V_o will be (assume ideal op-amp)



(a) equal to zero because the input is zero


(b) dependent on element values, hence nothing can be predicted without a knowledge of element values

(c) a square wave varying between $+V_{CC}$ and $-V_{CC}$

(d) a sinusoidal wave of amplifier V_{CC}

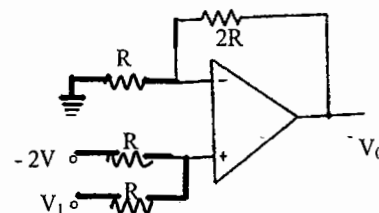16. A non-inverting op-amp is shown (assume ideal op-amp)

The output voltage V_o , for an input $V_i = [2 + \sin(100t)]\text{V}$ is



$$V_i = [2 + \sin(100t)]$$

- (a) $\frac{3}{2} \sin(100t)$
- (b) $3 \sin(100t)$
- (c) $2 \sin(100t)$
- (d) $3 \sin(100t) + \frac{1}{2}$

17. Match List-I (Circuit Name) with List-II (Characteristics) and select the correct answer using the codes given below the lists:

List-I

- A. Schmitt trigger
- B. Monostable multivibrator
- C. Astable multivibrator
- D. Blocking oscillator

List-II

1. It needs a pulse transformer
2. it is used to generate gating pulse whose width can be controlled
3. it is bistable circuit
4. it has no stable state


Codes:

	A	B	C	D
(a)	3	2	4	1
(b)	2	3	1	4
(c)	3	2	1	4
(d)	2	3	4	1

18. A triangular – square wave generator uses

- (a) A sine wave oscillator and a comparator
- (b) An integrator and a comparator
- (c) A differentiator and a comparator
- (d) A sine wave oscillator and a clipper

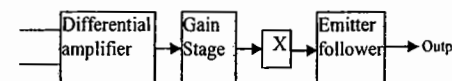
19. The stage marked X in the architecture of a two-stage op-amp is



- (a) Direct coupled amplifier
- (b) Buffer amplifier
- (c) Level shifter
- (d) Blocking oscillator


www.rghd.org

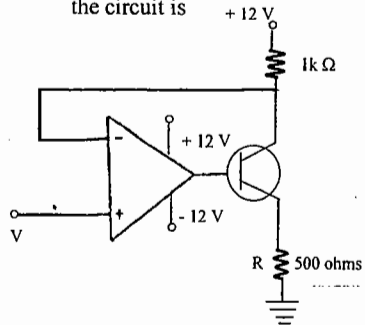20. The current through the resistor R in the circuit is




- (a) 1 mA (b) 4 mA
(c) 8 mA (d) 10 mA

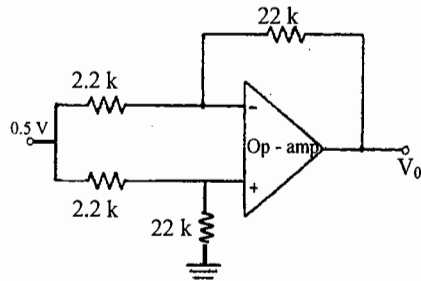21. In the op-amp circuit shown (assuming ideal op-amp), V_0 is



- (a) $V_0 = -5V$ (b) $V_0 = +5V$
(c) $V_0 = 0$ (d) $V_0 = -2V$


22. Consider the following circuit:

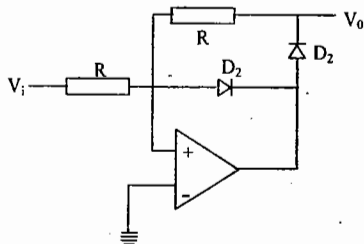

What is the function of diode D_2 in the above circuit?

- (a) To avoid saturation of the Op-Amp
(b) To provide negative feedback when the input is negative
(c) To reduce reverse breakdown voltage of D_1
(d) As a buffer


23. Consider the following circuit:

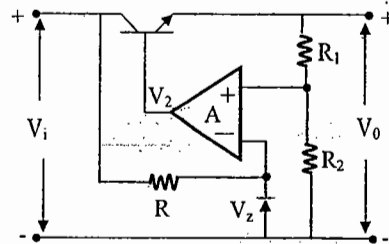

Which one of the following expressions for V_0 is correct?


- (a) $V_0 = V_Z$ (b) $V_0 = AV_Z$
(c) $V_0 = AV_Z$ (d) $V_0 = -AV_Z$

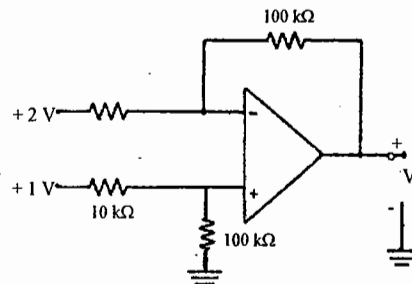24. Consider the following Op-Amp circuit: V_0 is equal to



- (a) +10 V (b) -10 V
(c) +11 V (d) -11 V


25. Consider the following circuit:

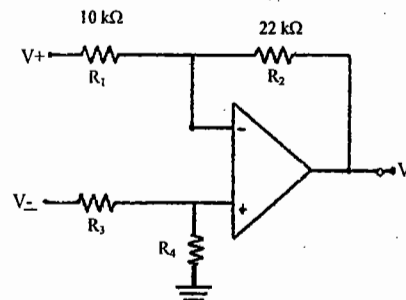

What is the value of R_4 in the above circuit, if the voltage V_- and V_+ are to be amplified by the same amplification factor?


- (a) 7 kΩ (b) 22 kΩ
(c) 33 kΩ (d) 35 kΩ

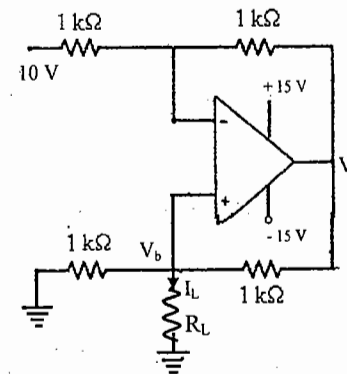26. The load current I_L in the circuit shown is



- (a) -5 mA (b) -10 mA
(c) +25 mA (d) +50 mA


27. Consider the following circuit:

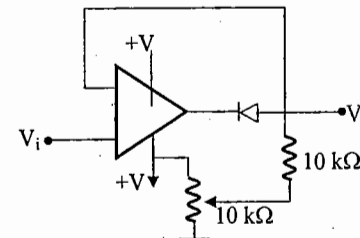

The above circuit works

- (a) As a logarithmic amplifier
(b) As a negative clipper
(c) As a positive clipper
(d) As a half-wave rectifier

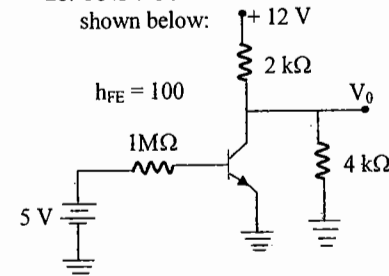28. Consider the NPN transistor circuit shown below:




The output voltage V_0 in the circuit is

- (a) 0 V (b) 12 V
(c) 9 V (d) 5 V

29. Pulses of definite width can be obtained from regular shaped pulses:

- (a) when it is given as input to a monostable multivibrator
(b) when it is given as triggering signal to a bistable multivibrator
(c) when it is used as input to a Schmitt trigger
(d) when it is used as input to a pulse transformer

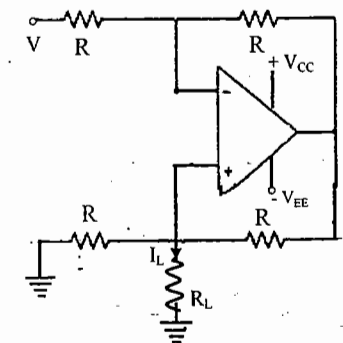30. For the circuit given below, what is I_L equal to?




- (a) V/R_L (b) V/R
(c) $V/(R+R_L)$ (d) $V/(2R+R_L)$

31. For a given op-amp, $CMRR=10^5$ and differential gain = 10^5 . What is the common mode gain of the op-amp?

- (a) 10^{10} (b) 2×10^{10}
(c) 10^5 (d) 1

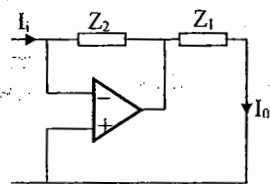32. In the circuit shown the transfer function I_0/I_i is



- (a) $-Z_2/Z_1$ (b) $-Z_1/Z_2$
(c) $1 + (Z_2/Z_1)$ (d) $1 + (Z_1/Z_2)$

33. Narrow pulses with adjustable mark to space ratio can be obtained from square wave input signal by using

1. Schmitt trigger
2. Monostable multivibrator
3. Clippers


Select the correct answer using the code given below:

- (a) only 1 (b) only 2
(c) 1 and 2 (d) 2 and 3

34. A differential amplifier has inputs, $V_1 = 1050 \mu V$ and $V_2 = 950 \mu V$ with $CMRR = 1000$. The error in the differential output is


- (a) 10% (b) 1%
(c) 0.1% (d) 0.01%

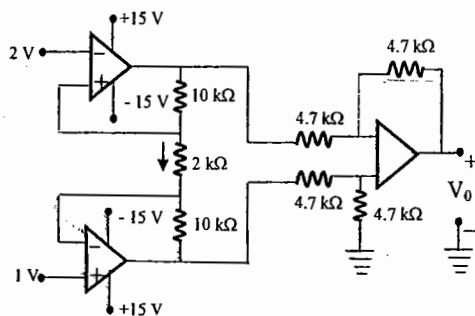35. The output voltage V_o of the circuit is




- (a) -11 V (b) 6 V (c) 11 V (d) -6 V

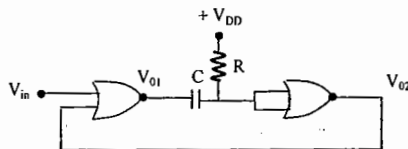36. The figure given shows the circuit of



- (a) Bi-Stable multivibrator
(b) Schmitt trigger
(c) Monostable multivibrator
(d) Astable multivibrator

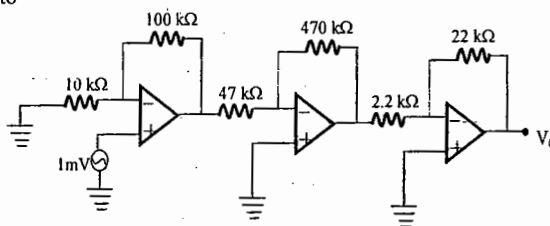37. The output voltage V_o of the below circuit is



- (a) -1.1 V (b) +1.1 V
(c) 1.0 V (d) 10 V

38. Consider the following statements:
Dominant-pole frequency compensation in an OP-AMP

1. Increases the slow-rate of the OP-AMP
2. increases the stability of the OP-AMP
3. reduces the bandwidth of the OP-AMP
4. reduces the CMRR of the OP-AMP

Which of the statements given above are correct?

- (a) 1 and 3 only (b) 1, 2 and 4
(c) 1 and 2 only (d) 2 and 3 only


KEY: SET B

- | | | | | | |
|--------|--------|--------|--------|--------|--------|
| (01) C | (02) A | (03) D | (04) C | (05) D | (06) A |
| (07) B | (08) B | (09) A | (10) B | (11) B | (12) A |
| (13) B | (14) A | (15) A | (16) A | (17) A | (18) B |
| (19) C | (20) D | (21) C | (22) B | (23) C | (24) B |
| (25) C | (26) B | (27) C | (28) A | (29) C | (30) B |
| (31) D | (32) A | (33) B | (34) B | (35) A | (36) C |
| (37) B | (38) C | | | | |

Sample and Hold Circuit, Schmitt Trigger & Multivibrators

SAMPLE AND HOLD CIRCUIT →

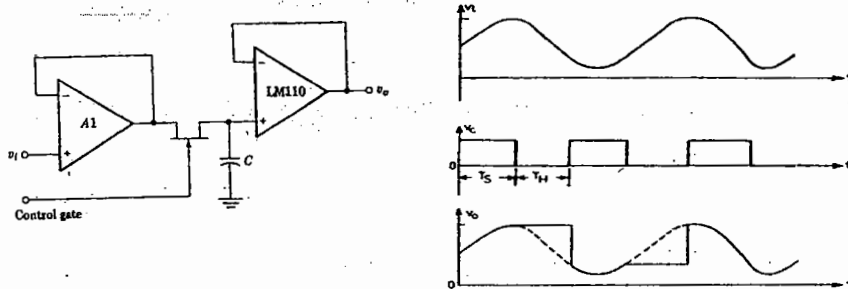A sample and hold circuit samples an input signal and holds on to its last sampled value until the input is sampled again.




The n-channel E-MOSFET works as a switch and is controlled by the control voltage V_C and the capacitor C stores the charge. The analog signal V_i to be sampled is applied to the drain of E-MOSFET and the control voltage v_i is applied to its gate. When v_i is positive, the E-MOSFET turns on and the capacitor C charges to the instantaneous value of input v_i with a time constant $[(R_0 + r_{DS(on)})C]$. Here R_0 is the output resistance of the voltage follower A_1 and $r_{DS(on)}$ is the resistance of the MOSFET when on. Thus the input voltage v_i appears across the capacitor C and then at the output through the voltage follower A_2 . During the time when control voltage v_i is zero, the E-MOSFET is off. The capacitor C is now facing the high input impedance of the voltage follower A_2 and hence cannot discharge. The capacitor holds the voltage across it. The time period T_S , the time during which voltage across the capacitor is equal to input voltage is called sample period. The time period T_H of v_o during which the voltage across the capacitor is held constant is called hold period. The frequency of the control voltage should be kept higher than (at least twice) the input so as to retrieve the input from output wave form.


SCHMITT TRIGGER →

This is also known as regenerative comparator. The input voltage is applied to the (-) input terminal and feed back voltage to the (+) input terminal. The input voltage v_i triggers the output v_o every time it exceeds certain voltage levels. These voltage levels are called upper threshold voltage (V_{UT}) and lower threshold voltage (V_{LT}). The hysteresis width is the difference between these two threshold voltages (i.e.,) $V_{UT} - V_{LT}$. These threshold voltages are calculated as follows. Suppose the output $v_o = +V_{sat}$. The voltage at (+) input

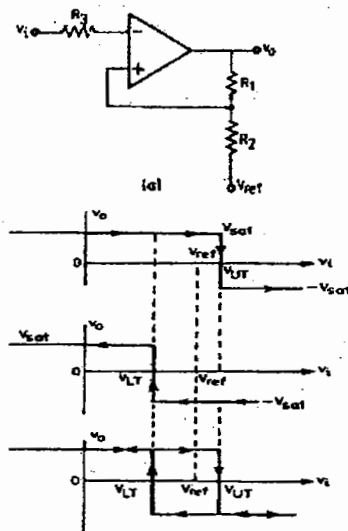terminal will be $V_{ref} + \frac{R_2}{R_1 + R_2} (V_{sat} - V_{ref}) = V_{UT}$



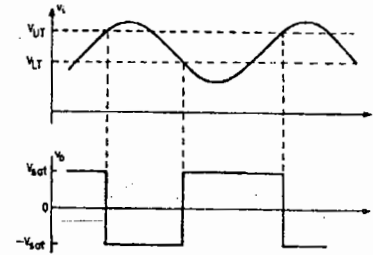As long as V_i is less than V_{UT} , the output v_o remains constant at $+V_{sat}$. When v_i is just greater than V_{UT} , the output regeneratively switches to $-V_{sat}$ and remains at this level as long as $v_i > V_{UT}$.



For $v_o = -V_{sat}$, the voltage at the (+) input terminal is,

$$V_{ref} - \frac{R_2 (V_{sat} + V_{ref})}{R_1 + R_2} = V_{LT}$$

The input voltage V_i must become lesser than V_{LT} in order to cause v_o to switch from $-V_{sat}$ to $+V_{sat}$. A regenerator transition takes place and the output v_o returns from $-V_{sat}$ to $+V_{sat}$ almost instantaneously.

The most important application of schmitt trigger circuit is to convert a very slowly varying input voltage into a square wave output.


If in the circuit, V_{ref} is chosen as zero volt,

$$V_{UT} = -V_{LT} = \frac{R_2 V_{sat}}{R_1 + R_2}$$

If an input sinusoid of frequency $f = 1/T$ is applied to such a comparator, a symmetrical square wave is obtained at the output.

MULTIVIBRATORS →

Astable Multivibrator

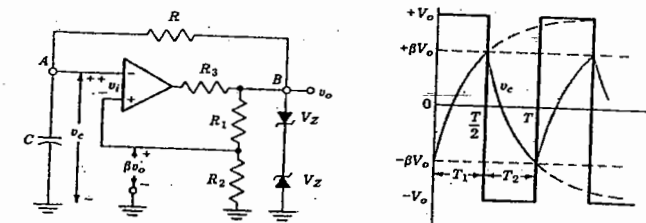

A simple op-amp square wave generator, also called a free running oscillator, the principle of generation of square wave output is to force an op-amp to operate in the saturation region.

A fraction $\beta = \frac{R_2}{R_1 + R_2}$ of the output is fed back to the (+) input terminal. Thus the reference

voltage V_{ref} is βV_0 and may take values as $+\beta V_{sat}$ or $-\beta V_{sat}$. The output is also fed back to the (-) input terminal after integrating by means of a low-pass RC combination. Whenever input at the (-) input terminal just exceeds V_{ref} , switching takes place resulting in a square wave output. In astable multi vibrator, both the states are quasi stable.

The frequency is determined by the time it takes the capacitor to charge from $-\beta V_{sat}$ to $+\beta V_{sat}$ and vice versa.

The voltage across the capacitor as a function of time is

given by, $V_C(t) = V_f + (V_i - V_f) e^{-t/RC}$
Where, the final value, $V_f = +V_{sat}$ and the initial value, $V_i = -\beta V_{sat}$
Therefore,

$$V_C(t) = V_{sat} + (-\beta V_{sat} - V_{sat}) e^{-t/RC}$$

$$\text{Or } V_C(t) = V_{sat} - V_{sat} (1 + \beta) e^{-t/RC}$$

At $t = T_1$, voltage across the capacitor reaches βV_{sat} and switching takes place, therefore,

$$V_C(T_1) = \beta V_{sat} = V_{sat} - V_{sat} (1 + \beta) e^{-T_1/RC}$$

After algebraic manipulation, we get

$$T_1 = RC \ln \frac{(1+\beta)}{(1-\beta)}$$

This gives only one half of the period

Total time period

$$T = 2T_1 = 2RC \ln \frac{(1+\beta)}{(1-\beta)} \text{ and the output waveform is symmetrical.}$$

If $R_1 = R_2$, then $\beta = 0.5$ and $T = 2RC \ln 3$. And for $R_1 = 1.16R_2$. It can be seen that $T = 2RC$.


$$\text{Or } f_0 = \frac{1}{2RC}$$

The output swings from $+V_{sat}$ to $-V_{sat}$, so,

$$v_0 \text{ peak-to-peak} = 2V_{sat}$$

The peak to peak output amplitude can be varied by varying the power supply voltage.

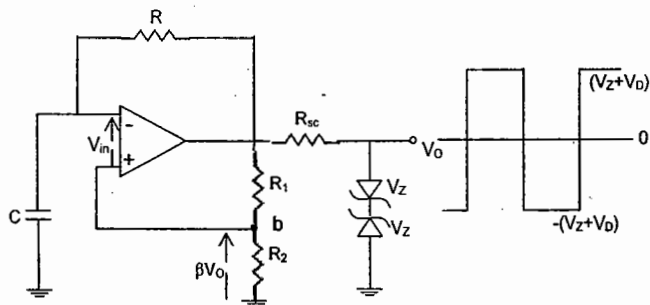However, a better technique is to use back Zener diodes.



The output voltage is regulated to $\pm(v_z + v_0)$ by the zener diodes.

$$v_0 \text{ peak to peak} = (v_z + v_0)$$

$$I_{SC} = \frac{V_{sat} - V_Z}{R_{SC}}$$

If an asymmetric square wave is desired, then zener diodes with different breakdown voltages v_{z1} and v_{z2} may be used.



$$V_{01} = v_{z1} + v_D$$

$$V_{02} = v_{z2} + v_D$$

$$T_1 = RC \ln \frac{1 + \beta (v_{02} / v_{01})}{1 - \beta}$$

An alternative method to get asymmetric square wave output is to add a dc voltage source v in series with R_2 .

MONOSTABLE MULTIVIBRATOR →

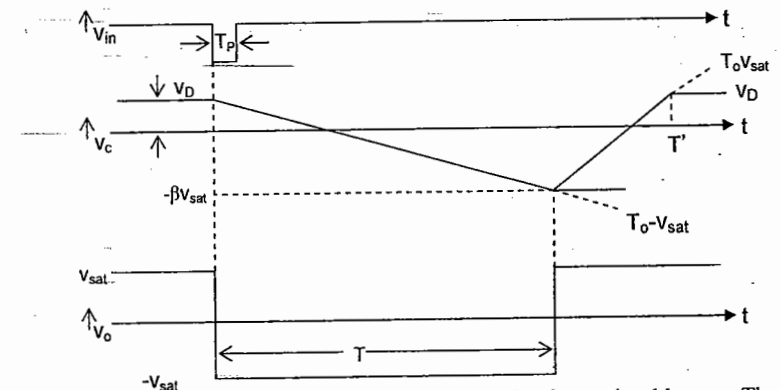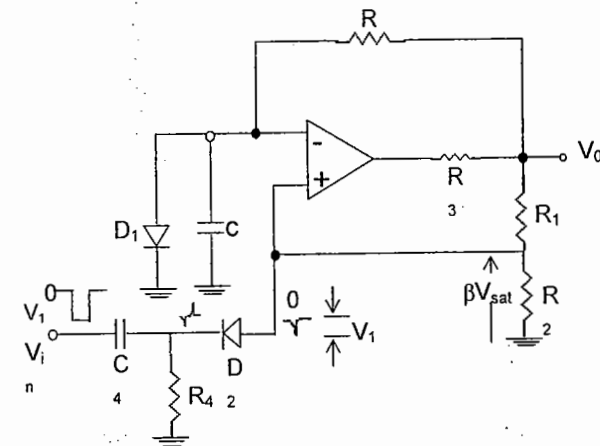

Monostable multivibrator has one stable state and the other is quasi stable state. The circuit is useful for generating single output pulse of adjustable time duration in response to a triggering signal.

A diode D_1 clamps the capacitor voltage to 0.7V when the output is at $+V_{\text{sat}}$. A negative going pulse signal of magnitude v_i passing through the differentiator R_4C_4 and diode D_2 produces a negative going triggering impulse and is applied to the (+) input terminal.

The pulse width T of magnitude multivibrator is calculated as follows :
The general solution for a single time constant low pass RC current with v_i and v_f as initial and final values is, $v_0 = v_f + (v_i - v_f) e^{-t/RC}$

For the circuit, $v_f = -V_{\text{sat}}$ and $v_i = v_D$
The output v_c is,
 $V_c = -V_{\text{sat}} + (v_D + V_{\text{sat}})e^{-t/RC}$
At $t = T$

$v_c = -\beta V_{\text{sat}}$
therefore $-\beta V_{\text{sat}} = -V_{\text{sat}} + (v_D + V_{\text{sat}})e^{-T/RC}$
After simplification, pulse width T is obtained as

$$T = RC \ln \frac{(1 + v_D / V_{\text{sat}})}{1 - \beta}$$

$$\text{where } \beta = \frac{R_2}{R_1 + R_2}$$

If $V_{\text{sat}} \gg v_D$ and $R_1 = R_2$ so that $\beta = 0.5$, then
 $T = 0.69 RC$

For monostable operation, the trigger pulse width T_p should be much less than T , the pulse width of the monostable multivibrator.


The monostable multivibrator circuit is also referred to as time delay circuit as it generates a fast transition at a pre determined time t after the application of input trigger.

OBJECTIVES QUESTIONS-

1. A sample and hold (S/H) circuit, having a holding capacitor of 0.1 nF , is used at the input of an ADC. The conversion time of the ADC is $1\text{ }\mu\text{sec}$, and during this time, the capacitor should not lose more than 0.5% of the charge put across it during the sampling time. The maximum value of the input signal to the S/H circuit is 5V . The leakage current of the S/H circuit should be less than
(GATE'01, EEE)

- a) $2.5\text{ }\mu\text{A}$ b) $0.25\text{ }\mu\text{A}$ c) $25.0\text{ }\mu\text{A}$ d) $2.5\text{ }\mu\text{A}$

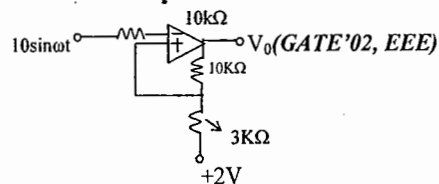
2. The output voltage (V_0) of the Schmitt trigger shown in figure swings between $+15\text{V}$ and -15V . Assume that the operational amplifier is ideal. The output will change from $+15\text{V}$ to -15V . When the instantaneous value of the input sine wave is



- a) 5V in the positive slope only
b) 5V in the negative slope only
c) 5V in the positive and negative slopes
d) 3V in the positive and negative slopes

3. The digital circuit using two inverters will act as

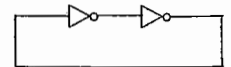
- a) a bistable multivibrator
b) an astable multivibrator
c) a monostable multivibrator d) an oscillator



(GATE'04, EEE)

4. In the Schmitt trigger circuit, if $V_{\text{CE(sat)}} = 0.1\text{V}$, the output logic low level (V_{OL}) is

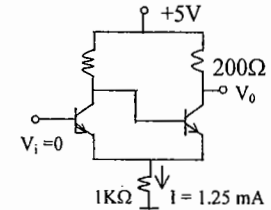- a) 1.25 V
b) 1.35 V
c) 2.50 V
d) 5.00 V



5. Consider the following two statements :

(GATE'01, ECE)

- Statement 1 : Astable multivibrator can be used for generating square wave.
Statement 2 : Bistable multivibrator can be used for storing binary information.

- a) only statement 1 is correct b) only statement 2 is correct
c) both the statements 1 and 2 are correct d) both the statements 1 and 2 are incorrect

6. The most commonly used amplifier in sample and hold circuits is (GATE-2000, ECE)

- a) a unity gain inverting amplifier b) a unity gain non-inverting amplifier
c) an inverting amplifier with a gain of 10 d) an inverting amplifier with a gain of 100

7. Match List – I and List – II and select the correct answer using the codes given below the lists :
(IES-2003, ECE)

- | | |
|-----------------------------|---|
| A. Schmitt trigger | 1. It needs a pulse transformer |
| B. Monostable multivibrator | 2. It is used to generate getting pulse whose width can be controlled |
| C. Astable multivibrator | 3. It is a bistable circuit |
| D. Blocking oscillator | 4. It has no stable state |
- a) A B C D b) A B C D c) A B C D d) A B C D
3 2 4 1 2 3 1 4 3 2 1 4 2 3 4 1

8. A Schmitt trigger circuit is used for

- (a) shaping an input pulse into a square pulse, (b) producing a delayed pulse,
(c) generating a ramp, (d) differentiating a pulse.

9. For producing an Identical delayed pulse, we should use a

- (a) bistable multivibrator, (b) astable multivibrator,
(c) monostable multivibrator, (d) Schmitt trigger.

10. A Bootstrap Sweep uses a

- (a) common-emitter amplifier with a large voltage gain,
(b) common-base amplifier with a large voltage gain,
(c) common-collector amplifier with a large voltage gain close to unity,
(d) high-gain narrow-band amplifier.

11. A Miller Sweep has a good linearity because it employs
 (a) negative current feedback, (b) positive voltage feedback,
 (c) negative voltage feedback, (d) compound feedback.
12. The speed-up capacitors are used in a bistable circuit in order to reduce
 (a) the settling time, (b) the transition time,
 (c) the trigger amplitude required, (d) the base biasing supply voltage.
13. In an ideal OPAMP, the input impedance R_i and output impedance R_o are given by
 (a) $R_i=0$, $R_o=0$, (b) $R_i=0$, $R_o=\infty$, (c) $R_i=\infty$, $R_o=\infty$, (d) $R_i=\infty$, $R_o=0$.
14. Differential amplifiers are very commonly used in low-level d.c. amplifiers because of
 (a) large bandwidth, (b) high input impedance,
 (c) large-gain, (d) low offsets and drifts.
15. The frequency, at which the gain of an OPAMP is 0dB, is called
 (a) cross-over frequency, (b) unity-gain cross-over frequency,
 (c) take-off frequency, (d) zero dB frequency.
16. Frequency compensation has to be used in OPAMP's in order to
 (a) increase the bandwidth, (b) increase the gain,
 (c) improve the stability of gain, (d) decrease the drift.
17. The common-mode rejection ratio, of a BJT difference amplifier, can be improved by
 (a) increasing the emitter resistance, (b) increasing the collector resistance,
 (c) decreasing the collector resistance, (d) decreasing the emitter resistance.
18. For square wave generation, _____ is used.
 (a) astable multivibrator (b) bistable multivibrator
 (c) monostable multivibrator (d) none
19. For pulse wave generation, _____ is used.
 (a) astable multivibrator (b) bistable multivibrator
 (c) monostable multivibrator (d) none
20. For flip-flop generation, _____ is used.
 (a) astable multivibrator (b) bistable multivibrator
 (c) monostable multivibrator (d) none
21. The disadvantage of astable multivibrator is _____
 (a) it is used as a square wave generator
 (b) frequency can be changes by increasing the voltage
 (c) both the transistors may go into saturation simultaneously. (d) None
22. Which of the following triggering is best suited for monostable multivibrator
 (a) symmetrical (b) asymmetrical
 (c) symmetrical positive triggering (d) symmetrical negative triggering

23. Purpose of collector catching diode in a binary is
 a) to maintain constant o/p swing b) to maintain constant base saturation currents
 c) both a & b d) none
24. Pulse width of a collector coupled monostable multivibrator is given by
 a) $T = 0.69RC$ b) $T = 1.38RC$ c) $T = RC$ d) $T = 0.707RC$
25. The frequency of oscillation of astable multivibrator with $R_1 = R_2 = 1k\Omega$, $C_1 = C_2 = 1\mu F$ is
 a) $(1/1.38)kHz$ b) $1.38kHz$ c) $(1/38)Hz$ d) $13.8Hz$
26. Advantages of emitter coupled astable over collector coupled circuit is
 a) it is inherently self starting b) o/p is free of recovery transients
 c) it has an isolated i/p d) all of these
27. Sine wave can be converted into square wave using
 a) monostable b) schmitt trigger
 c) clamping circuit d) astable multivibrator
28. Standard pulse generator usually employs _____ multivibrator
 a) astable b) monostable c) bistable d) none
29. Bistable multivibrator differ from astable multivibrator in the use of _____
 between states instead of RC coupling.
 a) triggering b) resistors c) capacitors d) none
30. Which of following is known as voltage to time converter.
 a) monostable b) bistable c) astable d) schmitt trigger
31. Which of the following is known as voltage to frequency converter
 a) astable b) bistable c) monostable d) schmitt trigger
32. Which of the following is used in frequency division
 a) positive b) negative c) either positive (or) negative d) none


KEY -- OBJECTIVE QUESTIONS

1. d 2. a 3. a 4. b 5. c 6. b 7. a 8. a 9. b 10. c
 11. c 12. b 13. c 14. a 15. b 16. d 17. a 18. a 19. c 20. c 21. c
 22. b 23. c 24. a 25. a 26. d 27. b 28. b 29. a 30. a 31. a 32. a

Chapter: 6 FEEDBACK AMPLIFIERS AND OSCILLATORS

Feedback amplifiers

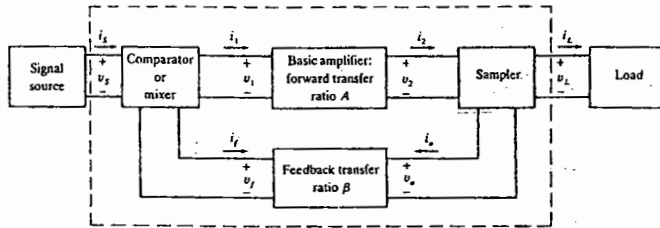A general feedback amplifier structure is shown below:




The input signal is applied to a mixer network, where it is combined with a feedback signal. The resultant signal from the mixer is applied to the basic amplifier. The amplifier output is sampled and applied to a feedback network. The output of feedback network is fed to a mixer. If the feedback signal is of opposite polarity to the input signal, negative feedback results. While negative feedback results in reduced overall gain, a number of improvements are obtained, among them being.

1. Stabilization of gain
2. Improved frequency response
3. Reduced noise
4. More linear operation

FEED BACK CONNECTION TYPES →

There are four basic ways of connecting the feedback signal. Both voltage and current can be fed back to the input either in series or parallel. Specifically there can be

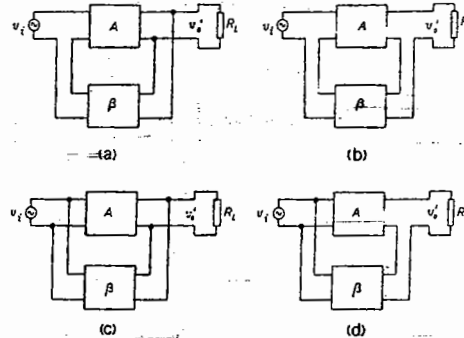1. Voltage – series feedback (fig-a)
2. Voltage – shunt feedback (fig-c)
3. Current – series feedback (fig-b)
4. Current – shunt feedback (fig-d)




Here voltage refers to connecting the output voltage as input to the feedback network; current refers to tapping off some output current through the feedback network. Series refers to connecting the feedback signal in series with the input signal voltage; shunt refers to connecting the feedback signal in shunt with an input current source.


Series feedback connection tends to increase the input resistance while shunt feedback connection tends to decrease the input resistance. Voltage feedback tends to decrease the

output impedance while current feedback tends to increase the output impedance. Typically, higher input and lower output impedances are desired for most cascade amplifiers. Both of these are provided using the voltage – series feedback connection.

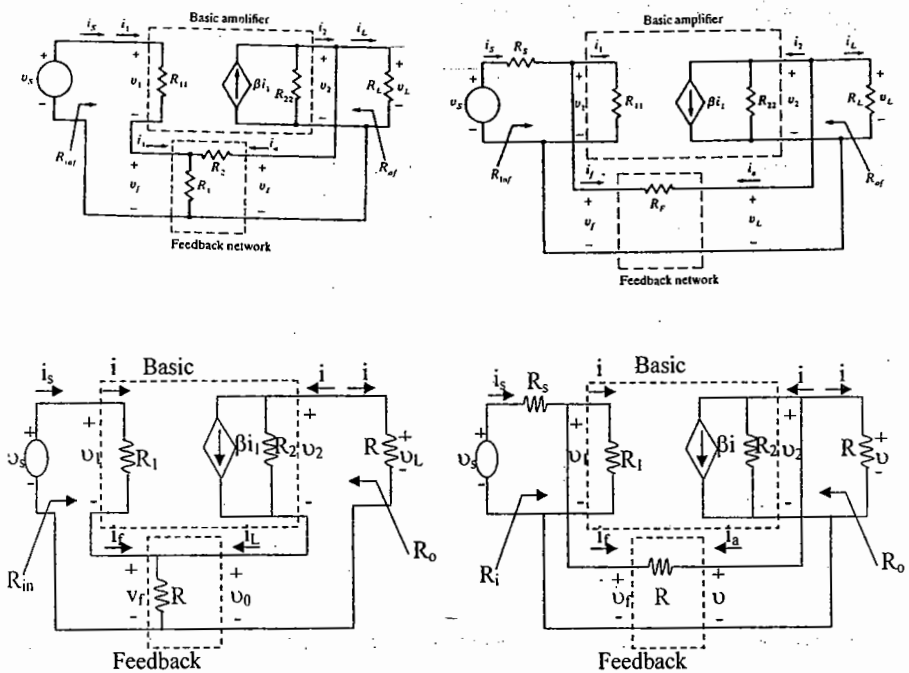The four feedback configurations with basic amplifier in its equivalent circuit form and feedback network with resistances are indicated below



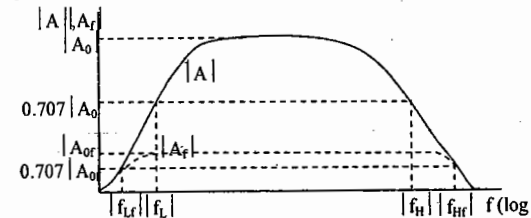Effect of Negative Feedback on Gain and Band width →



The above figure shows that the amplifier with negative feedback has more bandwidth (B_f) than the amplifier without feedback (B). The feedback amplifier has a higher upper 3-dB frequency. In fact, the product of gain and frequency remains the same so that the gain bandwidth product of the basic amplifier is the same value for the feedback amplifier.

Gain Stability with Feedback →

$$\left| \frac{dA_f}{A_f} \right| = \left| \frac{1}{1 + \beta A} \right| \left| \frac{dA}{A} \right|$$

$$\left| \frac{dA_f}{A_f} \right| \cong \left| \frac{1}{\beta A} \right| \left| \frac{dA}{A} \right| \quad \text{for } \beta A \gg 1$$

This shows that magnitude of the relative change in gain $\left| \frac{dA_f}{A_f} \right|$ is reduced by the factor βA


Compared to that without feedback $\left(\left| \frac{dA}{A} \right| \right)$

Parameter	Voltage series	Current shunt	Voltage shunt	Current series
1. Output signal	Voltage	Current	Voltage	Current
2. Input Signal	Voltage	Current	Current	Voltage
3. Basic amplifier	Voltage	Current	Transresistance	Transconductance
4. A (With out feedback)	$A_v = V_o/V_i$	$A_i = I_o/I_i$	$R_m = V_o/I_i$	$G_m = I_o/V_i$
5. β	V_f/V_o	I_f/I_o	I_f/V_o	V_f/I_o
6. $D = 1 + A\beta$	$1 + A_v\beta$	$1 + A_i\beta$	$1 + R_m\beta$	$1 + G_m\beta$
7. A_f	A_v/D	A_i/D	R_m/D	G_m/D
8. R_{if}	R_i/D	R_i/D	R_i/D	R_i/D
9. R_{of}	R_o/D	R_o/D	R_o/D	R_o/D
10. f_{if}	f_i/D	f_i/D	f_i/D	f_i/D
11. f_{of}	f_o/D	f_o/D	f_o/D	f_o/D
13. BW_f	$\cong BW.D$	$\cong BW.D$	$\cong BW.D$	$\cong BW.D$
14. d_f (distortion)	$=d/D$	$=d/D$	$=d/D$	$=d/D$
15. Noise	Decreases	Decreases	Decreases	Decreases

Oscillators: The use of positive feedback which results in a feedback amplifier having closed-loop gain A_f greater than 1 and satisfying the phase conditions will result in operation as an oscillator circuit. To understand how a feedback circuit performs as an oscillator consider the feed back circuit below.

When the switch at the amplifier output is open, no oscillation occurs. Consider that we have a fictitious voltage at the amplifier input (V_i). This results in an output voltage $V_o = AV_i$ after the amplifier stage and in a voltage $V_f = \beta(AV_i)$ after the feedback stage. Thus, we have a feedback voltage $V_f = \beta AV_i$, where βA is referred to as the loop gain. If the circuits of the

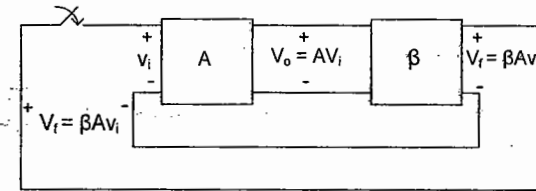base amplifier and feed back network provide βA of a correct magnitude and phase, V_f can be made equal to βV_i .



Then, when the switch is closed and fictitious voltage V_i is removed, the circuit will continue operating since the feedback voltage is sufficient to drive the amplifier and feed back circuits resulting in a proper input voltage to sustain the loop operation. The output waveform will still exist after the switch is closed. The condition $\beta A = 1$ is met. This is known as the Barkhausen Criterion for oscillation.

In reality, no input signal is needed to start the oscillator going. Only the condition $\beta A = 1$ must be satisfied for self sustained oscillations to result. In practice βA is made greater than 1, and the system is started oscillating by amplifying noise voltage which is always present.

Another way of seeing how the feed back circuit provides operation as an oscillator is obtained by noting the denominator in the basic feed back equation. $A_f = A / (1 + \beta A)$. When $\beta A = -1$ or magnitude 1 at a phase angle of 180° , the denominator becomes 0 and the gain with feedback, A_f , becomes infinite. Thus, an infinitesimal signal can provide a measurable output voltage, and the circuit acts as an oscillator even without an input signal.

Phase-Shift Oscillator:

Using classical network analysis, we find that

$$f = \frac{1}{2\pi RC \sqrt{6}}$$

$$\beta = \frac{1}{29}$$

and the phase shift is 180°

For the loop gain A to be greater than unity the gain of the amplifier stage must be greater than $1/\beta$ or 29:

$$A > 29$$


The frequency given above is that at which the total phase shift is 180° . If one measured the phase shift per RC section, each section would not provide the same phase shift. If it were desired to obtain exactly a 60° phase shift for each of three stages, then emitter-follower stages would be needed for each RC section to prevent each from being loaded from the following circuit.

Analysis of the ac circuit provides the following equation for the resulting oscillator frequency:

$$f = \frac{1}{2\pi RC} \frac{1}{\sqrt{6 + 4(R_c/R)}}$$

For the loop gain to be greater than unity, the requirement on the current gain of the transistor is found to be
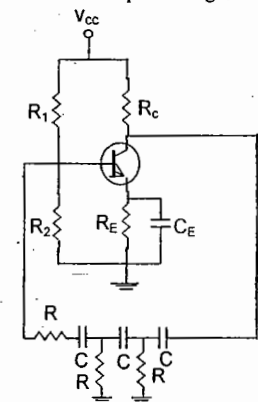
$$h_{fe} > 23 + 29 \frac{R}{R_c} + 4 \frac{R_c}{R}$$




FET phase shift Oscillator:

The amplifier stage is self biased with a capacitor bypassed source resistor R_S and a drain bias resistor R_D . The FET device parameters of interest are g_m and r_d .

$$A = g_m R_L \quad \text{where} \quad R_L = \frac{R_D r_d}{R_D + r_d}$$

It is assumed that the input impedance of the FET amplifier stage is infinite.

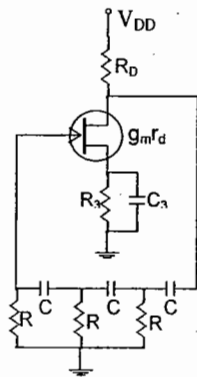**Wien Bridge Oscillator →**

The figure shows a basic version of a Wien bridge oscillator circuit. Resistors R_1 , R_2 and capacitors C_1 , C_2 form the frequency adjustment elements, while resistors R_3 and R_4 form part of the feedback path. Neglecting the loading effects of the op-amp input and output impedances, the analysis of the bridge circuit results in

$$\frac{R_3}{R_4} = \frac{R_1}{R_2} + \frac{C_2}{C_1}$$


$$\text{And } f_0 = \frac{1}{2\pi\sqrt{R_1 C_1 R_2 C_2}}$$

If, in particular, the values are $R_1 = R_2 = R$ and $C_1 = C_2 = C$, the resulting oscillator frequency is

$$f_0 = \frac{1}{2\pi RC}$$

$$\text{and } \frac{R_3}{R_4} = 2$$

Thus a ratio of R_3 to R_4 greater than 2 will provide sufficient loop gain for the circuit to oscillate.


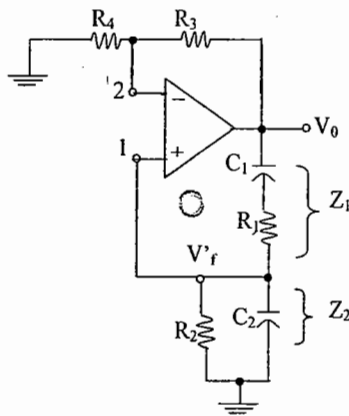
**Tuned Oscillator Circuit →**

Colpitts Oscillator:

The oscillator frequency can be found to be

$$f_0 = \frac{1}{2\pi\sqrt{LC_{eq}}}$$

$$\text{Where } C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

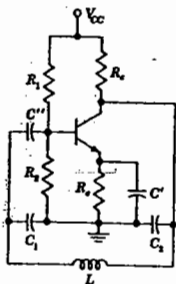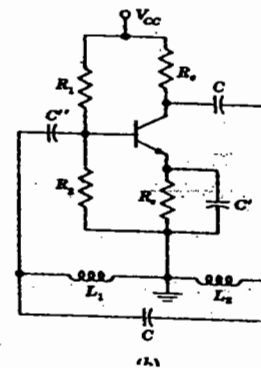**Hartley Oscillator:**

The inductors L_1 and L_2 have a mutual coupling, M , which must be taken into account in determining the equivalent inductance for the resonant tank circuit. The circuit frequency of oscillation is then given approximately by

$$f_0 = \frac{1}{2\pi\sqrt{L_{eq} C}}$$


$$\text{With } L_{eq} = L_1 + L_2 + 2M$$

Crystal Oscillator → A crystal oscillator is basically a tuned – circuit oscillator using a piezoelectric crystal as a resonant tank circuit. The crystal (usually quartz) has a greater stability in holding constant at whatever frequency the crystal is originally cut to operate. Crystal oscillators are used whenever great stability is required, for example, in communication transmitters and receivers.

OBJECTIVES SET - A

- In a common Emitter amplifier the unbypassed emitter resistance provides
 - Voltage shunt feedback
 - Current series feedback
 - Negative voltage feedback
 - Positive-current feedback
- A Wien bridge oscillator is shown in the figure. Which of the following statements are true, if 'f' is the frequency of oscillation?

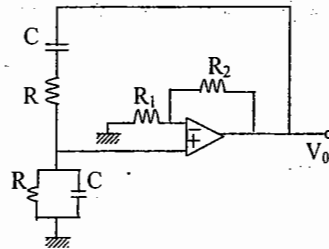- For $R = 1K$, $C = 1 \mu F$, $f = 1KHZ$
- For $R = 3K$, $C = 1 \mu F$, $f = 3KHz$
- The gain of the op-amp stage should be less than two for proper operation.
- The gain of the op-amp stage should be three for proper operation.




- A practical R-C sinusoidal oscillator is built using a positive feedback amplifier with a closed loop gain slightly less than unity. FALSE/TRUE

- The voltage series feedback in a feedback amplifier leads to increase in band width, while the voltage gain becomes less sensitive
 - decrease in overall gain, while the input resistance decreases
 - increase in distortion, while the output resistance decreases
 - decrease in input resistance, while the output resistance increases.


- The feedback factor for the circuit shown is

- 9/100
- 9/10
- 1/9
- 1/10

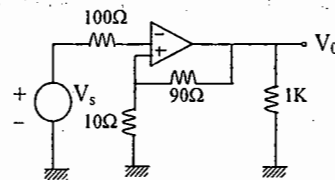


- For the oscillator circuit shown in figure, the expression for the time period of oscillation can be given by (where $\tau = RC$)

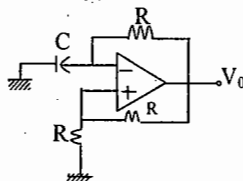- $\tau \ln 3$
- $2\tau \ln 3$
- $\tau \ln 2$
- $2\tau \ln 2$



- The feedback used in the circuit can be clarified as

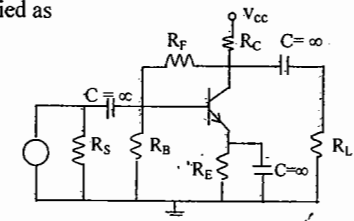- shunt-series feedback
- shunt-shunt feedback
- series-shunt feedback
- series-series feedback



- An amplifier without feedback has a voltage gain of 50, input resistance of $1K\Omega$ and output resistance of $2.5K\Omega$. The input resistance of the current-shunt negative feedback amplifier using the above amplifier with a feedback factor of 0.2 is


- 1/11 k Ω
- 1/5k Ω
- 5k Ω
- 11k Ω

- In a negative feedback amplifier using voltage-series feedback

- R_i decreases and R_o decreases
- R_i decreases and R_o increases
- R_i increases and R_o decreases
- R_i increases and R_o increases


- The circuit in figure employs a positive feedback and is intended to generate sinusoidal oscillations. If at a frequency f_0 , loop gain = 1 $\angle 0^\circ$, then to sustain oscillations at this frequency

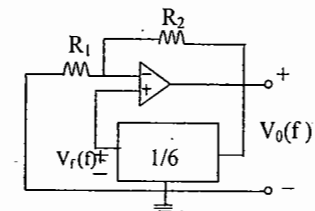- $R_2 = 5R_1$
- $R_2 = 6R_1$
- $R_2 = R_1/6$
- $R_2 = R_1/5$



- The oscillator circuit is

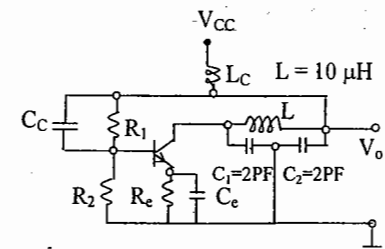- Hartley oscillator with $f_{osc} = 79.6$ MHz
- Colpitts oscillator with $f_{ox} = 79.6$ MHz
- Hartley oscillator with $f_{osc} = 159.2$ MHz
- Colpitts oscillator with $f_{osc} = 159.2$ MHz



- A higher-Q quartz crystal exhibits series resonance at the frequency ω_s and parallel resonance at the frequency ω_p . Then

- ω_s is very close to, but less than ω_p
- $\omega_s \ll \omega_p$
- ω_s is very close to, but greater than ω_p
- $\omega_s \gg \omega_p$

13. Introduction of feedback in an amplifier increases the input impedance from $1\text{K}\Omega$ to $40\text{K}\Omega$. It is due to

- a) positive feedback b) shunt-current negative feedback
c) series-current negative feedback d) shunt-voltage negative feedback


14. A radio frequency signal contains three frequencies: 870 KHz , 875 KHz and 880 KHz . This signal needs to be amplified. The amplifier used should be

- a) audio frequency amplifier b) wide-band amplifier
c) tuned voltage amplifier d) push-pull amplifier

15. An emitter follower circuit is widely used in electronic instruments because

- a) its voltage gain is less than unity
b) its output impedance is high and input impedance is low
c) its output impedance is low and input impedance is high
d) its voltage gain is very high

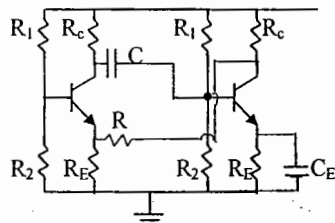16. In the circuit shown in fig, the feedback causes



- a) An increase in both the input and output impedances.
b) An increase in the input impedance but a decrease in the output impedance.
c) A decrease in both the input and output impedances.
d) A decrease in the input impedance but an increase in the output impedance.

17. The voltage gains of an amplifier without feedback and with negative feedback respectively are 100 and 20. The percentage of negative feedback (β) would be

- a) 40% b) 5% c) 20% d) 80%

18. If the Q of a single stage single-tuned amplifier is doubled, then its bandwidth
a) remains same b) becomes half c) becomes double
d) becomes four times

19. The negative feedback in an amplifier

- (a) reduces the voltage gain (b) increases the voltage gain
(c) does not affect the voltage gain
(d) can convert it into an oscillator if the amount of feedback is sufficient

20. Introduction of feedback in an amplifier increases the input impedance from $1\text{ k}\Omega$ to $40\text{ k}\Omega$. It is due to

- (a) positive feedback (b) shunt-current negative feedback
(c) series-current negative feedback (d) shunt-voltage negative feedback

21. One of the effects of negative feedback in amplifiers is to

- (a) increase the noise (b) increase the harmonic distortion
(c) decrease the bandwidth (d) decrease the harmonic distortion

22. Positive feedback, in an amplifier circuit will the gain of the amplifier.
(a) increase (b) decrease, (c) not alter

23. Gain stability in an amplifier can be improved by using

- (a) positive feedback, (b) negative feedback,
(c) both positive and negative feedback.

24. Effect of voltage negative feedback on the input impedance of an amplifier.

- (a) increase (b) decrease (c) not altered

25. Effect of voltage negative feedback on the output impedance of an amplifier

- (a) increase (b) decrease (c) not altered

26. Application of current negative feedback will

- (a) increase the input impedance (b) increase the output impedance
(c) increase both the input and output impedances

27. An emitter follower is an example of

- (a) current negative feedback
(b) voltage negative feedback
(c) neither voltage feedback nor current negative feedback.

28. An emitter follower has a input impedance value.

- (a) large (b) small (c) very small

29. An emitter follower has a output impedance value.
 (a) small (b) large (c) very large
30. With negative feedback, the bandwidth of an amplifier can be
 (a) increased (b) decreased (c) neither increased nor decreased
31. A emitter-follower amplifier can help to
 (a) match a low-resistance source with a high-resistance load
 (b) match a high-resistance source with a low-resistance load
 (c) match equal values of source resistance and load resistance
32. In a multistage amplifier, application of negative feedback can
 (a) produce stability in all cases (b) produce instability in some cases
 (c) produce instability in all cases
33. With negative feedback, the gain-bandwidth product of an amplifier would be
 (a) increased (b) decreased (c) neither increased nor decreased
34. The main advantage of applying negative feedback to an amplifier is to
 (a) increase the amplifier gain (b) decrease the amplifier gain
 (c) make the amplifier oscillate (d) improve the amplifier stability
35. A negative feedback amplifier, with $A=1000$ and $\beta=0.20$, will have an overall gain of about
 (a) 20 (b) 200 (c) 50 (d) 5 (e) -5
36. In a negative feedback voltage amplifier, with $A = 1000$ and $\beta = 0.2$ there is an unwanted hum voltage of 1V at its output before feedback is applied. With negative feedback, the hum voltage will be
 (a) 1 V (b) 0.2 V (c) 5 mV (d) 1 mV.
37. In a negative feedback voltage amplifier, with $A=1000$ and $\beta=0.2$, the input resistance is 1 K Ω before voltage negative feedback is applied. After negative feedback, the input resistance will be
 (a) 200 K Ω (b) 5 Ω (c) 1 M Ω (d) 5 K Ω
38. In a current amplifier, with $A=1000$ and $\beta=0.20$, the output resistance is 100 Ω before current negative feedback is applied. After negative feedback is applied, its output resistance will be
 (a) 0.5 Ω (b) 20 K Ω (c) 500 Ω (d) 20
39. For generating a 1-kHz note, the most suitable circuit is
 (a) Hartley oscillator (b) Colpitts oscillator
 (c) tuned-collector oscillator (d) Wien bridge oscillator
40. To generate a 1-MHz signal, the most suitable circuit is
 (a) Wien bridge oscillator (b) phase-shift oscillator
 (c) Colpitts oscillator (d) none of the above

41. We use a crystal oscillator because
 (a) it gives high output voltage (b) it works at high efficiency
 (c) the frequency of oscillations remains substantially constant
 (d) it requires very low dc supply voltage
42. Oscillator is a
 a) ac to dc converter b) dc to ac converter c) none
43. The condition which is required to get sustained oscillation is called
 a) Barkhausen criteria b) $|AB| = 1$
 c) The total phase shift introduced by both amplifier and feedback network must be equal to zero (or) multiples of 2π radians
 d) all of the above
44. In transistor tuned oscillator, frequency of oscillations is determined by
 a) RC network b) Tank circuit c) RC parallel circuit d) None
45. The minimum gain required by transistor, when it is used in RC phase shift oscillator is
 a) 44.5 b) 29 c) 3 d) None
46. The minimum gain is 29, when ----- is used in RC phase shift oscillator
 a) Transistor b) FET c) Tank circuit d) None
47. In RC phase shift oscillator, phase shift introduced by each RC network is
 a) 45° b) 90° c) 60° d) 180°
48. In Hartley oscillator, feedback network consists of -----
 a) Two inductors b) One capacitor c) Both a & b d) None
49. In Colpitts oscillator, feedback network consists of -----
 a) Two capacitors b) One inductor c) Both a & b d) None
50. The minimum gain required by the amplifier is -----, when it is used as a Wien-bridge oscillator
 a) 3 b) $\sqrt{29}$ c) 44.5 d) None
51. ----- is used as a feedback network in a Wien-bridge oscillator
 a) Feedback amplifier b) Wien-Bridge c) RC network d) None
52. The phase shift introduced by Wien bridge is -----
 a) 90° b) 180° c) 0° d) zero
53. Limitation of LC & RC oscillators: their frequency of operation varies with
 a) temperature b) LC network c) RC network d) None
54. Crystals are used to convert mechanical energy into electrical energy & vice versa. This phenomena is known as
 a) Piezo conductive effect b) Piezo magnetic c) Piezo electric effect d) None
55. Piezo electric effect is used in the following crystals
 a) Rochelle salt b) Quartz c) both a & b d) None
56. In transistor RC phase shift oscillator the type of feedback used is ----
 a) voltage - shunt b) voltage - series c) current - shunt d) current - series

57. In FET RC phase shift oscillator the type of feedback used is-----

- a) voltage - shunt b) voltage - series c) current - shunt d) current - series

58. In LC tuned oscillator the frequency of oscillations

- a) $f = \frac{1}{2\pi RC\sqrt{6+4K}}$ b) $f = \frac{1}{2\pi RC\sqrt{6}}$ c) $f = \frac{1}{2\pi\sqrt{LC}}$ d) None

59. In transistor RC phase shift oscillator the frequency of oscillations is

- a) $f = \frac{1}{2\pi RC\sqrt{6+\frac{R_C}{R}}}$ b) $f = \frac{1}{2\pi RC\sqrt{6+4R_C}}$
 c) $f = \frac{1}{2\pi RC\sqrt{6+4R}}$ d) None

60. In FET RC phase shift oscillator the frequency of oscillations is

- a) $f = \frac{1}{2\pi RC}$ b) $f = \frac{1}{2\pi RC\sqrt{6}}$ c) $f = \frac{1}{12\pi RC}$ d) None

61. In Hartley oscillator, the frequency of oscillations is

- a) $f = \frac{1}{2\pi\sqrt{LC}}$ b) $f = \frac{1}{2\pi\sqrt{L_1C_1}}$ c) $f = \frac{1}{2\pi(\sqrt{L_1+L_2})C}$ d) None

62. In Colpitts oscillator circuit, frequency of oscillation is

- a) $f = \frac{1}{2\pi\sqrt{L\left(\frac{c_1c_2}{c_1+c_2}\right)}}$ b) $f = \frac{1}{2\pi\sqrt{LC}}$ c) $f = \frac{1}{2\pi\sqrt{L_1C_1}}$ d) None

63. In Wien bridge oscillator, frequency of oscillations is

- a) $f = \frac{1}{2\pi\sqrt{RC}}$ b) $f = \frac{1}{2\pi RC}$ c) $f = \frac{1}{2\pi R_1C_1}$ d) none

64. Frequencies that can be obtained with crystals are within the range

- a) 25 kHz to 5 MHz b) 20 to 20 kHz c) 20 kHz to 10 MHz d) none

65. In tuned collector L = 50mH, C = 20PF is used. The frequency of operation is

- a) 10⁶ MHz b) 10⁶/2π Hz c) 2π/10⁶ Hz d) none

66. In FET RC phase oscillator, if the value of R is doubled, then frequency of operation is

- a) $f = 1/2\pi RC$ b) $f = \frac{1}{2\pi RC\sqrt{3}}$ c) $f = \frac{1}{2\pi RC\sqrt{6}}$ d) none

67. RC phase shift oscillator can have _____ RC stages in β network

- a) 3 b) 4 c) 6 d) all of the above

68. In Wien bridge oscillator $R_1 = R_2 = 100 \text{ kHz}$, $C_1 = C_2 = 0.01 \mu\text{F}$. The frequency of oscillations is

- a) 0.16 kHz b) 0.16 Hz c) 1 kHz d) none

69. Frequency of oscillations of RC phase shift oscillator is

- a) impossible to vary b) difficult to vary c) always variable d) none

70. A crystal has $L = 3.3\text{H}$, $C_s = 0.042\text{pF}$, $R = 390 \Omega$. If the crystal operates at 430 kHz, the Q of the crystal is

- a) 23 b) 230 c) 23000 d) none

71. RC phase shift oscillator can have

- a) $f_0 = \frac{\sqrt{6}}{2\pi RC}$ b) $f_0 = \frac{1}{2\pi RC\sqrt{6}}$ c) both a & b d) none

72. The oscillation frequency of a transistor Colpitts oscillator is ($C_1 = C_2 = 0.1\mu\text{F}$, $L = 200\mu\text{H}$)

- a) 0.16 MHz b) 0.16 Hz c) 0.16 kHz d) none

73. The operating frequency of a transistor Hartley oscillator, if $L_1 = 25\text{mH}$, $L_2 = 25\text{mH}$, $C = 20\text{pF}$, is

- a) 0.16Hz b) 0.06Hz c) 0.16mHz d) none

74. In Wien bridge oscillator gain & frequency are

- a) $|A| \geq 3, f_0 = \frac{1}{2\pi RC}$ b) $|A| \geq 2, f_0 = \frac{1}{2\pi RC}$
 c) $|A| \geq 29, f_0 = \frac{1}{2\pi\sqrt{6}RC}$ d) $|A| \geq 29, f_0 = \frac{1}{2\pi RC}$

75. An electronic oscillator is

- a) an amplifier b) an amplifier with negative F/B
 c) converter of ac to dc d) converter of dc to ac

76. In BJT RC phase shift oscillator, f_0 is

- a) $f_0 = \frac{1}{2\pi\sqrt{6+4k}RC}$ b) $f_0 = \frac{\sqrt{6+4k}}{2\pi R}$ c) both a and b d) none

77. In crystal oscillator, frequency determining parameters are

- a) thickness of crystal b) angle of cut
 c) physical size of crystal d) all of the above

78. To generate 1MHz frequency the most suitable oscillation is

- a) phase shift b) Wien bridge c) Colpitts d) none

79. For generating 1kHz frequency the most suitable oscillator is

- a) tuned oscillator b) Hartley c) Colpitts d) Wien bridge

80. The Q of a crystal is of the order of

- a) 100 b) 1000 c) 50 d) more than 10000

81. Crystal oscillator is commonly used in

- a) laboratories b) radio receivers c) radio transmitters d) none

82. _____ oscillator is a fixed frequency oscillator

- a) Wien bridge b) Crystal c) Hartley d) Colpitts

83. To change the frequency of crystal oscillator, we should change

- a) gain of the amplifier b) DC power supply c) crystal thickness d) none

84. In a particular oscillator circuit if the value of β is $1/100$, the min. gain required by the amplifier to get sustained oscillations is

- a) 10 b) 1000 c) 200 d) 100

85. In order to produce frequencies in the microwave region one should use _____ oscillator.

- a) Wien bridge b) crystal c) both (a) & (b) d) none

86. Frequency stability of RC oscillator is _____ than LC oscillator.

- a) greater b) lower c) same as d) none

87. In tuned collector oscillator if L value is multiplied by four, the frequency of oscillation is

- a) is halved b) doubles c) is reduced by four times d) remains constant

88. In BJT RC -phase shift oscillator, condition for sustained oscillations is

- a) $h_{fe} \geq 4k + 23 + \frac{49}{k}$ b) $h_{fe} \geq \frac{L_b}{L_a}$ c) $h_{fe} \geq \frac{L_b}{L_a} + \frac{h_{fe}}{RC} \frac{L_a}{L_b}$ d) none

89. In RC -oscillators, using gang capacitors, $\frac{f_0 \text{ max}}{f_0 \text{ min}}$ is

- a) 10 b) 3.3 c) $\frac{1}{10}$ d) $\frac{1}{3.3}$

90. In LC oscillators using gang capacitors, $\frac{f_0 \text{ max}}{f_0 \text{ min}}$ is

- a) 10 b) 3.3 c) $\frac{1}{10}$ d) $\frac{1}{3.3}$

91. In Hartley oscillator with inverting op-amp, condition for sustained oscillations is


- a) $\left| \frac{R_2}{R_1} \right| \geq \frac{L_b}{L_a}$ b) $\left| \frac{R_2}{R_1} \right| \geq \frac{L_b}{L_a} + \frac{h_{fe}}{R_c}$ c) $\left| 1 + \frac{R_2}{R_1} \right| \geq \frac{L_b}{L_a}$ d) none

92. In oscillators with $|A\beta| < 1$, we get

- a) square wave b) sinusoidal c) both square and sinusoidal d) triangular

93. For Clapp oscillator circuit shown below, the expression for f_0 is

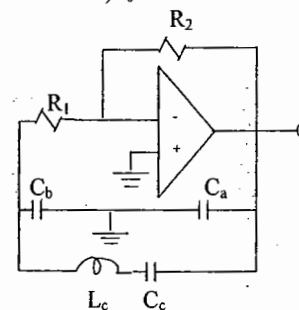- a) $f_0 = \frac{1}{2\pi\sqrt{L_c R_c}}$ b) $f_0 = \frac{1}{2\pi L_c R_c}$ c) $f_0 = \frac{1}{2\pi\sqrt{6}\sqrt{L_c R_c}}$ d) none



KEY

1. b 2. a,b,d 3. false 4. a 5. d 6. b 7. b 8. a 9. c 10. a 11. b
 12. a 13. c 14. c 15. c 16. b 17. a 18. b 19. a 20. c 21. d 22. a 23. b
 24. a 25. b 26. b 27. b 28. a 29. a 30. a 31. b 32. a 33. c 34. d 35. c
 36. c 37. a 38. a 39. d 40. c 41. c 42. b 43. d 44. b 45. b 46. b 47. -
 48. c 49. c 50. a 51. b 52. c 53. a 54. c 55. c 56. a 57. b 58. c 59. a
 60. b 61. c 62. a 63. b 64. a 65. b 66. c 67. a 68. a 69. b 70. c 71. c
 72. a 73. c 74. a 75. d 76. c 77. d 78. c 79. b 80. b 81. c 82. b 83. d
 84. d 85. b 86. b 87. a 88. a 89. a 90. b 91. a 92. a 93. a

SET - B


01. Negative feedback in an amplifier

- (A) reduces gain
- (B) increases frequency and phase distortions
- (C) reduces bandwidth
- (D) increases noise

02. An amplifier has an open-loop gain of 100, an input impedance of 1 k Ω , and an output impedance of 100 Ω . A feedback network with a feedback factor of 0.99 is connected to the amplifier in a voltage series feedback mode. The new input and output impedances, respectively, are

- (A) 10 Ω and 1 Ω
- (B) 10 Ω and 10 Ω
- (C) 100 k Ω and 1 Ω
- (D) 100 k Ω and 1 k Ω

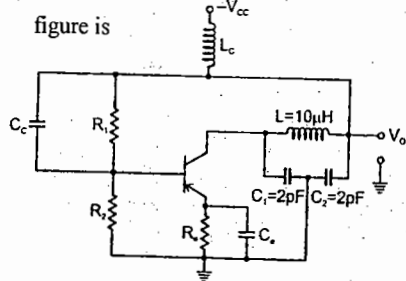03. The oscillator circuit shown in the figure is



- (A) Hartley oscillator with $f_{\text{oscillation}} = 79.6$ MHz
- (B) Colpitts oscillator with $f_{\text{oscillation}} = 50.3$ MHz
- (C) Hartley oscillator with $f_{\text{oscillation}} = 159.2$ MHz
- (D) Colpitts oscillator with $f_{\text{oscillation}} = 159.2$ MHz

04. In a negative feedback amplifier using voltage-series (ie. voltage-sampling, series mixing) feedback.

- (A) R_i decreases and R_o decreases
 - (B) R_i decreases and R_o increases
 - (C) R_i increases and R_o decreases
 - (D) R_i increases and R_o increases
- (R_i and R_o denote the input and output resistances respectively)

05. An amplifier without feedback has a voltage gain of 50, input resistance of 1 K Ω and output resistance of 2.5 K Ω . The input resistance of the current-shunt negative feedback amplifier using the above amplifier with a feedback factor of 0.2 is

- (A) 1/11 K Ω
- (B) 1/5 K Ω
- (C) 5 K Ω
- (D) 11 K Ω

06. Voltage series feedback (also called series-shunt feedback) results in

- (A) increase in both input and output impedances
- (B) decrease in both input and output impedances
- (C) increase in input impedance and decrease in output impedance
- (D) decrease in input impedance and increase in output impedance


07. The effect of current shunt feedback in an amplifier is to

- (A) increase the input resistance and decrease the output resistance
- (B) increase both input and output resistances
- (C) decrease both input and output resistances
- (D) decrease the input resistance and increase the output resistance

08. In a transconductance amplifier, it is desirable to have.

- (A) a large input resistance and a large output resistance
- (B) a large input resistance and a small output resistance
- (C) a small input resistance and a large output resistance
- (D) a small input resistance and a small output resistance

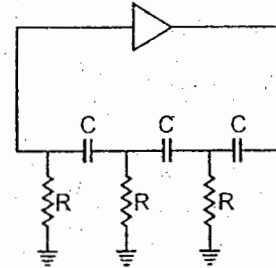09. The oscillator circuit shown in the figure has an ideal inverting amplifier. Its frequency of oscillations (in Hz) is



- (A) $\frac{1}{(2\pi\sqrt{6}RC)}$
- (B) $\frac{1}{(2\pi RC)}$
- (C) $\frac{1}{(\sqrt{6}RC)}$
- (D) $\frac{1}{\sqrt{6}(2\pi RC)}$


10. The input impedance (Z_i) and the output impedance (Z_o) of an ideal transconductance (voltage controlled current source) amplifier are

- (A) $Z_i = 0, Z_o = 0$
- (B) $Z_i = 0, Z_o = \infty$
- (C) $Z_i = \infty, Z_o = 0$
- (D) $Z_i = \infty, Z_o = \infty$

11. In a Common emitter amplifier, the unbypassed emitter resistance provides

- (A) Voltage-shunt feedback
- (B) Current-series feedback
- (C) Negative-voltage feedback
- (D) Positive-current feedback

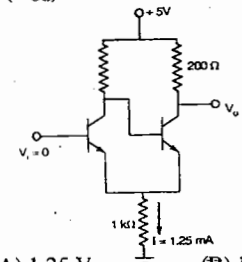12. In the Schmitt trigger circuit shown if $V_{CE(\text{sat})} = 0.1$ V, the output logic low level (V_{OL}) is



- (A) 1.25 V
- (B) 1.35 V
- (C) 2.50 V
- (D) 5.00 V

KEY: (1) A (2) C (3) B (4) C (5) A (6) C (7) D (8) A
(9) D (10) D (11) B (12) B


Chapter: 7

Power Amplifiers


An amplifier receives a signal from the input source or some pick up transducer and provides a larger version of the signal to some output device or to another amplifier stage. Since signal voltage and current are small in a small signal amplifier, the amount of power handling capacity and power efficiency are of little concern. Large – signal or power amplifiers, on the other hand, primarily provide sufficient power to an output load to drive a speaker or other power device. Thus the power amplifier circuits are used to handle large voltage signals at moderate to high current levels and their main features include power efficiency, the maximum amount of power that the circuit is capable of handling and the impedance matching to the output device.

One method used to categorise amplifiers is by class of operation. Basically, amplifier classes represent the duration the output signal varies over one cycle of operation for a full duration of input signal.

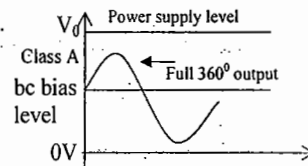Class A : The output signal varies for a full 360° of the cycle. This requires the Q –point to be biased at a level so that at least half the signal-swing of the output may vary up and swing down without going to a high enough voltage to be limited by the supply voltage level, or too low to approach the lower supply level.



Class B : A class B circuit provides an output signal varying over one-half the input signal cycle, or for 180°. Here the dc bias is at cut off (zero current). So, the output is not a faithful reproduction of the input as only one half cycle is present. Two class B operations, one to provide output on the positive-output half cycle and another output to provide operation on the negative – output half cycle are necessary. This type of connection is referred to as push – pull operation.

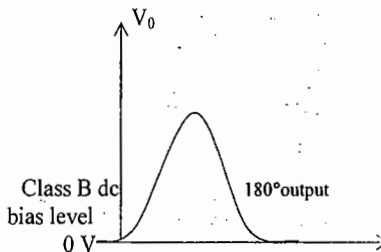

Class AB : An amplifier may be biased at a dc level above the zero base current level of class B and above one – half the supply voltage level of class. This bias condition is class AB. For class AB operation the output signal swing occurs between 180° and 360° and is neither class A nor class B operation.

Class C : The output of a class C amplifier is biased for operation at less than 180° of the cycle and will operate only with a tuned (resonant) circuit which provides a full cycle of operation for the tuned or resonant frequency.

Class D : This operating class is a form of amplifier operation using pulse signals which are on for a short interval and off for a longer interval. The major advantage of class D operation is that the amplifier is on only for short intervals and the overall efficiency can practically be very high.

Amplifier Efficiency: η

The power efficiency of an amplifier, defined as the ratio of power output to power input, improves (gets higher) going from class A to class D.

$$\% \eta = \frac{P_o(\text{ac})}{P_i(\text{dc})} \times 100\%$$

The larger the input signal, the larger the output swing up to the maximum set by the circuit. The ac power output delivered to the load (R_C) can be expressed in a number of ways.

$$P_o(\text{ac}) = V_{CE}(\text{rms}) I_C(\text{rms}) = I_C^2(\text{rms}) R_C = V_{CE}^2(\text{rms}) / R_C$$

$$\text{Where } V_{CE}(\text{rms}) = V_{CE}(\text{peak}) / \sqrt{2}$$

Using peak – to – peak signals : The ac power delivered to the load may be expressed using



$$P_o(\text{ac}) = \frac{V_{CE(p-p)} I_C(p-p)}{8} = \frac{I_C^2(p-p) R_C}{8} = \frac{V_{CE}^2(p-p)}{8 R_C}$$



The power efficiency of an amplifier represents the amount of ac power delivered from the dc source.

The maximum efficiency of a class A circuit, occurring for the largest output voltage and current swings, is only 25% with a direct or series fed load connection, and 50% with a transformer connection to the load. Class B operation, with no dc bias power for no input signal, can be shown to provide a maximum efficiency that reaches 78.5%.

Class D operation can achieve power efficiency over 90% and provides the most efficient operation of all the operating classes. Since class AB falls between class A and class B in bias, it also falls between their efficiency ratings – between 25% (or 50%) and 78.5%.

Series fed Class – A amplifier:

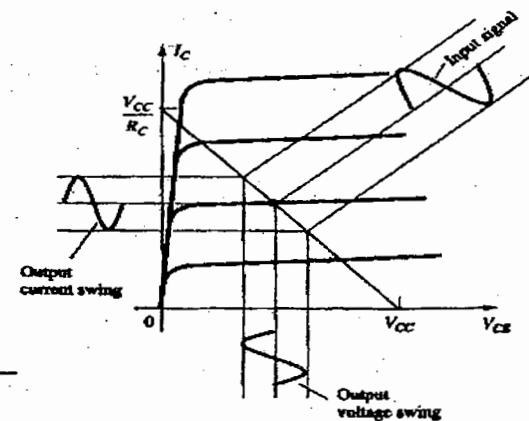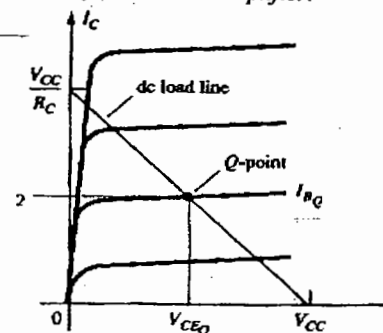

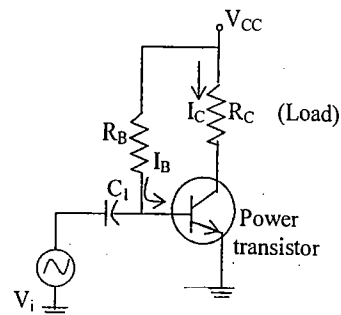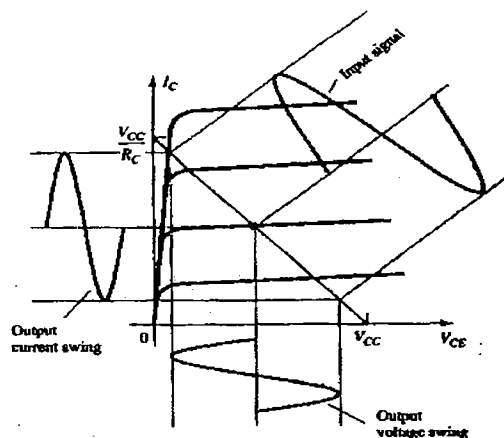

$$P_i(\text{dc}) = V_{CC} I_C$$

Even with an ac signal applied, the average current drawn from the supply remains the same. The output voltage and current varying around the bias point provide ac power to the load. This ac power is delivered to the load, R_C , in the circuit. The ac signal, V_i , causes the base current to vary around the dc bias.

$$V_{CE(p-p)} = V_{CC}$$

$$I_{C(p-p)} = V_{CC} / R_C$$

Using the maximum voltage swing.

$$\begin{aligned} \text{Maximum } P_o(\text{ac}) &= \frac{V_{CC}(V_{CC}/R_C)}{8} \\ &= \frac{V_{CC}^2}{8 R_C} \end{aligned}$$

The maximum power output can be calculated using the dc bias current set to half the maximum value.

$$\begin{aligned} \text{Maximum } P_i(\text{dc}) &= V_{CC}(\text{maximum } I_C) \\ &= V_{CC} \cdot \frac{V_{CC}/R_C}{2} = \frac{V_{CC}^2}{2 R_C} \end{aligned}$$

$$\text{Maximum } \% \eta = 25\%$$

This maximum efficiency of a class A series fed amplifier is seen to be 25%. Since this efficiency will occur only for ideal conditions of both voltage swing and current swing, most series fed circuits will provide efficiencies of much less than 25%.


Transformer Coupled Amplifier

A class A amplifier having maximum efficiency of 50% uses a transformer to couple the output signal to the load.

For a class A transformer – coupled amplifier the maximum theoretical efficiency goes up to 50%.


Based on the signals obtained using the amplifier, the efficiency can be expressed as
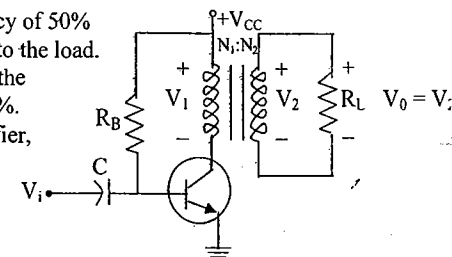
$$\% \eta = 50\% \left(\frac{V_{CE\text{max}} - V_{CE\text{min}}}{V_{CE\text{max}} + V_{CE\text{min}}} \right)^2$$



The larger the value of $V_{CE\text{max}}$ and the smaller the value of $V_{CE\text{min}}$, the closer the efficiency approaches the theoretical limit of 50%.

Push pull amplifier:

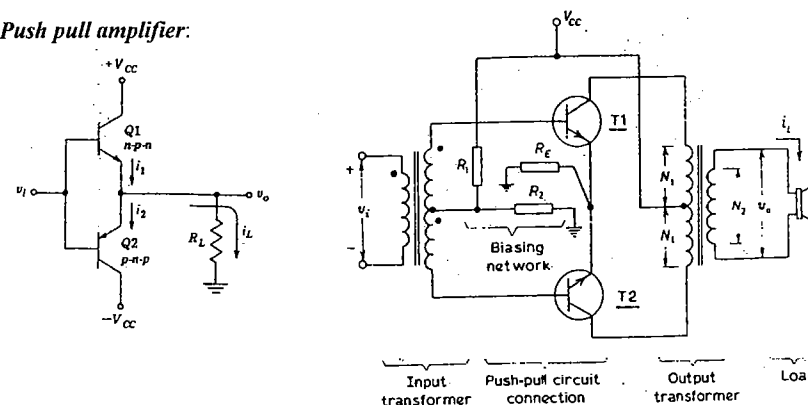

For class B operation the maximum output power is delivered to the load when $V_{L(p)} = V_{CC}$.

$$\text{Maximum } P_o(\text{ac}) = \frac{V_{CC}^2}{2 R_{L'}}$$

The corresponding peak ac current $I_{(p)}$ is then

$$I_{(p)} = \frac{V_{CC}}{R_{L'}}$$

So that the maximum value of average current from the supply is maximum

$$I_{dc} = \frac{2 I_p}{\pi} = \frac{2 V_{CC}}{\pi R_{L'}}$$

$$\therefore \text{Maximum } P_i(\text{dc}) = V_{CC}(\text{maximum } I_{dc}) = V_{CC} \left(\frac{2 V_{CC}}{\pi R_{L'}} \right) = \frac{2 V_{CC}^2}{\pi R_{L'}}$$

$$\text{Maximum } \% \eta = \frac{P_o(\text{ac})}{P_i(\text{dc})} \times 100\% = \frac{\pi}{4} \times 100\% = 78.54\%$$

For $V_{min} \neq 0$, the circuit efficiency is less than 78.5%. For class B operation the maximum power dissipated by the output transistors does not occur at the maximum power input or

output condition. The maximum power dissipated by the two output transistors occurs when the output voltage across the load is

$$V_{L(P)} = 0.636 V_{CC} (= \frac{2}{\pi} V_{CC})$$

For a maximum transistor power dissipation of


$$P_C(\max) = \frac{2V_{CC}^2}{\pi^2 R_L} = \frac{4}{\pi^2} P_0(\max) \approx 0.4 P_0(\max)$$

For example, if it is desired to deliver 10W from a class B push – pull amplifier, $P_C(\max) = 4W$. Hence transistors are to be selected with collector dissipation rating of 2W each.

Class C:

Class C amplifiers, while not used as audio amplifiers, do find use in tuned amplifiers.

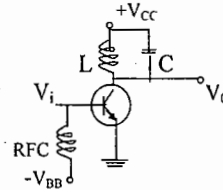The tuned circuit (L and C tank circuit) in the output of class C amplifier will provide a full cycle of output signal for the fundamental or resonant frequency of that tuned circuit (L and C tank circuit) of the output. This type of operation is therefore limited to use at one fixed frequency.



Amplifier Distortion : A pure sinusoidal signal has a single frequency at which the voltage varies positive and negative by equal amounts. Any signal varying over less than the full 360° cycle is considered to have distortion. When distortion occurs the output will not be an exact duplicate of the input signal. Distortion can occur because the device characteristics are not linear, in which case non linear or amplitude distortion occurs. This occurs with all classes of amplifier operation. Distortion can also occur because the circuit elements and devices respond to the input signal differently at various frequencies, this being frequency distortion.

A signal is considered to have harmonic distortion when there are harmonic frequency components. If the fundamental frequency has an amplitude, A_1 , and the n^{th} frequency component has an amplitude, A_n , a harmonic distortion can be defined as % n^{th} harmonic distortion = % $D_n = |A_n| / |A_1| \times 100\%$

The fundamental component is typically larger than any harmonic component,

When an output signal has a number of individual harmonic distortion components, the signal can be seen to have a total harmonic distortion based (THD)

$$\% \text{ THD} = D = \sqrt{D_2^2 + D_3^2 + D_4^2 + \dots} \times 100\%$$

For a signal occurring in class AB or class B, the distortion may be mainly due to even harmonics, of which the second harmonic component is the largest.

When distortion is present, the output power delivered to the load resistor R_C due to the fundamental component of the distorted signal is $P_1 = I_1^2 R_C / 2$

The total power due to all the harmonic components of the distorted signal can then be

$$P = (I_1^2 + I_2^2 + I_3^2 + \dots) \frac{R_C}{2}$$

The total power can also be expressed in terms of THD,

$$P = (1 + D_2^2 + D_3^2 + \dots) \frac{I_1^2 R_C}{2} = (1 + D^2) P_1$$

OBJECTIVES SET - A

- A class A transformer coupled, transistor power amplifier is required to deliver a power output of 10 watts. The maximum power rating of the transistor should not be less than.
 - 3W
 - 10W
 - 20W
 - 40W
- A power amplifier delivers 50W output at 50% efficiency. The ambient temperature is 25°C. If the maximum allowable junction temperature is 150°C, then the maximum thermal resistance θ_{jc} that can be tolerated is
- Crossover distortion behaviour is characteristic of
 - Class A output stage
 - Class B output stage
 - Class AB output stage
 - Common – base output stage
- The output power of a power amplifier is several times less than its input power. This is possible because
 - the power amplifier introduces negative resistance
 - the power amplifier converts a part of the input dc power into ac output power.
 - positive feedback exists in the circuit
 - step-up transformer is used in the circuit
- The main function of the transformer used in the output of a power amplifier is
 - to step-up the voltage
 - to increase the voltage gain
 - to match the load impedance with dynamic output resistance of the transistor
 - to safeguard the transistor against overheating
- Heat sinks are used in power amplifier circuits
 - to increase the output power
 - to reduce the heat losses in the transistor
 - to increase the voltage gain of the power amplifier
 - to increase the collector dissipation rating of the transistor
- Match each of the member of column A with appropriate member of column B

Column A	Column B
1. Maximum efficiency of a class-B amplifier is	(a) 50 %
2. Maximum efficiency of a class-A amplifier is	(b) 78.5%
3. Maximum efficiency of a class-C amplifier is	(c) 100%
- In a Class C transistor power amplifier, the base bias is
 - less than that corresponding to the collector current cut-off value,
 - equal to that corresponding to the collector current cut-off value,
 - more than that corresponding to the collector current cut-off value.
- As compared to a Class B power amplifier, a Class C power amplifier gives..... of the current signal waveform.
 - less distortion
 - the same distortion
 - more distortion

10. In the case of a Class C power amplifier, the load must be
 (a) a pure resistance (b) a parallel tuned circuit (c) a series tuned circuit.
11. The output tuned circuit, in a Class C power amplifier, must have
 (a) a large Q value (b) a small Q value (c) a medium Q value.
12. In a Class A power amplifier, the angle of flow, of the device output current, is
 (a) 90° (b) 180° (c) 360°
13. Class A power amplifier systems are
 (a) linear (b) somewhat non-linear (c) non-linear.
14. Class B power amplifier systems are
 (a) less efficient than Class A power amplifier systems
 (b) more efficient than Class C power amplifier systems
 (c) more efficient than Class A power amplifier systems but less efficient than Class C power amplifier systems.
15. Under non-signal conditions, a Class A power amplifier device as compared to a Class B power amplifier device dissipates
 (a) less energy (b) more energy (c) same energy
16. A Class A power amplifier is used for amplifying
 (a) wide-band audio frequency signals, (b) narrow-band high frequency signals,
 (c) wide-band high frequency signals.
17. As compared to parallel operation, push-pull operation, of devices, gives rise to
 (a) more distortion and less output, (b) less distortion and more output,
 (c) less distortion and less output.
18. As compared to single-ended operation, push-pull operation of devices in amplifiers, causes ----- of the signal waveform.
 (a) more distortion, (b) less distortion, (c) same distortion
19. Push-pull operation, of devices in amplifiers, helps to minimize (in the output signal waveform)
 (a) odd harmonic components (b) even harmonic components
 (c) neither odd harmonic nor even harmonic components.
20. The device rating, in the case of a Class A power amplifier, should correspond to
 (a) only the non-signal condition (b) only the signal condition
 (c) the non-signal as well as the signal condition.
21. A Class B power amplifier is termed as a linear system, if the load is
 (a) a parallel-tuned circuit (b) a resistance (c) a transformer.
22. As compared to the impedance of the signal source, the input impedance of a voltage amplifier should be
 (a) small (b) large (c) equal (d) infinite



23. A radio-frequency signal contains following three frequencies: 800 kHz, 875 kHz and 880 kHz. This signal needs to be amplified. The amplifier used should be
 (a) audio-frequency amplifier (b) wide-band amplifier
 (c) tuned voltage amplifier (d) push-pull amplifier
24. An amplifier of pass-band 450 kHz to 460 kHz will be named as
 (a) wide-band amplifier (b) audio-frequency amplifier
 (c) tuned voltage amplifier (d) video amplifier
25. A narrow-band amplifier is one that has a pass-band
 (a) Limited to 2000 Hz only
 (b) Limited to audio-frequency range only
 (c) Approximately 10% of its central frequency
 (d) Somewhere in the region near the cut-off region of the active device used
26. Tuned voltage amplifiers are not used
 (a) in public-address systems (b) in radio receivers
 (c) where a band of frequencies is to be selected and amplified
 (d) in television receivers
27. In a series resonant circuit, the impedance at resonance is
 (a) minimum, and is equal to the resistance of the coil
 (b) maximum and is equal to $Q \times R$ where Q is the quality factor of the coil and R is its resistance
 (c) equal to $2R$, where R is the coil resistance
 (d) equal to $R/2$, where R is the coil resistance
28. For a series or parallel LC circuit, resonance occurs when
 (a) X_L is ten times X_C (c) X_L is equal to X_C
 (b) X_L is Q times X_C (d) X_C is 10 times X_L
29. An ac circuit resonates at 1000 kHz. It has a quality factor 50. The bandwidth (BW) and half-power points are
 (a) BW = 10 kHz; $f_1 = 1000$ kHz; $f_2 = 1010$ kHz
 (b) BW = 20 kHz; $f_1 = 1000$ kHz; $f_2 = 1020$ kHz
 (c) BW = 20 kHz; $f_1 = 990$ kHz; $f_2 = 1010$ kHz
 (d) BW = 10 kHz; $f_1 = 995$ kHz; $f_2 = 1005$ kHz

KEY

1. c 2. 5 ° C/W 3. b 4. b 5. c 6. d 7. 1-b, 2 -a, 3 -c 8. a 9. a 10. b
 11.a 12.c 13.c 14.c 15.b 16.a 17.b 18.b 19.b 20.a 21.b
 22.b 23.c 24.c 25.c 26.a 27.a 28.c 29.c

Chapter: 8 FUNCTION GENERATOR & 555 TIMER

Voltage Controlled Oscillator (VCO) →

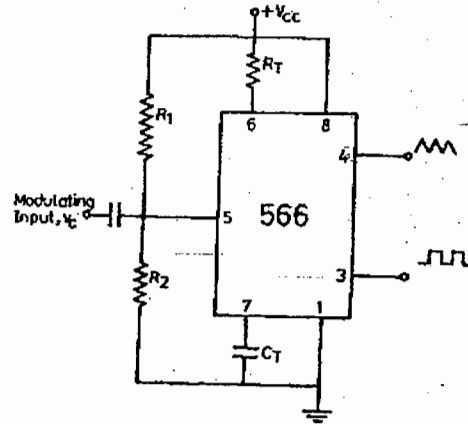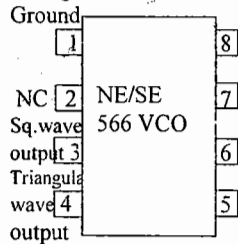

A common type of VCO available in IC form is signetics NE/SE 566. The pin configuration and basic block diagram of 566 VCO is shown above.

A timing capacitor C_T is linearly charged or discharged by a constant current source/sink. The amount of current can be controlled by changing the voltage V_C applied at the modulating input pin 5 or by changing the timing resistor R_T external to IC chip. The voltage at pin 6 is held at the same voltage as pin 5.

The voltage across the capacitor C_T is applied to the inverting input terminal of Schmitt trigger A_2 via buffer amplifier A_1 . The output voltage swing of the Schmitt trigger is designed to V_{CC} and $0.5 V_{CC}$. When the voltage on the capacitor C_T exceeds $0.5 V_{CC}$ during charging, the output of the Schmitt trigger goes Low ($0.5 V_{CC}$). The capacitor now discharges and when it is at $0.25 V_{CC}$, the output of Schmitt trigger goes HIGH (V_{CC}). Since the source and sink currents are equal, capacitor charges and discharges for the same amount of time. This gives a triangular voltage waveform across C_T which is also available at pin 4. The square wave output of the Schmitt trigger is inverted by inverter A_3 and is available at pin 3.

The frequency of oscillator f_0 is,

$$f_0 = \frac{1}{T} = \frac{i}{0.5 V_{CC} C_T} \text{ Where } i = \frac{V_{CC} - V_C}{R_T}$$

Where V_C is the voltage at pin 5,

$$\therefore f_0 = \frac{2(V_{CC} - V_C)}{C_T R_T V_{CC}}$$

The output frequency of the VCO can be changed either by (i) R_T , (ii) C_T or (iii) the voltage V_C at the modulating input terminal pin 5.


A parameter of importance for VCO is voltage to frequency conversion factor K_V and is defined as

$$K_V = \frac{\Delta f_0}{\Delta V_C}$$

Here ΔV_C is the modulation voltage required to produce the frequency shift Δf_0 for a VCO

$$\begin{aligned} \Delta f_0 &= f_1 - f_0 \\ &= \frac{2(V_{CC} - V_C + \Delta V_C)}{C_T R_T V_{CC}} - \frac{2(V_{CC} - V_C)}{C_T R_T V_{CC}} \\ &= \frac{2\Delta V_C}{C_T R_T V_{CC}} \\ \Delta V_C &= \frac{\Delta f_0 C_T R_T V_{CC}}{2} \end{aligned}$$

555 Timer →

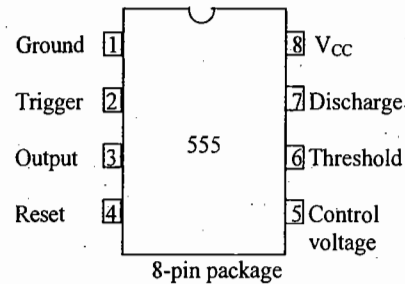

The three $5K\Omega$ internal resistors act as voltage divider, providing bias voltage of $2/3 V_{CC}$ to the upper comparator and $1/3 V_{CC}$ to the lower comparator, where V_{CC} is the supply voltage. Since these two voltages fix the necessary comparator threshold voltage, they also aid in determining the time interval. It is possible to vary time electronically too, by applying a modulation voltage to the control voltage input terminal (pin 5). A negative going trigger pulse is applied to pin 2 and should have its dc level greater than the threshold level of the lower comparator (i.e. $V_{CC}/3$). The reset input (pin 4) provides a mechanism to reset the FF in a manner which over rides the effect of any instruction coming to FF from lower comparator. The transistor Q_2 serves as a buffer to isolate the reset input from the FF and transistor Q_1 . The transistor Q_2 is driven by an internal reference voltage V_{ref} obtained from supply voltage V_{CC} .

Monostable Operation →

Voltage across the capacitor is given by

$$V_C = V_{CC} (1 - e^{-t/RC})$$

$$\text{At } t=T, \quad V_C = 2/3 V_{CC}$$


$$\text{Therefore, } 2/3 V_{CC} = V_{CC} (1 - e^{-T/RC})$$

$$\text{Or } T = RC \ln(1/3)$$


$$\text{Or } T = 1.1 RC \text{ seconds.}$$

Missing pulse detector, Linear Ramp Generator, Frequency divider, pulse width Modulation are output

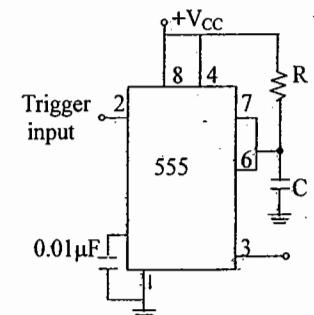the applications of Monostable Operation of 555 timer.



Astable Operation →

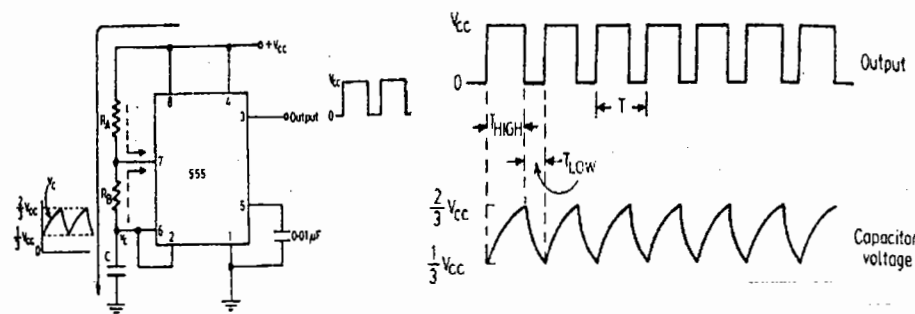

Capacitor voltage for a low pass RC circuit subjected to a step input of V_{CC} volts is given by

$$V_C = V_{CC}(1 - e^{-t/RC})$$

The time t_1 taken by the circuit to charge from 0 to $2/3 V_{CC}$

$$2/3 V_{CC} = V_{CC}(1 - e^{-t_1/RC})$$

$$\text{or } t_1 = 1.09 RC$$

and time t_2 to charge from 0 to $1/3 V_{CC}$ is,

$$1/3 V_{CC} = V_{CC}(1 - e^{-t_2/RC})$$

$$\text{or } t_2 = 0.405 RC$$

so the time to charge from $1/3 V_{CC}$ to $2/3 V_{CC}$ is

$$t_{\text{High}} = t_1 - t_2 = 0.69 RC = 0.69 (R_A + R_B)C$$

The output is low while the capacitor discharges from $2/3 V_{CC}$ to $1/3 V_{CC}$ and the voltage across the capacitor is given by

$$1/3 V_{CC} = 2/3 V_{CC} e^{-t/RC}$$

$$t = 0.69 RC$$

$$t_{\text{Low}} = 0.69 R_B C$$

Notice that both R_A and R_B are in the charge path, but only R_B is in the discharge path.

$$\text{Total time } T = t_{\text{HIGH}} + t_{\text{LOW}} = 0.69 (R_A + 2R_B) C$$

$$\text{So, } f = \frac{1}{T} = \frac{1.45}{(R_A + 2R_B)C}$$

Resistors R_A and R_B could be made variable to allow adjustment of frequency and pulse width. If $R_A = R_B$, then 50% duty cycle is achieved.]


FSK generator, pulse position Modulator are applications of the stable mode of operation of 555 Timer.

Practically a 555 timer is used in oscillators, pulse generators, ramp and square wave generator, monoshot multivibrator, burglar alarm, traffic light control and voltage monitor etc.

OBJECTIVES

1. The circuit shows a 555 Timer IC connected as an astable multivibrator. The value of the capacitor C is 10 nF . The values of the resistors R_A and R_B for a frequency of 10 kHz and a duty cycle of 0.75 for the output voltage waveform are (GATE 2003, EEE)

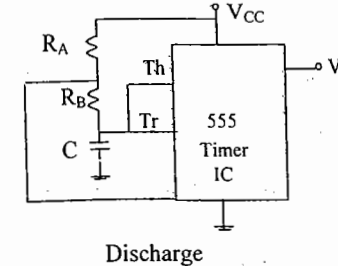
- a) $R_A = 3.62 \text{ k}\Omega$, $R_B = 3.62 \text{ k}\Omega$
 b) $R_A = 3.62 \text{ k}\Omega$, $R_B = 7.25 \text{ k}\Omega$
 c) $R_A = 7.25 \text{ k}\Omega$, $R_B = 3.62 \text{ k}\Omega$
 d) $R_A = 7.25 \text{ k}\Omega$, $R_B = 7.25 \text{ k}\Omega$



Discharge


2. The function of the Diode D in the timer circuit shown below is to (IES 2003, ECE)
- a) Increase the charging time of C

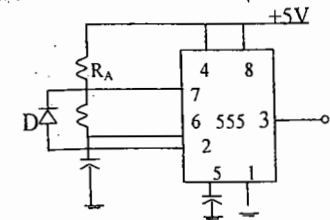- b) Decrease the charging time of C
 c) Increase the discharging time of C
 d) Decrease the discharging time of C




3. Circuit shown in the figure represents (IES '99, ECE)
- a) an astable MV

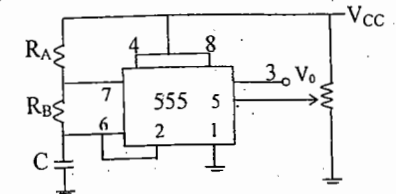- b) a monostable MV
 c) VCO
 d) Ramp generator



4. The output of the circuit shown in the figure will be (IES '97, ECE)
- a) delayed pulses

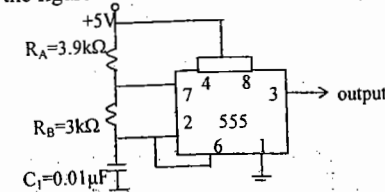- b) square waves
 c) triangular waves
 d) trapezoidal waves




5. The given figure shown the application of 555-timer circuit as an astable multivibrator.

The charging discharging time constants are respectively.

(IES '96, ECE)

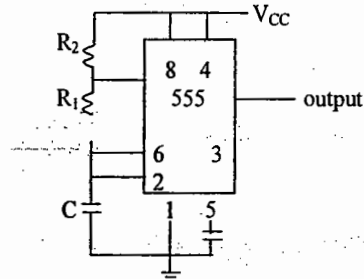- $R_1 C$ and $R_2 C$
- $R_1 C$ and $(R_1 + R_2) C$
- $(R_1 C + R_2) C$ and $R_1 C$
- $R_2 C$ and $R_1 C$



Key: 1.c 2.d 3.a 4.b 5.c


Objective Questions Revision and Practice Set

ONE MARK QUESTIONS

01. The first dominant pole encountered in the frequency response of a compensated op-amp is approximately at
GATE - 1999
- 5 Hz
 - 10 kHz
 - 1 MHz
 - 100 MHz

02. Negative feedback in an amplifier
GATE - 1999
- reduces gain
 - increases frequency and phase distortions
 - reduces bandwidth
 - increases noise

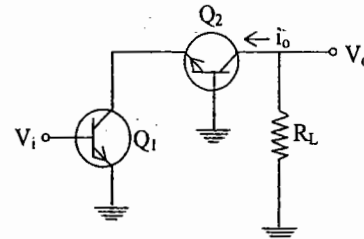
03. In the cascode amplifier shown in the figure, if the common-emitter stage (Q_1) has a transconductance g_{m1} , and the common base stage (Q_2) has a transconductance g_{m2} , then the overall transconductance $g(=i_o/v_i)$ of the cascode amplifier is
GATE - 1999



- g_{m1}
- g_{m2}
- $g_{m1}/2$
- $g_{m2}/2$


04. Crossover distortion behaviour is characteristic of
GATE - 1999
- Class A output stage
 - Class B output stage
 - Class AB output stage
 - Common-base output stage

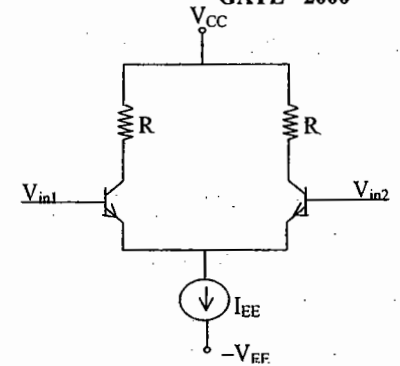05. In the differential amplifier of the figure, if the source resistance of the current source I_{EE} is infinite then the common-mode gain is
GATE - 2000



- zero
- infinite
- indeterminate
- $(V_{in1} + V_{in2})/2V_T$

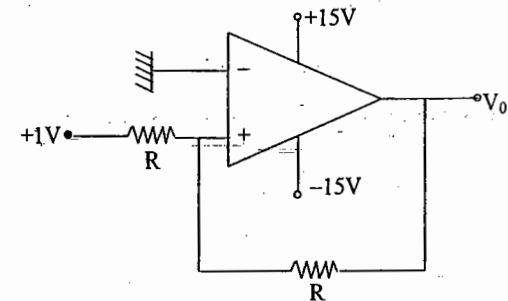06. In the circuit of the figure, V_o is
GATE - 2000



- 1 V
- 2V
- +1V
- +15V

"To win the RACE join the ACE"

"All the best"


07. Introducing a resistor in the emitter of a common emitter amplifier stabilizes the dc operating point against variations in **GATE - 2000**

(a) only the temperature
(b) only the β of the transistor
(c) both temperature and β
(d) none of the above

08. The current gain of a bipolar transistor drops at high frequencies because of **GATE - 2000**

(a) transistor capacitances
(b) high current effects in the base
(c) parasitic inductive elements
(d) the Early effect

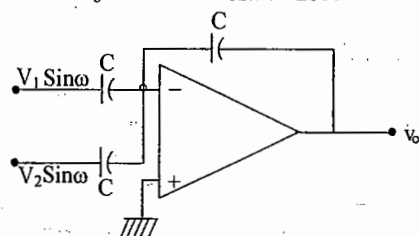09. If the op-amp in the figure, is ideal, then v_o is **GATE - 2000**




(a) zero
(b) $(V_1 - V_2) \sin \omega t$
(c) $-(V_1 + V_2) \sin \omega t$
(d) $(V_1 + V_2) \sin \omega t$

10. The most commonly used amplifier in sample and hold circuits is **GATE- 2000**


(a) a unity gain inverting amplifier
(b) a unity gain non-inverting amplifier
(c) an inverting amplifier with a gain of 10
(d) an inverting amplifier with a gain of 100

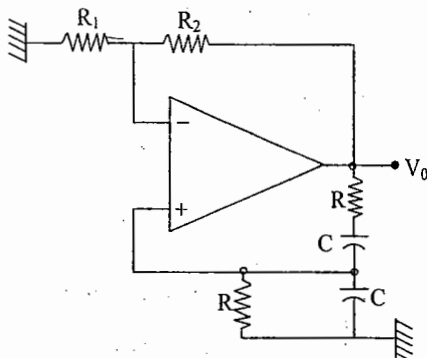11. The configuration of the figure is a **GATE - 2000**



(a) precision integrator
(b) Hartley oscillator
(c) Butterworth high pass filter
(d) Wien-bridge oscillator

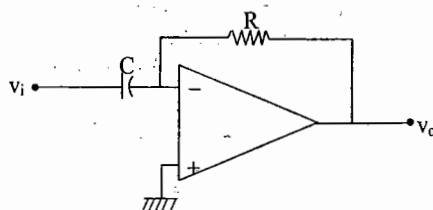12. Assume that the op-amp of the figure is ideal. If v_i is a triangular wave, then v_o will be **GATE - 2000**



(a) square wave
(b) triangular wave
(c) parabolic wave
(d) sine wave

- 13 The current gain of a BJT is **GATE - 2001**

(a) $g_m r_o$ (b) g_m / r_o
(c) $g_m I_E$ (d) g_m / I_E

14. The ideal OP-AMP has the following characteristics. **GATE - 2001**

(a) $R_i = \infty, A = \infty, R_o = 0$
(b) $R_i = 0, A = \infty, R_o = 0$
(c) $R_i = \infty, A = \infty, R_o = \infty$
(d) $R_i = 0, A = \infty, R_o = \infty$

15. Consider the following two statements

Statement 1:

Astable multivibrator can be used for generating square wave.

Statement 2:

Bitable multivibrator can be used for storing binary information






GATE - 2001

(a) Only statement 1 is correct
(b) Only statement 2 is correct
(c) Both the statements 1 and 2 are correct
(d) Both the statements 1 and 2 are incorrect

16. In a negative feedback amplifier using voltage-series (i.e., voltage sampling, series mixing) feedback. **GATE - 2002**

(a) R_i decreases and R_o decreases
(b) R_i decreases and R_o increases
(c) R_i increases and R_o decreases
(d) R_i increases and R_o increases
(R_i and R_o denote the input and output resistances respectively)

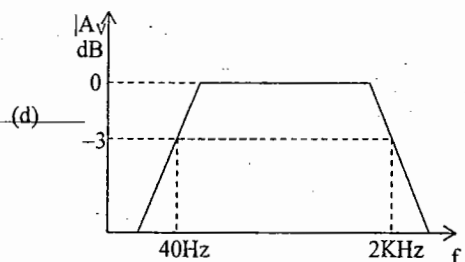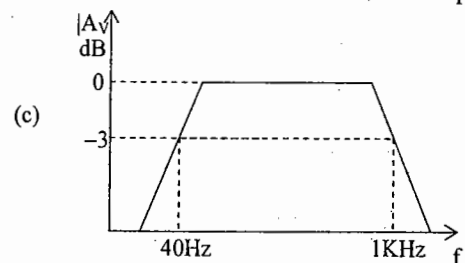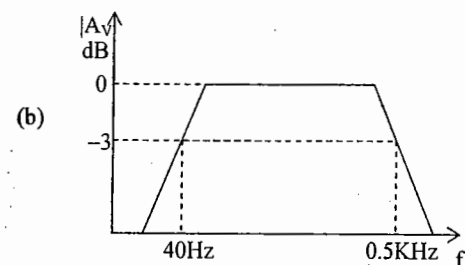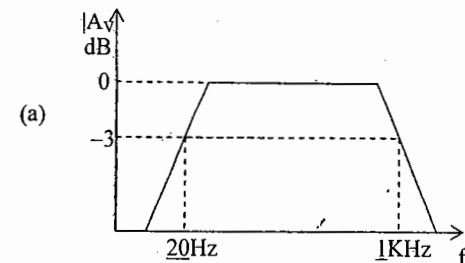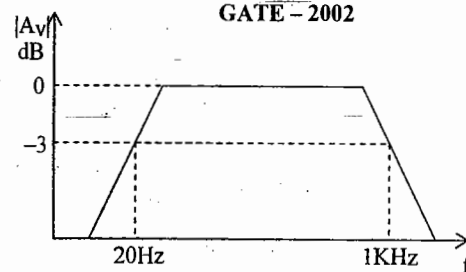17. Three identical RC-coupled transistor amplifiers are cascaded. If each of the amplifiers has a frequency response as shown in the figure, the overall frequency response is as given in **GATE - 2002**



18. A 741-type opamp has a gain-bandwidth product of 1 MHz. A non-inverting amplifier using this opamp and having a voltage gain of 20 dB will exhibit a -3- dB bandwidth of **GATE - 2002**

(a) 50 KHz (b) 100 KHz
(c) 1000/17 KHz (d) 1000/7.07 KHz

19. Choose the correct match for input resistance of various amplifier configurations shown below


Configuration Input resistance

CB: Common Base LO: Low
CC: Common Collector MO: Moderate
CE: Common Emitter HI: high

GATE – 2003


- (a) CB-LO, CC-MO, CE-HI
(b) CB-LO, CC-HI, CE-MO
(c) CB-MO, CC-HI, CE-LO
(d) CB-HI, CC-LO, CE-MO

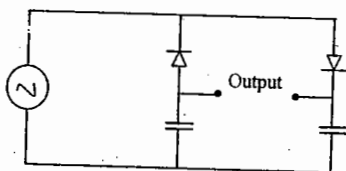20. The circuit shown in the figure is best described as a **GATE – 2003**



- (a) bridge rectifier
(b) ring modulator
(c) frequency discriminator
(d) voltage doubler

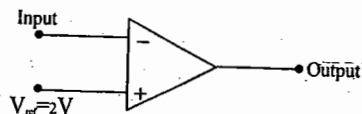21. If the input to the ideal comparator shown in the figure is a sinusoidal signal of 8V (peak to peak) without any DC component, then the output of the comparator has duty cycle of **GATE – 2003**



- (a) 1/2 (b) 1/3
(c) 1/6 (d) 1/12

22. If the differential voltage gain and the common mode voltage gain of a differential amplifier are 48 dB and 2 dB respectively, then its common mode rejection ratio is **GATE – 2003**


- (a) 23 dB (b) 25 dB
(c) 46 dB (d) 50 dB

23. Generally, the gain of a transistor amplifier falls at high frequencies due to the **GATE – 2003**
- (a) internal capacitances of the device
(b) coupling capacitor at the input
(c) skin effect
(d) coupling capacitor at the output

24. An ideal op-amp is an ideal **GATE – 2004**
- (a) voltage controlled current source
(b) voltage controlled voltage source
(c) current controlled current source
(d) current controlled voltage source

25. Voltage series feedback (also called series-shunt feedback) results in **GATE – 2004**
- (a) increase in both input and output impedances
(b) decrease in both input and output impedances
(c) increase in input impedance and decrease in output impedance
(d) decrease in input impedance and increase in output impedance

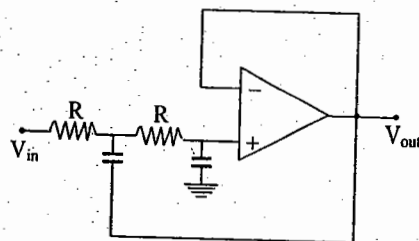
26. The circuit in the figure is a **GATE – 2004**



- (a) low-pass filter
(b) high-pass filter
(c) band-pass filter
(d) band-reject filter


27. Assuming $V_{CEsat} = 0.2V$ and $\beta = 50$, the minimum base current (I_B) required to drive the transistor in the figure to saturation is **GATE – 2004**

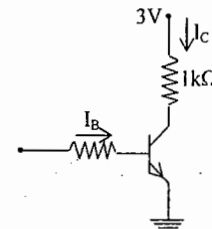- (a) 56 μA
(b) 140 mA
(c) 60 μA
(d) 3 mA



28. The effect of current shunt feedback in an amplifier is to **GATE – 2005**
- (a) increase the input resistance and decrease the output resistance
(b) increase both input and output resistances
(c) decrease both input and output resistances
(d) decrease the input resistance and increase the output resistance

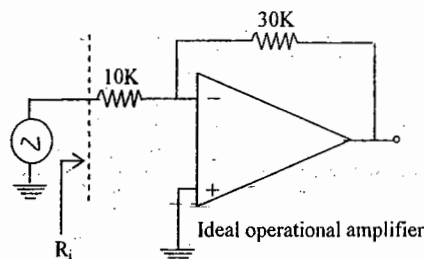29. The input resistance R_i of the amplifier shown in the figure is **GATE – 2005**



- (a) 30/4 kΩ (b) 10 kΩ
(c) 40 kΩ (d) infinite





30. The cascade amplifier is a multistage configuration of **GATE – 2005**
- (a) CC-CB (b) CE-CB
(c) CB-CC (d) CE-CC

31. The input impedance (Z_i) and the output impedance (Z_o) of an ideal transconductance (voltage controlled current source) amplifier are **GATE – 2006**
- (a) $Z_i = 0, Z_o = 0$ (b) $Z_i = 0, Z_o = \infty$
(c) $Z_i = \infty, Z_o = 0$ (d) $Z_i = \infty, Z_o = \infty$

32. An n-channel depletion MOSFET has following two points on its $I_D - V_{GS}$ curve:


- (i) $V_{GS} = 0$ at $I_D = 12$ mA and
(ii) $V_{GS} = -6$ Volts at $I_D = 0$
Which of the following Q-points will give the highest trans-conductance gain for small signals? **GATE – 2006**
- (a) $V_{GS} = -6$ Volts (b) $V_{GS} = -3$ Volts
(c) $V_{GS} = 0$ Volts (d) $V_{GS} = 3$ Volts

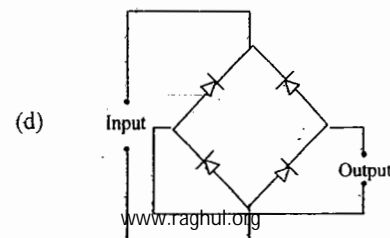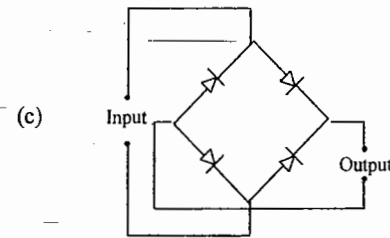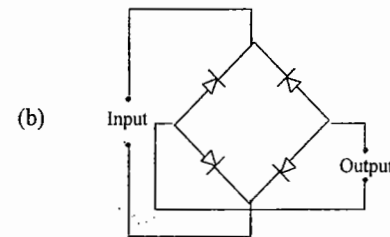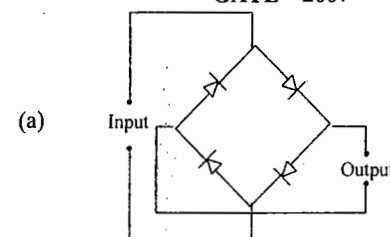33. The correct full wave rectifier is **GATE – 2007**



34. In a transconductance amplifier, it is desirable to have **GATE - 2007**
- a large input resistance and large output resistance
 - a large input resistance and a small output resistance
 - a small input resistance and a large output resistance
 - a small input resistance and a small output resistance

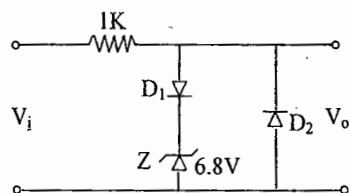35. In the following limiter circuit, an input voltage $V_i = 10 \sin 100\pi t$ is applied. Assume that the diode drop is 0.7 V when it is forward biased. The Zener breakdown voltage is 6.8 V.



The maximum and minimum values of the output voltage respectively are

GATE - 2008

- 6.1 V, -0.7 V
- 0.7 V, -7.5 V
- 7.5 V, -0.7 V
- 7.5 V, -7.5 V

KEY

1. a 2. b 3. a 4. b 5. a 6. d
 7. c 8. a 9. c 10. b 11. d 12. a
 13. c 14. a 15. c 16. c 17. a 18. b
 19. b 20. d 21. b 22. c 23. a 24. b
 25. c 26. a 27. a 28. d 29. b 30. b
 31. d 32. d 33. c 34. a 35. c

TWO MARKS QUESTIONS

01. An npn transistor (with $C_\mu = 0.3$ pF) has a unity-gain cutoff frequency f_T of 400 MHz at dc bias current $I_C = 1$ mA. The value of its C_μ (in pF) is approximately ($V_T = 26$ mV)

GATE - 1999

- 15
- 30
- 50
- 96

02. An amplifier has an open-loop gain of 100, an input impedance of $1\text{ k}\Omega$, and an output impedance of 100Ω . A feedback network with a feedback factor of 0.99 is connected to the amplifier in a voltage series feedback mode. The new input and output impedances respectively, are

GATE - 1999

- 10Ω and 1Ω
- 10Ω and $10\text{ k}\Omega$
- $100\text{ k}\Omega$ and 1Ω
- $100\text{ k}\Omega$ and $10\text{ k}\Omega$

03. A dc power supply has a no-load voltage of 30 V, and a full-load voltage of 25 V at a full-load current of 1 A. Its output resistance and load regulation respectively, are

GATE - 1999

- 5Ω and 20%
- 25Ω and 20%
- 5Ω and 16.7%
- 25Ω and 16.7%


04. An amplifier is assumed to have a single-pole high-frequency transfer function. The rise time of its output response to a step function input is 35 nsec. The upper-3 dB frequency (in MHz) for the amplifier to a sinusoidal input is approximately at

GATE - 1999

- 4.55
- 10
- 20
- 28.6

05. In the circuit of the figure, assume that the transistor is in the active region. It has a large β and its base-emitter voltage is 0.7 V. The value of I_E is


GATE - 2000

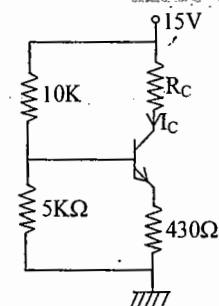

- Indeterminate since R_c is not given
- 1 mA
- 5 mA
- 10 mA

06. If the op-amp in the figure has an input offset voltage of 5 mV and an open-loop voltage gain of 10,000, then v_o will be

GATE - 2000

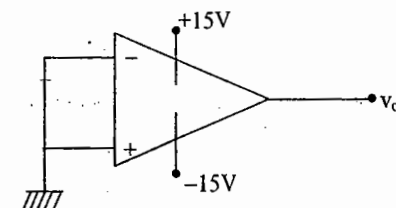

- 0 V
- 5 mV
- +15 V or -15 V
- +50V or -50 V


07. An npn BJT has $g_m = 38 \text{ mA/V}$, $C_\mu = 10^{-14} \text{ F}$, $C_\pi = 4 \times 10^{-13} \text{ F}$, and DC current gain $\beta_o = 90$. For this transistor f_T and f_β are

GATE - 2001

- (a) $f_T = 1.64 \times 10^8 \text{ Hz}$ and $f_\beta = 1.47 \times 10^{10} \text{ Hz}$
 (b) $f_T = 1.47 \times 10^{10} \text{ Hz}$ and $f_\beta = 1.64 \times 10^8 \text{ Hz}$
 (c) $f_T = 1.33 \times 10^{12} \text{ Hz}$ and $f_\beta = 1.47 \times 10^{10} \text{ Hz}$
 (d) $f_T = 1.47 \times 10^{10} \text{ Hz}$ and $f_\beta = 1.33 \times 10^{12} \text{ Hz}$

08. The transistor shunt regulator shown in the figure has a regulated output voltage of 10 V, when the input varies from 20 V to 30 V. The relevant parameters for the zener diode and the transistor are: $V_Z = 9.5 \text{ V}$, $V_{BE} = 0.3 \text{ V}$, $\beta = 99$. Neglect the current through R_B . Then the maximum power dissipated in the zener diode (P_Z) and the transistor (P_T) are


GATE - 2001

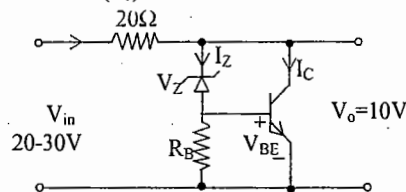

- (a) $P_Z = 75 \text{ mW}$, $P_T = 7.9 \text{ W}$
 (b) $P_Z = 85 \text{ mW}$, $P_T = 8.9 \text{ W}$
 (c) $P_Z = 95 \text{ mW}$, $P_T = 9.9 \text{ W}$
 (d) $P_Z = 115 \text{ mW}$, $P_T = 11.9 \text{ W}$

09. The oscillator circuit shown in the figure is

GATE - 2001

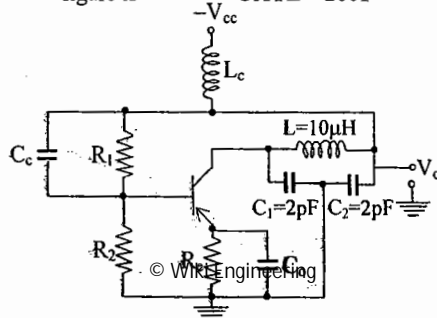


- (a) Hartley oscillator with $f_{\text{oscillation}} = 79.6 \text{ MHz}$
 (b) Colpitts oscillator with $f_{\text{oscillation}} = 79.6 \text{ MHz}$
 (c) Hartley oscillator with $f_{\text{oscillation}} = 159.2 \text{ MHz}$
 (d) Colpitts oscillator with $f_{\text{oscillation}} = 159.2 \text{ MHz}$

10. The inverting OP-AMP shown in the figure has an open-loop gain of 100.

The closed-loop gain $\frac{V_o}{V_s}$ is


GATE - 2001

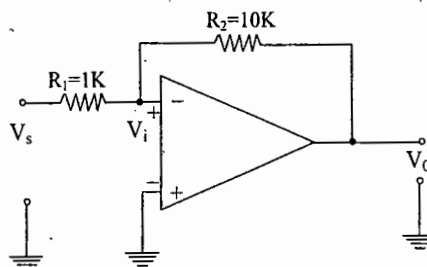

- (a) -8
 (b) -9
 (c) -10
 (d) -11

11. In the figure assume the OP-AMPs to be ideal. The output V_o of the circuit is

GATE - 2001

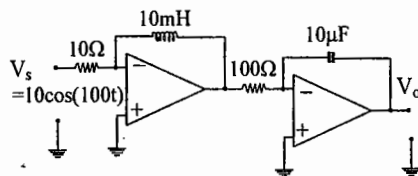

- (a) $10\cos(100t)$ (b) $10 \int \cos(100\tau) d\tau$
 (c) $10^{-4} \int \cos(100\tau) d\tau$
 (d) $10^{-4} \frac{d}{dt} \cos(100\tau)$

12. An amplifier using an opamp with a slew-rate $SR = 1 \text{ V}/\mu\text{sec}$ has a gain of 40 dB. If this amplifier has to faithfully amplify sinusoidal signals from dc to 20 KHz without introducing any slew-rate induced distortion, then the input signal level must not exceed.

GATE - 2002

- (a) 795 mV (b) 395 mV
 (c) 79.5 mV (d) 39.5 mV

13. An amplifier without feedback has a voltage gain of 50, input resistance of $1 \text{ K}\Omega$ and output resistance of $2.5 \text{ k}\Omega$. The input resistance of the current-shunt negative feedback amplifier using the above amplifier with a feedback factor of 0.2 is


GATE - 2003

- (a) $1/11 \text{ K}\Omega$ (b) $1/5 \text{ K}\Omega$
 (c) $5 \text{ K}\Omega$ (d) $11 \text{ K}\Omega$

14. The circuit in the figure employs positive feedback and is intended to generate sinusoidal oscillation. If at a frequency f_o , then to sustain oscillation at this frequency

$$B(f) = \frac{V_o(f)}{V_i(f)} = \frac{1}{6} \angle 0^\circ$$


GATE - 2002

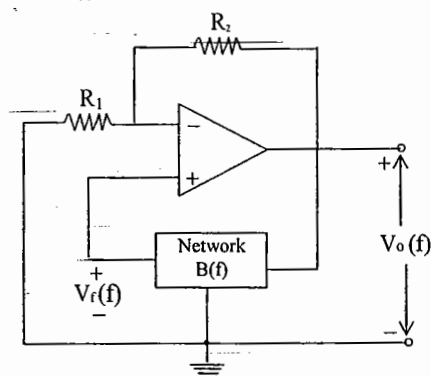

- (a) $R_2 = 5 R_1$ (b) $R_2 = 6 R_1$
 (c) $R_2 = \frac{R_1}{6}$ (d) $R_2 = \frac{R_1}{5}$

15. A zener diode regulator in the figure is to be designed to meet the specifications: $I_L = 10 \text{ mA}$, $V_o = 10 \text{ V}$ and V_{in} varies from 30 V to 50 V. The zener diode has $V_Z = 10 \text{ V}$ and I_{zk} (knee current) = 1 mA. For satisfactory operation.


GATE - 2002

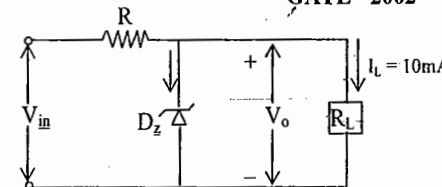

- (a) $R \leq 1800 \Omega$
 (b) $2000 \Omega \leq R \leq 2200 \Omega$
 (c) $3700 \Omega \leq R \leq 4000 \Omega$
 (d) $R > 4000 \Omega$

16. The voltage gain $A_v = V_o / V_i$ of the JFET amplifier shown in the figure is


GATE - 2002

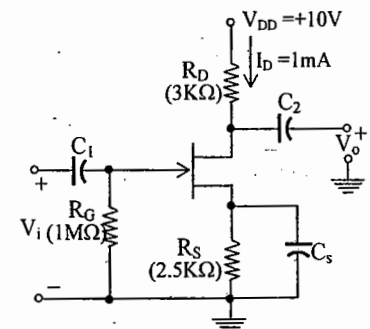

$I_{DSS} = 10 \text{ mA}$ $V_p = -5 \text{ V}$
 (Assume C_1 , C_2 and C_3 to be very large)

- (a) +18 (b) -18
 (c) +6 (d) -6

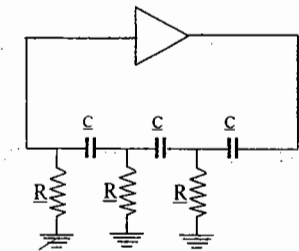17. The oscillator circuit shown in the figure has an ideal inverting amplifier. Its frequency of oscillation (in Hz) is
GATE - 2003




- (a) $\frac{1}{(2\pi\sqrt{6}RC)}$ (b) $\frac{1}{(2\pi 2\pi R)}$
(c) $\frac{1}{(\sqrt{6}RC)}$ (d) $\frac{\sqrt{6}}{(2\pi 2\pi R)}$

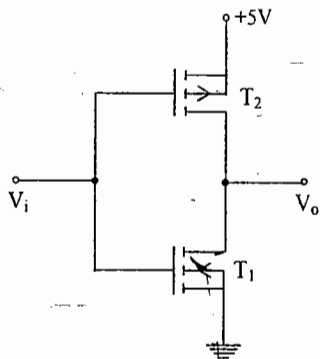18. Consider the following statements in connection with the CMOS inverter in the figure, where both the MOSFETs are of enhancement type and both have a threshold voltage of 2V.

Statement 1: T_1 conducts when $V_i \geq 2V$.


Statement 2: T_1 is always in saturation when $V_o = 0V$.



Which of the following is correct?
GATE - 2002


- (a) Only Statement 1 is TRUE
(b) Only Statement 2 is TRUE
(c) Both the Statements are TRUE
(d) Both the Statements are FALSE

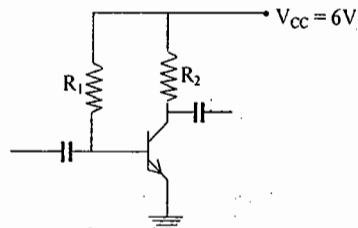19. In the amplifier circuit shown in the figure, the values of R_1 and R_2 are such that the transistor is operating at $V_{CE} = 3V$ and $I_C = 1.5mA$ when its β is 150. For a transistor with β of 200, the operating point (V_{CE} , I_C) is
GATE - 2003



- (a) (2V, 2mA) (b) (3V, 2mA)
(c) (4V, 2mA) (d) (4V, 1mA)

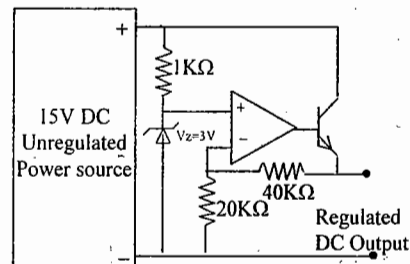20. The output voltage of the regulated power supply shown in the figure is
GATE - 2003




- (a) 3 V (b) 6 V
(c) 9 V (d) 12 V

21. The action of a JFET in its equivalent circuit can best be represented as a
GATE - 2003

- (a) Current Controlled Current Source
(b) Current Controlled Voltage Source
(c) Voltage Controlled Voltage Source
(d) Voltage Controlled Current Source

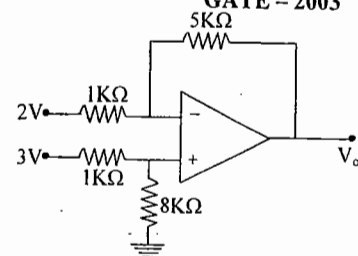22. If the op-amp in the figure is ideal, the output voltage V_{out} will be equal to
GATE - 2003



- (a) 1 V (b) 6 V
(c) 14 V (d) 17 V

23. Three identical amplifiers with each one having a voltage gain of 50, input resistance of $1k\Omega$ and output resistance of 250Ω , are cascaded. The open circuit voltage gain of the combined amplifier is
GATE - 2003

- (a) 49 dB (b) 51 dB
(c) 98 dB (d) 102 dB


24. An ideal sawtooth voltage waveform of frequency 500 Hz and amplitude 3 V is generated by charging a capacitor of $2\mu F$ in every cycle. The charging requires
GATE - 2003

- (a) constant voltage source of 3 V for 1 ms
(b) constant voltage source of 3 V for 2 ms
(c) constant current source of 3 mA for 1 ms
(d) constant current source of 3 mA for 2 ms

25. A bipolar transistor is operating in the active region with a collector current of 1 mA. Assuming that β of the transistor is 100 and the thermal voltage (V_T) is 25 mV, the transconductance (g_m) and the input resistance (r_π) of the transistor in the common emitter configuration, are
GATE - 2004


- (a) $g_m = 25mA/V$ and $r_\pi = 15.625 k\Omega$
(b) $g_m = 40mA/V$ and $r_\pi = 4.0 k\Omega$
(c) $g_m = 25mA/V$ and $r_\pi = 2.5 k\Omega$
(d) $g_m = 40mA/V$ and $r_\pi = 2.5 k\Omega$

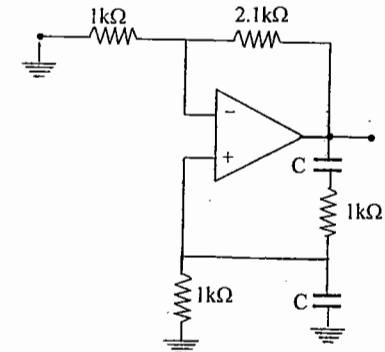26. The value of C required for sinusoidal oscillations of frequency 1 kHz in the circuit of the figure is
GATE - 2004




- (a) $\frac{1}{2\pi} \mu F$ (b) $2\pi \mu F$
(c) $\frac{1}{2\pi\sqrt{6}} \mu F$ (d) $2\pi\sqrt{6} \mu F$

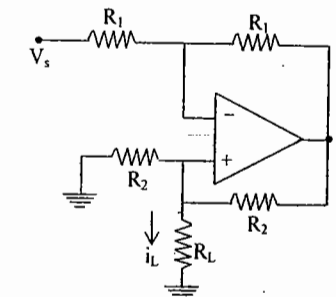27. In the op-amp circuit given in the figure, the load current i_L is
GATE - 2004



- (a) $-\frac{V_s}{R_2}$ (b) $\frac{V_s}{R_2}$ (c) $-\frac{V_s}{R_L}$ (d) $\frac{V_s}{R_L}$

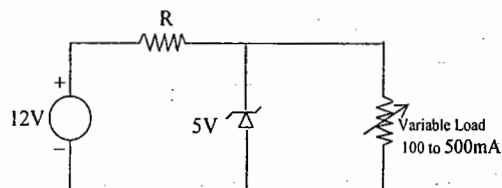28. In the voltage regulator shown in the figure, the load current can vary from 100 mA to 500 mA. Assuming that the Zener diode is ideal (i.e., the Zener knee current is negligibly small and Zener resistance is zero in the breakdown region), the value of R is
GATE – 2004




- (a) 7Ω (b) 70Ω
(c) $70/3\Omega$ (d) 14Ω

29. In a full-wave rectifier using two ideal diodes, V_{dc} and V_m are the dc and peak values of the voltage respectively across a resistive load. If PIV is the peak inverse voltage of the diode, then the appropriate relationships for this rectifier are
GATE – 2004


- (a) $V_{dc} = \frac{V_m}{\pi}$, $PIV = 2V_m$
(b) $V_{dc} = 2\frac{V_m}{\pi}$, $PIV = 2V_m$
(c) $V_{dc} = 2\frac{V_m}{\pi}$, $PIV = V_m$
(d) $V_{dc} = \frac{V_m}{\pi}$, $PIV = V_m$

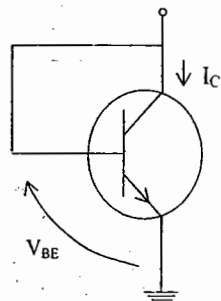30. For an npn transistor connected as shown in the figure, $V_{BE} = 0.7$ volts. Given that reverse saturation current of the junction at room temperature 300°K is 10^{-13} A , the emitter current is
GATE – 2005




- (a) 30 mA (b) 39 mA
(c) 49 mA (d) 20 mA

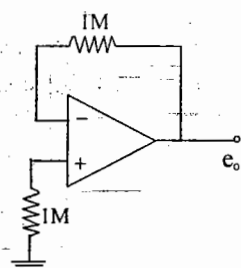31. The voltage e_o indicated in the figure has been measured by an ideal voltmeter. Which of the following can be calculated?
GATE – 2005




- (a) Bias current of the inverting input only
(b) Bias current of the inverting and non-inverting inputs only
(c) Input offset current only
(d) Both the bias currents and the input offset current

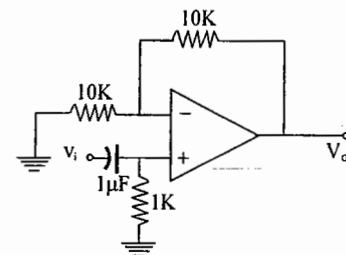32. The op-amp circuit shown in the figure is a filter. The type of filter and its cut-off frequency are respectively
GATE – 2005




- (a) high pass, 1000 rad/sec.
(b) low pass, 1000 rad/sec.
(c) high pass, 10000 rad/sec.
(d) low pass, 10000 rad/sec.

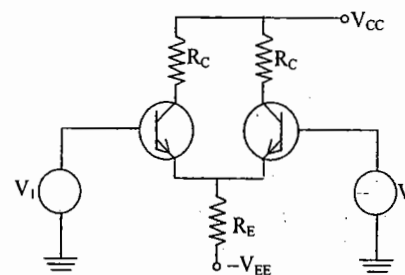33. In an ideal differential amplifier shown in the figure, a large value of R_E
GATE – 2005




- (a) increases both the differential and common-mode gains
(b) increases the common-mode gain only
(c) decreases the differential-mode gain only
(d) decreases the common-mode gain only.

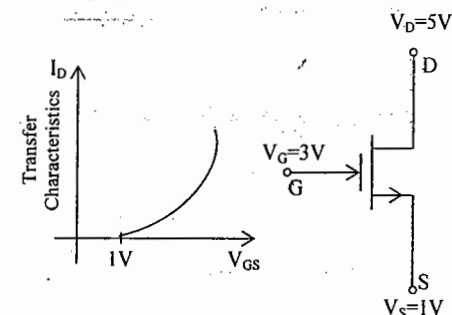34. For an n-channel MOSFET and its transfer curve shown in the figure, the threshold voltage is GATE – 2005



- (a) 1 V and the device is in active region
(b) -1 V and the device is in saturation region
(c) 1 V and the device is in saturation region
(d) -1 V and the device is in active region.

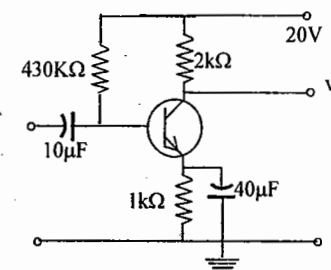
35. The circuit using a BJT with $\beta = 50$ and $V_{BE} = 0.7\text{ V}$ is shown in the figure. The base current I_B and collector voltage V_C are respectively
GATE – 2005



- (a) 43 μA and 11.4 Volts
(b) 40 μA and 16 Volts
(c) 45 μA and 11 Volts
(d) 50 μA and 10 Volts

36. The zener diode in the regulator circuit shown in the figure has a zener voltage of 5.8 volts and a zener knee current of 0.5 mA. The maximum load current drawn from this circuit ensuring proper functioning over the input voltage range between 20 and 30 volts is






GATE - 2005

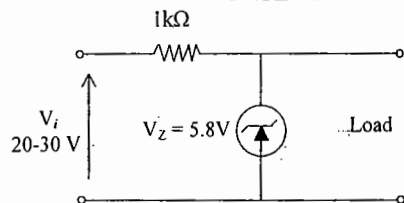

- (a) 23.7 mA (b) 14.2 mA
(c) 13.7 mA (d) 24.2 mA

37. Given the ideal operational amplifier circuit shown in the figure indicate the correct transfer characteristics assuming ideal diodes with zero cut-in voltage.


GATE - 2005

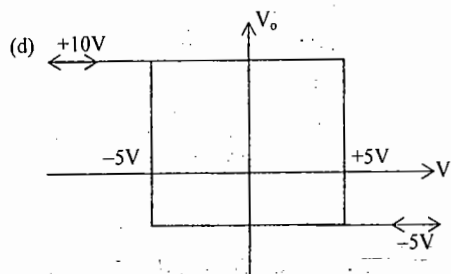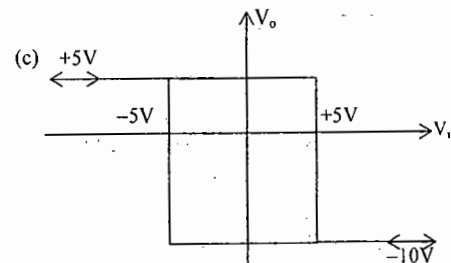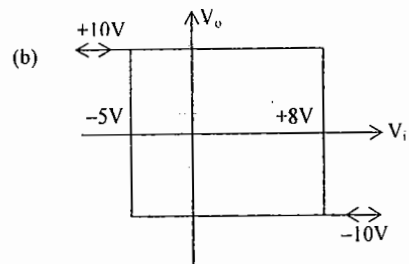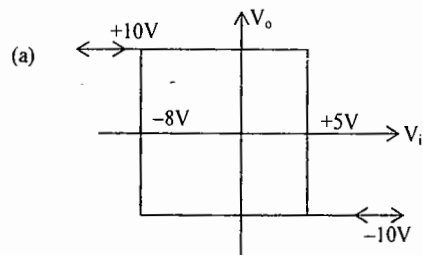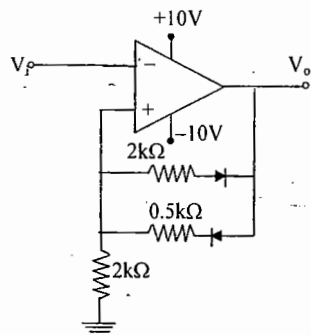

Common Data Questions 38, 39, 40

Given, $r_d = 20 \text{ k}\Omega$, $I_{DSS} = 10 \text{ mA}$,
 $V_p = -8 \text{ V}$

GATE - 2005

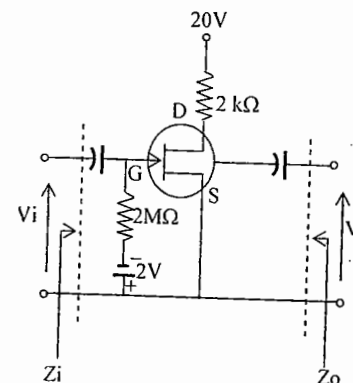

38. Z_i and Z_o of the circuit are respectively
GATE - 2005

- (a) 2 MΩ and 2 kΩ
(b) 2 MΩ and 20/11 kΩ
(c) infinity and 2 kΩ
(d) infinity and 20/11 kΩ,


39. I_D and V_{DS} under DC conditions are respectively
GATE - 2005

- (a) 5.625 mA and 8.75 V
(b) 7.500 mA and 5.00 V
(c) 4.500 mA and 11.00 V
(d) 6.250 mA and 7.50 V

40. Transconductance in milli-Siemens (mS) and voltage gain of the amplifier are respectively. GATE - 2005

- (a) 1.875 mS and 3.41
(b) 1.875 mS and -3.41
(c) 3.3 mS and -6
(d) 3.3 mS and 6


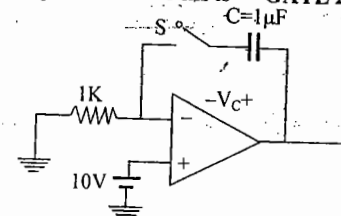
41. For the circuit shown in the following figure, the capacitor C is initially uncharged. At $t = 0$, the switch S is closed. The voltage V_C across the capacitor at $t = 1 \text{ ms}$ is
GATE 2006



In the figure shown above, the OP-AMP is supplied with $\pm 15 \text{ V}$.

- (a) 0 Volt (b) 6.3 Volts
(c) 9.45 Volts (d) 10 Volts

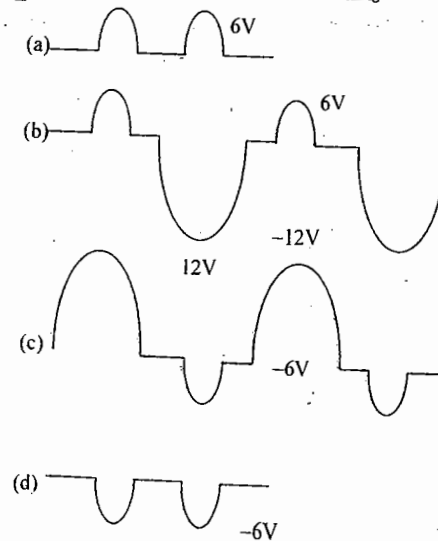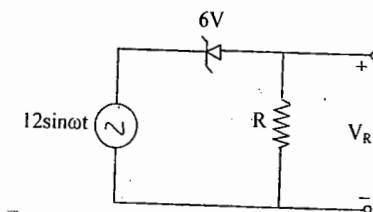
42. For the circuit shown below, assume that the zener diode is ideal with a breakdown voltage of 6 volts. The waveform observed across R is
GATE - 2006



Common Data for Questions 43, 44 & 45.

In the transistor amplifier circuit shown in the figure below, the transistor has the following parameters:

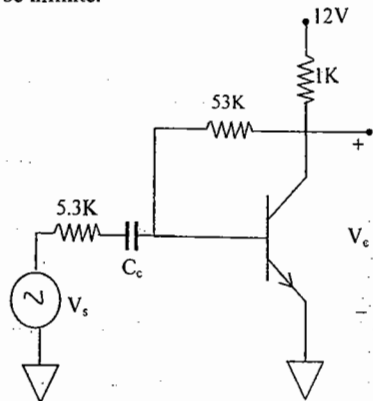$\beta_{DC} = 60$, $V_{BE} = 0.7$ V, $h_{ie} \rightarrow \infty$, $h_{fe} \rightarrow \infty$
The capacitance C_C can be assumed to be infinite.



In the figure above, the ground has been shown by the symbol ∇

GATE - 2006

43. Under the DC conditions, the collector-to-emitter voltage drop is
(a) 4.8 Volts (b) 5.3 Volts
(c) 6.0 Volts (d) 6.6 Volts


44. If β_{DC} is increased by 10%, the collector-to-emitter voltage drop
(a) increases by less than or equal to 10%
(b) decreases by less than or equal to 10%
(c) increases by more than 10%
(d) decreases by more than 10%

45. The small-signal gain of the amplifier V_c/V_s is
(a) -10 (b) -5.3
(c) 5.3 (d) 10

GATE - 2006

Statement for Linked Answer 46 & 47.

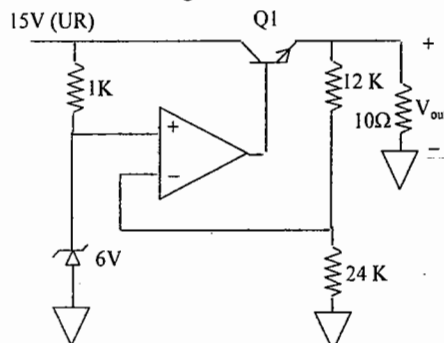A regulated power supply, shown in figure below, has an unregulated input (UR) of 15 V and generates a regulated output V_{out} . Use the component values shown in the figure.




In the figure above, the ground has been shown by the symbol ∇

GATE - 2006

46. The power dissipation across the transistor Q1 shown in the figure is
(a) 4.8 Watts (b) 5.0 Watts
(c) 5.4 Watts (d) 6.0 Watts
47. If the unregulated voltage increases by 20% the power dissipation across the transistor Q1..
(a) increases by 20%
(b) increases by 50%
(c) remains unchanged
(d) decreases by 20%

48. For the Op-Amp circuit shown in the figure, V_o is

GATE - 2007

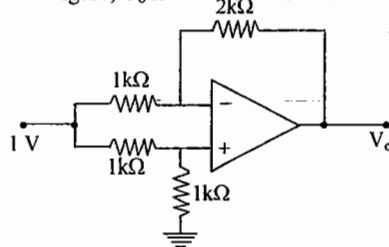


- (a) -2V (b) -1 V
(c) -0.5 V (d) 0.5 V

49. The DC current gain (β) of a BJT is 50. Assuming that the emitter injection efficiency is 0.995, the base transport factor is
(a) 0.980 (b) 0.985
(c) 0.990 (d) 0.995

GATE - 2007

50. For the BJT circuit shown, assume that the β of the transistor is very large and $V_{BE} = 0.7$ V. The mode of operation of the BJT is


GATE - 2007

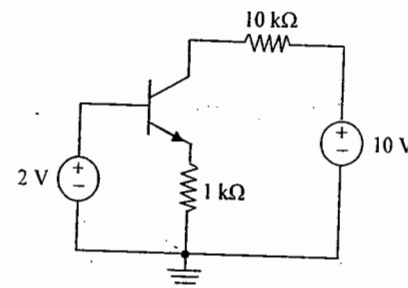

- (a) cut-off (b) saturation
(c) normal active (d) reverse active

51. In the Op-Amp circuit shown, assume that the diode current follows the equation $I = I_s \exp(V/V_T)$. For $V_i = 2$ V, $V_o = V_{o1}$, and for $V_i = 4$ V, $V_o = V_{o2}$. The relationship between V_{o1} and V_{o2} is


GATE - 2007

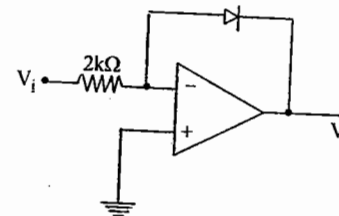

- (a) $V_{o2} = \sqrt{2} V_{o1}$
(b) $V_{o2} = e^2 V_{o1}$
(c) $V_{o2} = V_{o1} \ln 2$
(d) $V_{o1} - V_{o2} = V_T \ln 2$

52. In the CMOS inverter circuit shown, if the transconductance parameters of the NMOS and PMOS transistors are $k_n = k_p = \mu_n C_{ox}$
 $\frac{W_n}{L_n} = \mu_n C_{ox} \frac{W_p}{L_p} = 40 \mu A/V^2$ and their threshold voltages are $V_{THn} = |V_{THp}| = 1$ V, the current I is


GATE - 2007

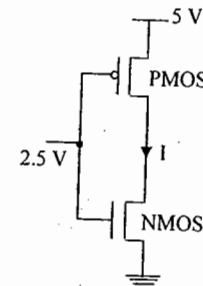

- (a) 0 A (b) 25 μA
(c) 45 μA (d) 90 μA

53. For the Zener diode shown in the figure, the Zener voltage at knee is 7 V, the knee current is negligible and the Zener dynamic resistance is 10 Ω . If the input voltage (V_i) range is from 10 to 16V, the output voltage (V_o) ranges from


GATE - 2007

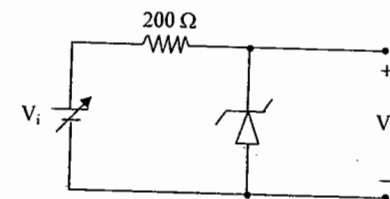

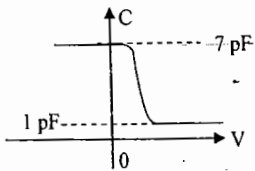- (a) 7.00 to 7.29 V (b) 7.14 to 7.29 V
(c) 7.14 to 7.43 V (d) 7.29 to 7.43 V

Common Data for Questions 54, 55, 56 :

The figure shows the high-frequency capacitance-voltage (C-V) characteristics of a Metal/SiO₂/silicon (MOS) capacitor having an area of $1 \times 10^{-4} \text{ cm}^2$. Assume that the permittivities ($\epsilon_0 \epsilon_r$) of silicon and SiO₂ are $1 \times 10^{-12} \text{ F/cm}$ and $3.5 \times 10^{-13} \text{ F/cm}$ respectively.



54. The gate oxide thickness in the MOS capacitor is **GATE - 2007**

- (a) 50 nm (b) 143 nm
(c) 350 nm (d) 1 μm

55. The maximum depletion layer width in silicon is **GATE - 2007**

- (a) 0.143 μm (b) 0.857 μm
(c) 1 μm (d) 1.143 μm


56. Consider the following statements about the C-V characteristics plot:
S1 : The MOS capacitor has as n-type substrate.
S2 : If positive charges are introduced in the oxide, the C-V plot will shift to the left.

Then which of the following is true?

GATE - 2007

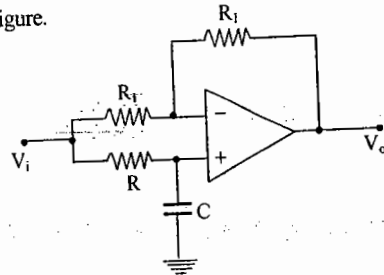- (a) Both S1 and S2 are true
(b) S1 is true and S2 is false
(c) S1 is false and S2 is true
(d) Both S1 and S2 are false

Statement for Linked Answer Questions 57 & 58 :
Consider the Op-Amp circuit shown in the figure.



57. The transfer function $V_o(s)/V_i(s)$ is **GATE - 2007**

- (a) $\frac{1-sRC}{1+sRC}$ (b) $\frac{1+sRC}{1-sRC}$
(c) $\frac{1}{1-sRC}$ (d) $\frac{1}{1+sRC}$


58. If $V_i = V_1 \sin(\omega t)$ and $V_o = V_2 V_1 \sin(\omega t + \phi)$, then the minimum and maximum values of ϕ (in radians) are respectively **GATE - 2007**

- (a) $-\pi/2$ and $\pi/2$ (b) 0 and $\pi/2$
(c) $-\pi$ and 0 (d) $-\pi/2$ and 0

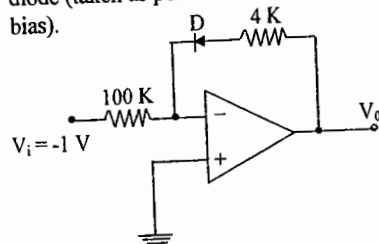59. Consider the following circuit using an ideal OPAMP. The I-V characteristics of the diode is described by the relation

$$I = I_o \left(e^{\frac{V}{V_T}} - 1 \right) \text{ where } V_T = 25 \text{ mV, } I_o = 1 \mu\text{A}$$

and V is the voltage across the diode (taken as positive for forward bias).




For an input voltage $V_i = -1 \text{ V}$, the output voltage V_o is

GATE - 2008

- (a) 0 V (b) 0.1 V
(c) 0.7 V (d) 1.1 V

60.

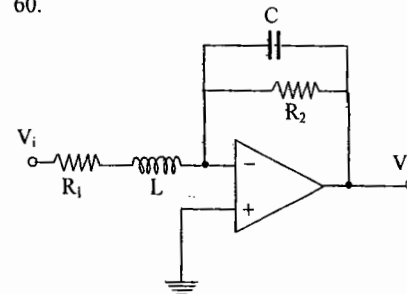


The OPAMP circuit shown above represents a **GATE - 2008**

- (a) high pass filter
(b) low pass filter
(c) band pass filter
(d) band reject filter

51. Two identical NMOS transistors M1 and M2 are connected as shown below. V_{bias} is chosen so that both transistors are in saturation. The equivalent g_m of the pair is defined to be $\frac{\partial I_{\text{out}}}{\partial V_i}$ at

constant V_{out} .

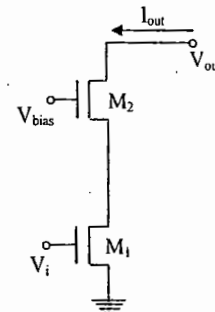


The equivalent g_m of the pair is

GATE - 2008

- (a) the sum of individual g_m 's of the transistors
(b) the product of individual g_m 's of the transistors
(c) nearly equal to the g_m of M1
(d) nearly equal to g_m/g_o of M2

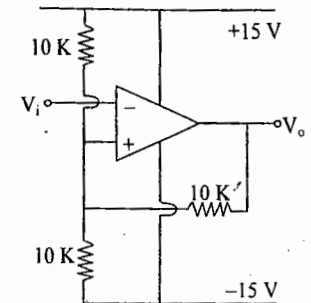62. Consider the Schmidt trigger circuit shown below.




A triangular wave which goes from -12 V to 12 V is applied to the inverting input of the OPAMP. Assume that the output of the OPAMP swings from +15 V to -15 V. The voltage at the non-inverting input switches between.

GATE - 2008

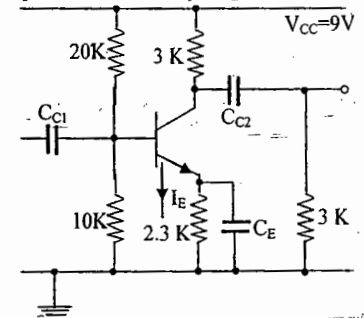- (a) -12 V and +12 V
(b) -7.5 V and +7.5 V
(c) -5 V and +5 V
(d) 0 V and 5 V

Statement for linked Answer Questions 63 and 64:

In the following transistor circuit, $V_{BE} = 0.7 \text{ V}$, $r_e = 25 \text{ mV}/I_E$, and β and all the capacitances are very large.




63. The value of DC current I_E is

- (a) 1 mA (b) 2 mA
(c) 5 mA (d) 10 mA

64. The mid-band voltage gain of the amplifier is approximately.


- (a) -180 (b) -120
(c) -90 (d) -60

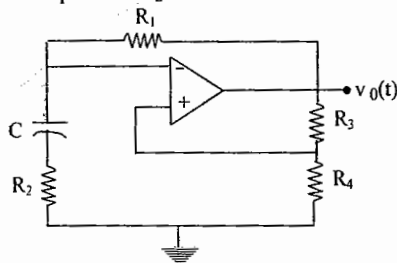65. In the following astable multivibrator circuit, which properties of $v_o(t)$ depend on R_2 ? GATE - 2009




- (a) Only the frequency
(b) Only the amplitude
(c) both the amplitude and the frequency
(d) Neither the amplitude nor the frequency

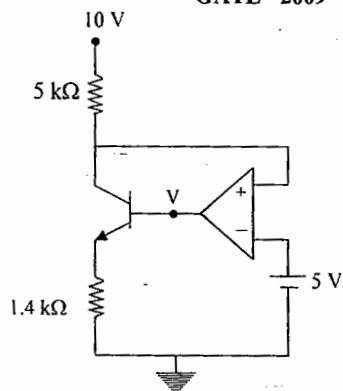66. In the circuit shown below, the op-amp is ideal, the transistor has $V_{BE} = 0.6$ V and $\beta = 150$. Decide whether the feedback in the circuit is positive or negative and determine the voltage V at the output of the op-amp. GATE - 2009



- (a) Positive feedback, $V = 10$ V
(b) Positive feedback, $V = 0$ V
(c) Negative feedback, $V = 5$ V
(d) Negative feedback, $V = 2$ V

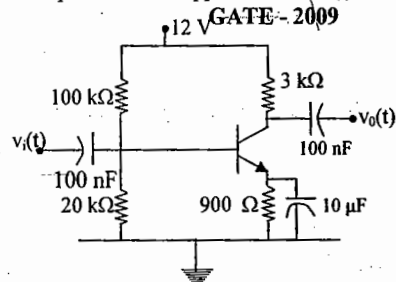67. A small signal source $v_i(t) = A \cos 20t + B \sin 10^6 t$ is applied to a transistor amplifier as shown below. The transistor has $\beta = 150$ and $h_{ie} = 3$ k Ω . Which expression best approximates $v_o(t)$? GATE - 2009



- (a) $v_o(t) = -1500(A \cos 20t + B \sin 10^6 t)$
(b) $v_o(t) = -150(A \cos 20t + B \sin 10^6 t)$
(c) $v_o(t) = -1500 B \sin 10^6 t$
(d) $v_o(t) = -150 B \sin 10^6 t$

68. Which one of the following type of negative feedback increases the input resistance and decreases the output resistance of an amplifier? IES 2009

- (a) Current series feedback
(b) Voltage series feedback
(c) Current shunt feedback
(d) Voltage shunt feedback

69. Consider a 565 PLL with $R_T = 10$ k Ω and $C_T = 0.01$ μ F. What is the output frequency of the V_{CO} ? IES 2009

- (a) 10 kHz (b) 5 kHz
(c) 2.5 kHz (d) 1.25 kHz

KEY

1. a 2. c 3. b 4. b 5. d 6. c
7. b 8. c 9. b 10. b 11. a 12. c
13. a 14. a 15. a 16. d 17. a 18. c
19. a 20. c 21. d 22. b 23. c 24. d
25. d 26. a 27. a 28. d 29. b 30. c
31. c 32. a 33. d 34. c 35. b 36. a
37. b 38. b 39. a 40. b 41. d 42. b
43. c 44. b 45. a 46. d 47. b 48. c
49. b 50. b 51. d 52. d 53. c 54. a
55. c 56. d 57. a 58. c 59. b 60. b
61. c 62. c 63. a 64. d 65. 66.
67. 68. 69.

OUR GATE 2010 TOPPERS

ELECTRONICS & COMMUNICATION ENGINEERING TOPPERS

S.NO	STUDENT NAME	GATE H.T NO	RANK
01	HARINARAYANAN K K	EC-7158116	1
02	SHAIK AZEEMUDDIN	EC-1430532	6
03	SREEKAR S	EC-7006081	9

COMPUTER SCIENCE & ENGINEERING TOPPERS

S.NO	STUDENT NAME	GATE H.T NO	RANK
01	MALLADI HARIKRISHNA	CS-1390148	1
02	ADINARAYANA PULAPARTHI	CS-6109316	8

MECHANICAL ENGINEERING TOPPERS

S.NO	STUDENT NAME	GATE H.T NO	RANK
01	GAURAV NAIR	ME-1530117	4
02	MITHUN P	ME-1560133	9

ELECTRICAL ENGINEERING TOPPERS

S.NO	STUDENT NAME	GATE H.T NO	RANK
01	C VEERAAIAH	EE-1010022	5
02	THEJOSWAMY NAIDU B	EE-1490267	7

INSTRUMENTATION ENGINEERING TOPPERS

S.NO	STUDENT NAME	GATE H.T NO	RANK
01	KAMANI DEEPESH HASMUKHLAL	IN-1290044	6
02	KARTHIKEYAN S	IN-1290364	8

CIVIL ENGINEERING TOPPERS

S.NO	STUDENT NAME	GATE H.T NO	RANK
01	ACHARYA PRERANA U	CE-1270825	9

